

JANUARY 1987 / \$2.50

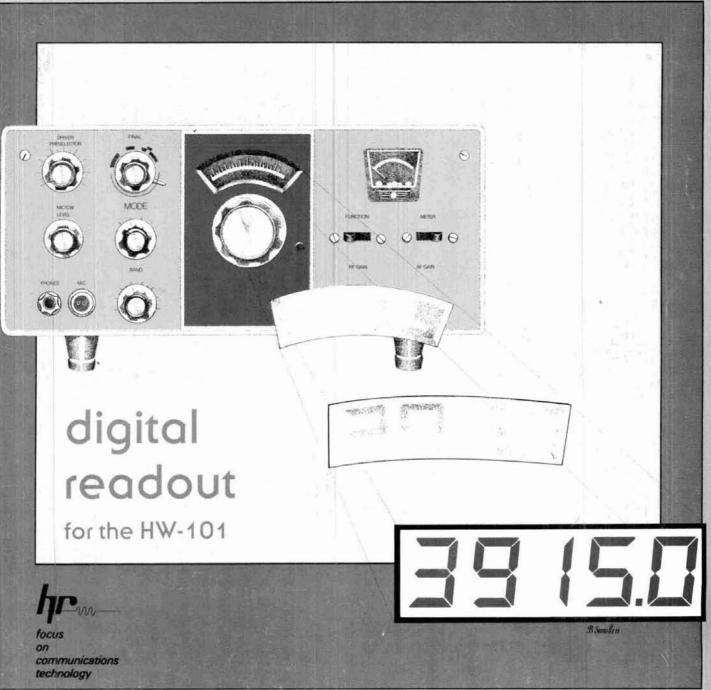

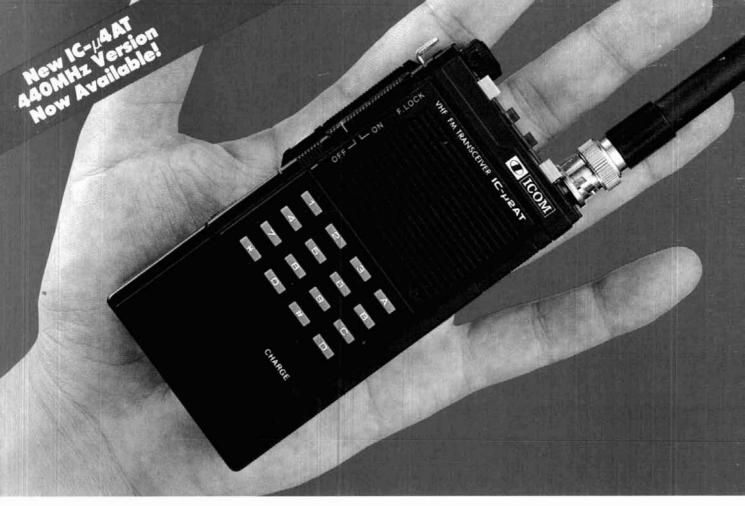



# ICOM MICRO ONLY ICOM COULD BUILD IT!

#### A new micro-sized 2-meter handheld with all the performance and reliability you've come to expect from an ICOM!

The IC- $\mu$ 2AT. A breakthrough that ends every amateur radio operator's quest for that one true, go-anywhere 2-meter handheld.

Miniaturization. The Micro gives you all the advantages and performance of a larger handheld, in a package so small, so refined, so well built that only ICOM could build it.

Measuring only 4.6" high by 2.3" wide, by 1.1" deep, the Micro fits in your pocket or purse as easily as a cassette tape. This miniaturization doesn't compromise ICOM quality. It's exactly what you'd expect from ICOM: high performance in a micro package.

Full Featured. And ICOM hasn't compromised features for size. The IC-µ2AT DTMF version includes ten


programmable memories, odd offset capability, an LCD readout on the top



panel for easy readability, up to three watts of output (optional), 32 built-in subaudible tones AND wideband receive coverage from 138 to 162.995MHz in 5kHz steps for MARS/CAP operation and weather broadcasts. There's also a simple to use digital **TouchStep Tuning System** for fast shirt-pocket frequency adjustments. An IC-µ2A version is also available without DTMF and PL tones.

All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. #2AT1186-3

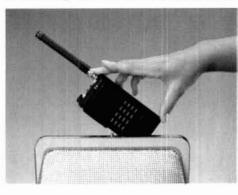Accessories. The Micro utilizes most existing ICOM handheld accessories plus it hosts a new line of battery packs, long life to alkaline battery cases.





ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 Customer Service Hotline (206) 454-7619 3150 Premier Drive, Suite 126, Irving, TX 75063 ICOM CANADA, A Division of ICOM America, Inc., 3071-#5 Road, Unit 9, Richmond, B.C. V6X 2T4 Canada

## Work VHF or HF Packet On Any Computer With Kantronics Complete Packet Communicator KPC-2

From IBM to C-64, or any computer with an asynchronous serial port, you can now work packet on VHF or HF with one TNC, the KPC-2! Extra cost options are unnecessary. KCP-2 is packed full of features and backed by our full-time customer support departments. KPC-2 has totally new hardware and software, Kantronics designed. For more information contact Kantronics or a Kantronics dealer.

Suggested Retail \$ 219.00 \$169

### Features

- AX.25 Version 2.0 software
- Supports multiple connects, up to 26
- RS232 or TTL compatible (C-64 too!)
- HF modem included! (both U.S. and European tones)
- Carrier Detect, and software squelch operation
- FCC Part 15 Certified
- Kantronics industry standard extruded aluminum case
- Power supply and cabling included
- All EPROM software is Kantronics sourced and copyrighted



- 128K EPROM, 16K RAM expandable to 32K, 4K EEPROM.
- Advanced software HDLC routines, eliminating costly out-ofdate chips

## Customer Support

- Extensive dealer network
- In-house programmers/engineers
- In-house service representatives
- Periodic software updates (like 2.0!)

#### Want more information on Packet? Contact us about our new PACKET VIDEO.

\$ 25.00 (shipping included), VHS or BETA format.

RF Data Communications Specialists 1202 E. 23 Street Lawrence, Kansas 66046 (913) 842-7745

# KENWOOD

... pacesetter in Amateur radio

# "DX-cellence!"

TS-940S The new TS-940S is a serious radio

The new TS-940S is a serious radio for the serious operator. Superb interference reduction circuits and high dynamic range receiver combine with superior transmitter design to give you no-nonsense, no compromise performance that gets your signals through! The exclusive multi-function LCD sub display graphically illustrates VBT, SSB slope, and other features.

- 100% duty cycle transmitter. Super efficient cooling system using special air ducting works with the internal heavy-duty power supply to allow continuous transmission at full power output for periods exceeding one hour.
- High stability, dual digital VFOs. An optical encoder and the flywheel VFO knob give the TS-940S a positive tuning "feel."
- Graphic display of operating features.

Exclusive multi-function LCD sub-

display panel shows CW VBT, SSB slope tuning, as well as frequency, time, and AT- 940 antenna tuner status.

- Low distortion transmitter. Kenwood's unique transmitter design delivers top "quality Kenwood" sound.
- Keyboard entry frequency selection. Operating frequencies may be directly entered into the TS-940S without using the VFO knob.
- QRM-fighting features. Remove "rotten QRM" with the SSB slope tuning, CW VBT, notch filter, AF tune, and CW pitch controls.
- · Built-in FM, plus SSB, CW, AM, FSK.
- Semi or full break-in (QSK) CW.
- 40 memory channels. Mode and frequency may be stored in 4 groups of 10 channels each.
- Programmable scanning.
- General coverage receiver. Tunes from 150 kHz to 30 MHz.
- 1 yr. limited warranty. Another Kenwood First!
  - Optional accessories: • AT-940 full range (160-10m) automatic antenna tuner • SP-940 external



Conduct Inter

speaker with audio filtering • YG-455C-1 (500 Hz), YG-455CN-1 (250 Hz), YK-88C-1 (500 Hz) CW filters; YK-88A-1 (6 kHz) AM filter • VS-1 voice synthesizer • SO-1 temperature compensated crystal oscillator • MC-43S UP/DOWN hand mic. • MC-60A, MC-80, MC-85 deluxe base station mics. • PC-1A phone patch • TL- 922A linear amplifier • SM-220 station monitor • BS-8 pan display • SW-200A and SW-2000 SWR and power meters.



Complete service manuals are available for all the Kenwood transceivers and most accessories.

Specifications and prices are subject to change without notice or obligation



More TS-940S information is available from authorized Kenwood dealers.



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

## ham radio magazine

## contents

- 8 a true-frequency digital readout for the HW-101
- 21 2.3-GHz prescaler
- 29 x-band beacons Steve J. Noll, WA6EJO
- 55 ham radio techniques Bill Orr, W6SAI
- microwave and millimeter-wave update
- A. G. Sheffield, VE7CB/W6
- function generator circuits part 2
- 94 open-wire line for 2 meters
- 97 the weekender: aural vco provides relative metering Peter Bertini, K1ZJH
- 101 an i-f sweep generator Bob Griffith, W2ZUC
- 118 advertisers index 110 new products and reader service 4 reflections
  - 27.72 short circuits 6 comments
- 110 DX forecaster
- 114 flea market
- 116 ham mart

- Ed Murdoch, NU4F
- Jerry Hinshaw, N6JH
- 41 top-down filter design J.A. Koehler, VE5FP
- "white noise": technology bites back
- 63 vhf/uhf world Joe Reisert, W1JR
- 74 a deluxe logic probe M, Wilde
- 81 modifying microphones
- 89 practically speaking Joe Carr, K4IPV
- Henry G. Elwell, Jr., N4UH

## **JANUARY 1987**

#### volume 20, number 1

T. H. Tenney, Jr., W1NLB publisher

> Rich Rosen, K2RR editor-in-chief and associate publisher

**Dorothy Rosa, KA1LBO** assistant editor

> Joseph J. Schroeder, W9JUV Alfred Wilson, W6NIF associate editors Susan Shorrock editorial production

#### editorial review board

Peter Bertini, K1ZJH Forrest Gehrke, K2BT Michael Gruchalla, P.E. Bob Lewis, W2EBS Mason Logan, K4MT Vern Riportella, WA2LQQ Ed Wetherhold, W3NQN

publishing staff J. Craig Clark, Jr., N1ACH assistant publisher Rally Dennis, KA1JWF director of advertising sales Dorothy Sargent, KA1ZK advertising production manager Susan Shorrock circulation manager Therese Bourgault circulation cover art: Barbara Smullen

ham radio magazine is published monthly by Communications Technology, Inc. Greenville, New Hampshire 03048-0498 Telephone: 603-878-1441

subscription rates

United States: one year, \$22.95; two years, \$38.95; three years, \$49.95 Canada and other countries (via surface mail): one year, \$3100; two years, \$5500; three years, \$74.00 Europe, Japan, Africa (via Air Forwarding Service): one year, \$37 All subscription orders payable in U.S. funds, via international postal money order or check drawn on U.S. bank

#### international subscription agents: page 114

Microfilm copies are available from University Microfilms, International Ann Arbor, Michigan 48106 Order publication number 3076

Cassette tapes of selected articles from ham radio are available to the blind and physically handicapped from Recorded Periodicals 919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1986 by Communications Technology, Inc. Title registered at U.S. Patent Office

> Second class postage paid Second class postage para at Greenville. New Hampshire 03048-0498 and at additional mailing offices ISSN 0148-5989


Send change of address to ham radio Greenville, New Hampshire 03048-0498







## Amateur Radio's Retiree of The Year

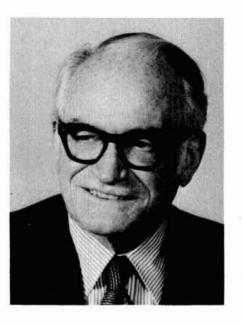

There's a slim, funny book of cartoons making its way around the office these days. Titled, It's Time To Retire When. . .," it makes a case for retiring when . . . you start calling everybody "kids" . . . you hear yourself saying, "We already tried that and it didn't work" . . . more than half your income comes from winning sports pools . . . you tell "war stories" and the "kids" ask, "Which war?"

Now, we don't know much about retirement because the only one of us who's been around long enough to be retired has retired – and *un*retired – three times. But we do know that our readers and authors who claim to be retired seem to be just as busy and involved in the business of living as anybody else. Try getting them to answer the phone on a Tuesday afternoon. Forget it. They're out building something in the shop, tinkering with antennas, volunteering in community service, or traveling. Sometimes they're even starting new businesses or careers, packing two or three or four lifetimes into one.

We expect such will be the case with Barry Goldwater, K7UGA, Amateur Radio's unofficial Retiree of the Year. Moments before the 99th Congress concluded its work, he delivered a characteristically succinct farewell address, bringing his distinguished political career to a close with fewer than 100 words. His equally notable military career had come to an end in 1967, when, with the rank of Major General, he retired from the United States Air Force Reserve.

There aren't enough pages in this or any other magazine to begin to describe what this one man has done for Amateur Radio. Licensed as 6BPI in 1923 — and later, in the early 1960's, after a period of inactivity, as K7UGA — Goldwater has, over the years, been ham radio's indispensable ally on Capitol Hill. Besides working behind the scenes with integrity and finesse, he sponsored much enabling legislation, including that which led to the implementation of the VEC program and the ARRL/FCC Amateur Auxiliary.

During the Vietnam era, Goldwater's station, staffed by volunteers and operating around the clock, ran more than 240,000 phone patches from service personnel in Southeast Asia to families and friends back home. As the war wound down, RTTY replaced phone patches and 150,000 more messages were passed. Though Goldwater's busy schedule left little time for operating, his station manager — Tom Moore, W7FCQ, AFA6PU/AFF6C — told us that whenever the Senator was in town, particularly over the Christmas/New Year's recess, he'd frequently join the volunteers, often taking a full eight-hour shift.

The Senator's equipment, said to put many a broadcaster's station to shame, was based on a four-function Collins 208-U3 transmitter. A Collins 237B rotatable log periodic (6.5 to 30 MHz) with a 64-foot boom (longest element: 81 feet) was mounted on an 80-foot tower atop a hill 200 feet above ground, which was already some 2200 feet ASL. Traffic handling continued until January, 1983, when diminished activity in Southeast Asia allowed the station to be closed.

According to Tom Moore, most of the volunteers at K7UGA were retirees who "just wanted to help out." (Tom had a dual purpose: his son was a POW, and he joined the crew partly in hope of contacting him. Though they never connected through K7UGA, they were eventually reunited. Now retired, Tom still handles traffic from Southeast Asia, with 24,000 "Mom and Dad Morale" messages passed — an average of 500 per month — since the closing of K7UGA.)

Although we can't begin to do justice, in this small space, to Barry Goldwater's contributions to Amateur Radio, there is enough room to say a heartfelt "Thanks" and wish him all the best in his retirement. We'll be watching, with interest and appreciation, to see what he does next.

Dorothy Rosa, KA1LBO Assistant Editor

It's Time To Retire When... is published by Ivory Tower Publishing Co., Inc., Watertown, Massachusetts.

# KENWOOD

... pacesetter in Amateur radio

## **Three Choices for 2m!** TM-2570A/2550A/2530A · Big multi-color LCD and back-lit

Feature-packed 2m FM transceivers

The all-new "25-Series" gives you three RF power choices for 2m FM operation: 70 W, 45 W, and 25 W. Here's what you get:

- Telephone number memory and autodialer (up to 15 seven-digit phone numbers). A Kenwood exclusive!
- High performance GaAs FET front end receiver
- 23 channel memory stores offset, frequency, and subtone. Two pairs may be used for odd split operation
- 16-key DTMF pad with audible monitor
- Extended frequency coverage for MARS and CAP (142-149 MHz; 141-151 MHz modifiable)
- Center-stop tuning—a Kenwood exclusive!



- New 5-way adjustable mounting system
- Automatic repeater offset selection another Kenwood exclusive!
- Direct keyboard frequency entry
- Front panel programmable 38-tone CTCSS encoder includes 97.4 Hz (optional)

controls for excellent visibility

O MI AS MIDE

 The TM-3530A is a 25 watt version covering 220-225 MHz. The first full featured 220 MHz rig!



Introducing ... **Digital Channel Link** 

Compatible with Kenwood's DCS (Digital Code Squelch), the DCL system enables your rig to automatically QSY to an open channel. Now you can automatically switch over to a simplex channel after repeater contact! Here's how it works:

The DCL system searches for an open channel, remembers it, returns to the original frequency and transmits control information to another DCLequipped station that switches both radios to the open channel. Microprocessor control assures fast and reliable operation. The whole process happens in an instant!



#### **Optional Accessories**

- TU-7 38-tone CTCSS encoder
- MU-1 DCL modem unit
- VS-1 voice synthesizer
- PG-2N extra DC cable
- PG-3B DC line noise filter • MB-10 extra mobile bracket
- CD-10 call sign display
- . PS-430 DC power supply for TM-2550A/2530A/3530A
- PS-50 DC power supply for TM-2570A
- MC-60A/MC-80/MC-85 desk mics.
- MC-48B extra DTMF mic. with UP/DWN switch
- MC-43S UP/DWN mic.
- . MC-55 (8-pin) mobile mic. with time-out timer
- SP-40 compact mobile speaker
- SP-50B mobile speaker
- SW-200A/SW-200B SWR/power meters
- SW-100A/SW-100B compact SWR/power meters
- SWT-1 2m antenna tuner

Complete service manuals are available for all Trio-Kenwood transceivers and most accessones Specifications and prices are subject to change without notice or obligation Specifications guaranteed on Amateur bands only

#### Actual size front panel



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220



#### packet board update

#### **Dear HR:**

A number of improvements have been made to the HAPN packet board described in our article, "A Packet Radio TNC for the IBM PC" [August, 1986, page 10]. Readers who have purchased, or plan to purchase, the bare board should be sure to follow the assembly instructions provided on the HAPN-1 diskette (ASSEMBLY.LST) rather than the instructions presented in the article. Otherwise, there's bound to be some confusion regarding the parts list and parts designations. Also, an oscilloscope is no longer required for setting up the board.

> Jack Botner, VE3LNY Hamilton and Area Packet Network

#### SSTV on the C64

#### Dear HR:

Thank you for publishing our article concerning receiving and transmitting SSTV via Commodore 64 without any external interface ["Get on SSTV – With the C64," October, 1986, page 2 43]. It is a great honor for us.

Copies of the complete machine language program, with two pages of instructions, are available on disk or cassette directly from us. Machine code means immediate transmission (the long delay to compose the picture affects only the BASIC version) and easy TX/RX functions; surely readers who have had problems in loading the published listings will be glad to know that.

I have never heard of the references

Jim Grubbs, K9EI, mentioned in his translation of our article. They are not available in Italy. In the future we will try to surprise you with an article including some of the incredible software we are preparing.

On another topic, I was in the hell of Beirut in the Italian Army (United Nations contingent) and I have lots of pictures in my mind which cannot be forgotten. I very vividly remember the day which changed my life, when while patrolling in our tank, we were distracted by some gunfire and drove in the direction from which it came. We realized that a few U.S. Marines whose car was set on fire were defending their lives in a corner of a building. Maneuvering our tank and using it as shield, we succeeded in getting all of the marines into a safe position - or so we thought until seconds after, when I realized that one of them had been shot and was lying on the ground, still under fire. I immediately jumped out of our tank, and together with a brave Marine, among screams and shots, succeeded in getting that poor young man safely inside.

I remember nothing after that, since I had been shot myself and the world became black over me. Hospitals and re-education centers did not make the miracle; meanwhile I have lost my job and problems to the nervous system affect me. So thanks to the computers, I survive for the time being by writing articles and programs for magazines.

From time to time, a question comes to mind: was a medal and some words spoken in a speech by a Prime Minister worth so many problems and pain? Well, no matter — the true recompense is knowing that the life of a man was saved.

The name of the spring which pulled me out of my secure tank was simply altruism and solidarity, qualities common among us Amateur Radio operators. Would I do it again? Certainly, yes — though possibly in a less instinctive way.

> Giuseppe Cameroni, I2CAB Vigevano, Italy

### should VEs issue callsigns?

#### Dear HR:

I propose that the FCC end the waiting period for previously unlicensed applicants (i.e., those who had no prior callsign) who pass VE examinations.

The FCC would issue random blocks of 2x3 callsigns to VECs in unmarked envelopes. The VECs would not be *issuing* the calls (the FCC does that); they would merely be *distributing* the callsigns to successful applicants at each test session, acting on the FCC's behalf just as they're doing when they administer Amateur radio exams.

The expiration date of each call would be ten years after the date of the examination. New Amateurs who didn't like their new calls could simply send in a form 610 and request a callsign change.

As soon as applicants received their callsigns, they could get on the air and enjoy their new privileges immediately. The FCC could still cancel the licenses of any newly-licensed Amateurs found in violation of FCC rules.

The FCC could use their existing sealed-envelope technology for distributing callsigns to the VECs. The VE group would then request a specific number of callsigns for their test session and pass the callsigns out to successful applicants.

Each callsign — known only to the FCC until the envelope is opened would be printed on the license form. The VE would add the successful applicant's name and address and the expiration date of the license, giving one copy to the new licensee and sending another to the FCC for processing.

It's interesting to note that there's no waiting period when you get your driver's license. You get your license and drive off. When you pass an Amatuer Radio exam, you should be able to get your license, go home, and use those new privileges right away.

Conrad Ekstrom, WB1GXM Claremont, New Hampshire 03743

# KENWOOD

... pacesetter in Amateur radio

## Matching Pair PHASE UIL TS-711A/811A VHF/UHF all-mode base stations

The TS-711A 2 meter and the TS-811A 70 centimeter all mode transceivers are the perfect rigs for your VHF and UHF operations. Both rigs feature Kenwood's new Digital Code Squelch (DCS) signaling system. Together, they form the perfect "matching pair" for satellite operation.

- Highly stable dual digital VFOs. The 10 Hz step, dual digital VFOs offer excellent stability through the use of a TCXO (Temperature Compensated Crystal Oscillator).
- Large fluorescent multi-function display.
   Shows frequency, RIT shift, VFO A/B, SPLIT, ALERT, repeater offset, digital code, and memory channel.
- 40 multi-function memories. Stores frequency, mode, repeater offset, and CTCSS tone. Memories are backed up with a built-in lithium battery.



- Versatile scanning functions. Programmable band and memory scan (with channel lock-out). "Center-stop" tuning on FM. An "alert" function lets you listen for activity on your priority channel while listening on another frequency. A Kenwood exclusive!
- RF power output control. Continuously adjustable from 2 to 25 watts.

 Automatic mode selection. You may select the mode manually using the front panel mode keys. Manual mode selection is verified in International Morse Code.

Digital QSC

- · All-mode squelch.
- · High performance noise blanker,
- Speech processor.
   For maximum efficiency on SSB and FM.
- IF shift.
- "Quick-Step" tuning.
   Vary the tuning characteristics from "conventional VFO feel" to a stepping action.
- Built-in AC power supply. Operation on 12 volts DC is also possible.
- · Semi break-in CW, with side tone.
- VS-1 voice synthesizer (optional)
  - More TS-711A/811A information is available from authorized Kenwood dealers.



- IF-10A computer interface
- IF-10A computer interface
   IF-232C level translator
- CD-10 call sign display
- SP-430 external speaker
- VS-1 voice synthesizer
- TU-5 CTCSS tone unit
- MB-430 mobile mount
- MC-60A, MC-80, MC-85
- deluxe desk top microphones
- MC-48B 16-key DTMF, MC-43S UP/ DOWN mobile hand microphones
- SW-200A/B SWR/power meters: SW-200A 1.8-150 MHz
   SW-200B 140-450 MHz
   SWT-1 2-m antenna tuner
- SWT-1 2-m antenna tuner
   SWT-2 70-cm antenna tuner
- SW1-2 70-cm antenna tun
   DC power cable
- PG-2U DC power cable

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

## KENWOOD

TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

## a true-frequency digital readout for the HW-101

# for more precise tuning

If you've ever operated an HW-101, you know how frustrating it can be to try to tune it to a specific frequency; the main tuning dial simply isn't precise enough. In an effort to solve the problem, I decided to add a digital readout to my rig.

I didn't really want to *build* one; I just wanted to find an old SB-650 Digital Frequency Display, the Heathkit readout designed to accompany its HW- and SB- series equipment. But I couldn't find one for sale locally, and Heath had long ago sold out its final inventory. I decided to go ahead on my own. I tried to get a copy of the SB-650 manual, but Heath had no more.

Why this seeming obsession with the SB-650? In order to develop a reading from an HW-101, all three transceiver oscillators must be sampled and multiplexed into the counter section in proper sequence. The counting circuitry itself is more or less standard, but the multiplexing circuit is the key to success. I knew that Heath's circuit worked, and the gating and logic tables I came up with looked too unwieldy to be correct.



Photo A. The top, bottom, and digit boards (left to right), are shown interconnected and ready for mounting.

Although Heath couldn't provide a manual, the company did supply several schematics of the multiplexing and time chain circuitry. The multiplexing used in my readout more or less duplicates the Heath circuit.

#### theory of operation


A transceiver digital readout is basically a frequency counter preceded by processing circuits that allow proper sampling of the circuits in the transceiver that determine the final operating frequency. In the HW-101 the operating frequency is determined by heterodyne action among three oscillators. The heterodyne oscillator is a high-frequency oscillator, while the carrier and VFO oscillators are relatively low in frequency. Both the carrier and VFO frequencies are essentially subtracted from the higher-frequency heterodyne oscillator frequency to establish the operating frequency. The processing circuitry of the readout first enters the highest frequency into the counters, then subtracts, one at a time, the other two oscillator frequencies from it. The true operating frequency is then presented to the digital display through the latches. (Although the "addition" and "subtraction" mixing takes place in different stages of the transceiver for Transmit than for Receive, the same oscillators ultimately perform the same job. Thus by tapping the oscillator outputs, the readout is accurate to within 100 Hz  $\pm$  clock error, and reads the same frequency in either send or receive mode.)

#### system flow


In the transceiver, samples of the three oscillators are connected by coax to phono jacks added to the back of the transceiver chassis. These are connected by 36-inch phono cables to three input phono jacks on the back of the readout chassis. (See **fig. 1** for transceiver sampling hookups.)

Each jack connects to an input stage consisting of a 40673 MOSFET preamp and a 2SC945 (or 276-2016) pulse-shaper circuit. After passing through buffer gates in U1 and being divided by four in frequency in flip-flop

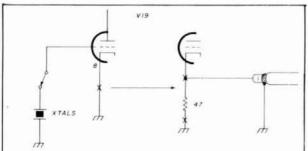
By Ed Murdoch, NU4F, Route 1, Box 238, Omega, Georgia 31775



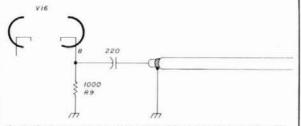Heterodyne Oscillator: bandpass board, Tube V19, Pin 8 (cathode). This cathode is normally grounded. Break foil at X, solder 470 watt resistor across break. Connect center of coax to tube pin side, shield to adjacent foil ground. Coax goes to phono jack on rear of chassis.



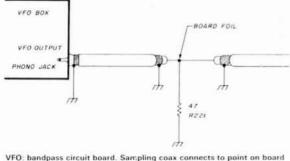Carrier Oscillator: modulator board, Tube V16, pin 8 (cathodes). This point also connects to other cathode of V16. These are already above ground with appropriate RF voltage. Coax is coupled to pin 8 foil through 220 pF capacitor.



VFO: bandpass circuit board. Sampling coax connects to point on board where output coax of tube V20 connects. Connect coax center conductor to the foil point adjacent to high side of R221 (47 ohms).

fig. 1. Transceiver sampling connections (all connections made to underside of board). Each length of coax goes to a phono jack installed on the back of the transceiver chassis. Regular 36-inch shielded phono cables connect to digital readout.

U2, these three circuits are gated sequentially into the Least Significant Digit (LSD) counter, U17, by multiplexer chips U3, U4, and U13 through U15. The gating pulses for *enable* and *inhibit* are developed from the timing chain combination of oscillator-buffer-feedback gates U5, divide-by-four flip-flop U6, and time-division decade counters U7 through U12. The reset pulses for pulse counters U17 through U22 come from U15, pin 3. The reset pulses for divide-by-four flip-flop U2 come from U16, pin 6. The transfer pulses for the latches come from U16, pin 3.

In order to feed the correct oscillator signal to the counters at the proper time, a time frame of four intervals is established. This is done by gating several combinations of outputs from U10, U11, and U12 in the timing chain. These in turn are interlocked by other gates to allow each oscillator to be counted once per frame and

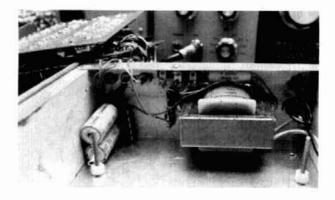


Photo B. Power supply components are mounted on rear chassis wall.

shifted to the up count (add) or the down count (subtract), as is appropriate. The fourth interval is used for pulse development by the RC network connected between U13, pin8 and ground. After both reset pulses and the transfer pulse have been established, the next clock pulse starts the cycle again.


The counting section, which consists of a cascaded series of six 74LS192 up/down decade counters (with one counter for each display digit), provides a frequency divided-by-ten output to the following counter and its parallel output to its own digit decoder in binary-coded decimal (1-2-4-8, also referred to as ABCD in the accompanying figures). Therefore each counter has what it needs to produce the correct reading for its own LED digit, which it feeds to the digit by way of a 74LS75 latch. The divided-by-ten output is then passed on to the next counter chip, which acts in a similar fashion.


Each storage latch holds the previously transmitted number until the transfer pulse occurs, causing the latches to accept the newest measurement offered by their respective counter's ABCD outputs. Each of these "updates" is caused by a combination of reset pulses to the various flip-flops and counters so that each new count is synchronized. The latches feed the ABCD data to the input lines of their respective 74LS47 BCD to seven-segment decoder/drivers, which decode the ABCD numbers and provide the drive for the correct segments of the seven-segment display digit.

Overall synchronization is established by a master clock oscillator from which the various pulses, time intervals, and switching sequences are derived. The time occurrence of the individual gating pulses is also determined by frequency division (by divide-by-four flip-flops 74LS73, and by divide-by-ten and divide-by-two counters 74LS90). The clock frequency of 1 MHz was chosen to make frequency-division factors easily obtainable.
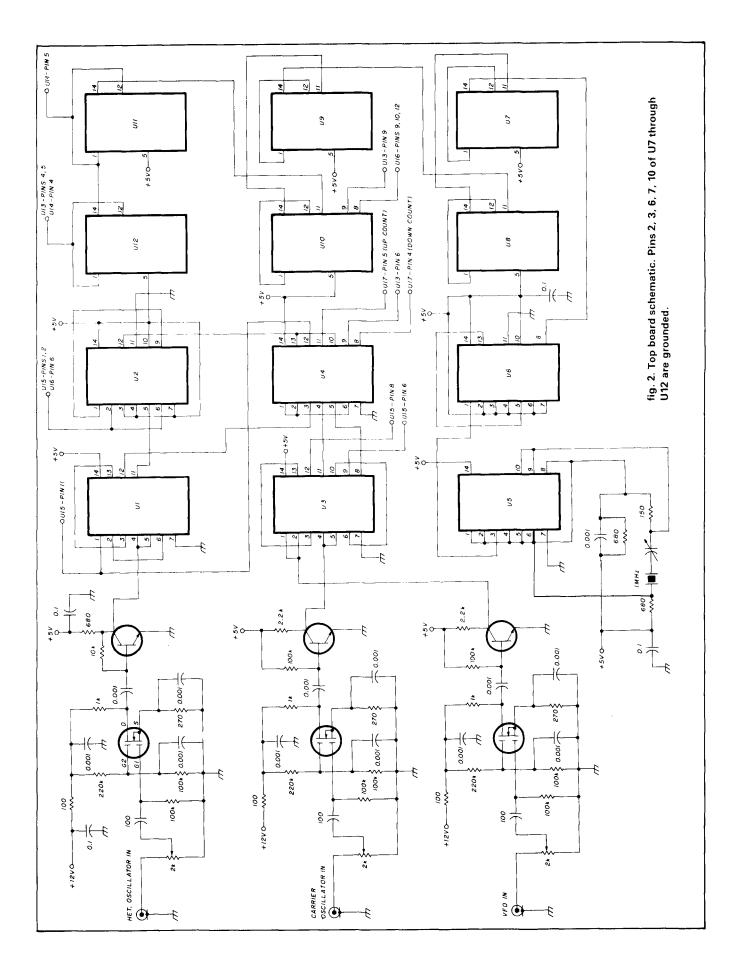
#### construction

The circuits were planned on quad paper and then built up on two  $41/2 \times 65/8$ -inch circuit boards and one  $23/4 \times 33/4$ -inch board (**Photo A**). The two large



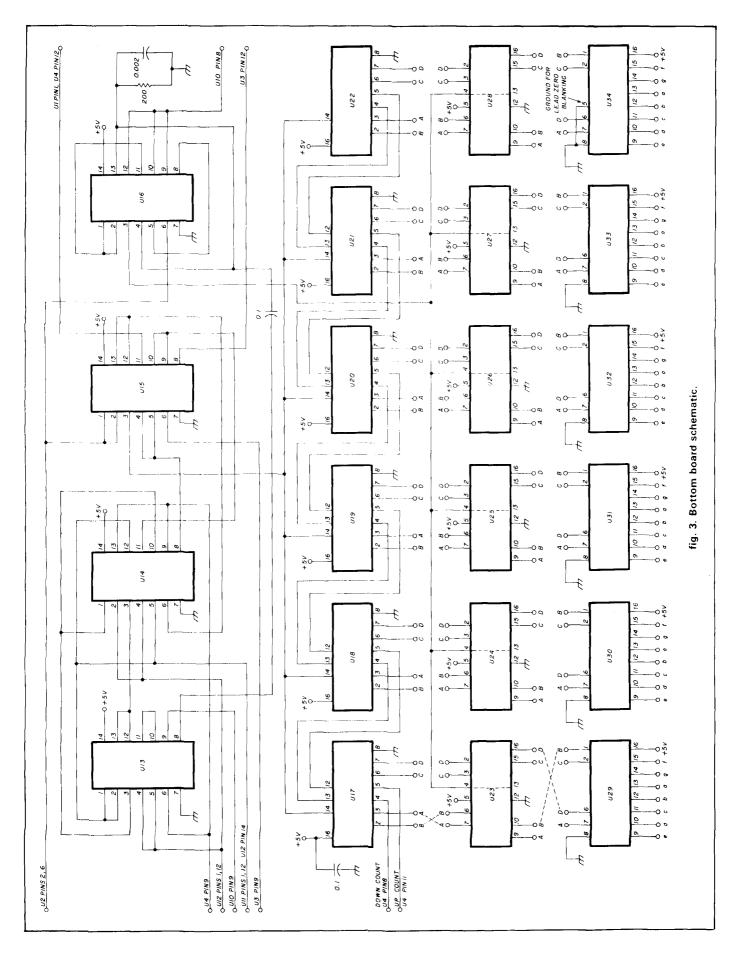

### Table 1. Parts list. Cost of project should be approximately \$85.00.

40673 MOSFETs	MHz Electronics*
2SC945 Transistor	Radio Shack 276-2051 or
	276-2016
	or MPS 3904
U1,U3,U4,U5	74LS00 QuadNand Gates**
U2,U6	74LS73 Dual J-K flip-flops**
U7-U12	74LS90 Decade (bi-quinary)
	counters**
U17-U22	74LS192 up/down decade
	counterst
U23-U28	74LS75 Quad latch**
U29-U34	74LS47 BCD/seven-segment
	decoder/driver**
0.3-inch seven-segment	Radio Shack 276-053 (common
digit display	anode)
Chassis	No. EDCH-2881
Top and bottom boards	Radio Shack 276-147

\*MHz Electronics, 2111 West Camelback Road, Phoenix, Arizona 85015.
\*\*DoKay Electronics, 2100 De La Cruz Boulevard, Santa Clara, California 95050.

tAll Electronics, P.O. Box 20406, Los Angeles, California 90006.

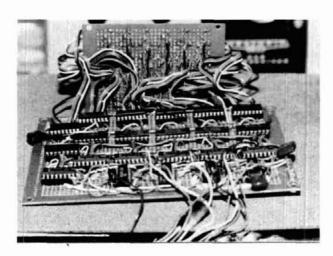


Photo D. A closer view of the bottom and digit boards illustrates interconnections.

boards are mounted upside-down in the chassis and separated by spacers. The top board contains the input wave shaping circuits, the timing chain, and part of the multiplex circuitry. The bottom board contains the remainder of the multiplex circuitry, the counters, latches, and decoder/drivers. The outputs of the decoder/drivers are cabled to their respective segment dropping resistors mounted on the third board, which also holds the digits. This board is at right angles to the other boards. A window is cut in the chassis front to accommodate the digits.

The power supply parts are mounted on the rear wall of the chassis. So are the three input jacks. Prototype

wiring is shown in **Photo B**; the input wiring was later changed to coax.

#### building the chassis

The first step is to determine the location of each part. Next, mark off and drill the mounting holes for the input phono jacks, the fuse holder, and front panel switch. Then drill the transformer and heat-sink-regulator mounting holes, tie-point holes, and holes in the chassis top for the circuit board bolts.

With an awl, mark guidelines for cutting the digit window. Drill holes in diagonally opposite corners of the outline to accommodate the sabre saw blade and cut the rough opening. This is a tricky and possibly dangerous step, so I'd suggest you secure the chasiss firmly in a vise while you make the cut. Stay slightly to the inside of the guidelines; use a small, flat file to smooth the edge of the opening to its finished size. For the window its self, I cut a piece of clear plastic (box covers are ideal) and glued it into place.

Photo A also shows the approximate board locations of all parts and wiring paths for the multiplexer interconnections. Other wiring shown in the remaining figures according to normal schematic drafting practice.

#### the power supply

The power supply (**fig. 5**) is typical of so-called "economy" supplies in that a single secondary winding is used to develop two voltage levels. (The MOSFETs need 12 volts; the rest uses 5 volts. Both are regulated.) The transformer supplies 18 volts ac through a bridge rectifier to the filter for the 12-volt section, regulated by a 12-volt Zener diode; a center tap provides 9 volts ac to the filter of the 7805 5-volt regulator.

The power supply components, installed on the back of the chassis, are partially supported by tie points. The 7805 regulator is mounted on a standard T-220 type heat sink positioned directly against the chassis for improved heat removal. With the circuit boards in place, it's a pretty close fit; I blew out a bridge rectifier and the fuse by not watching a test probe closely enough while making tests. I have now covered exposed terminals with a tape wrap.

#### circuit boards

The digit display board (**fig. 4** and **Photo C**) contains the six LED digits, sockets, and 42 1/2-watt 330-ohm dropping resistors — one resistor per digit segment. This board should be wired first. Note that this is the only place wire-wrap sockets are used. This is because I planned to support the digit board against the chassis front by its cable pressure and put several turns on each pin for extra stability. I made a seven-wire color-coded combination for each digit: a four-wire section plus a three-wire section.

After making all cable solder connections, cut off all

# FLACESSOR

#### 300 WATT ANTENNA TUNER HAS SWR/WATTMETER, ANTENNA SWITCH, BALUN. MATCHES VIRTUALLY EVERYTHING FROM 1.8 TO 30 MHz.



\$99.95 MFJ-941D

## RTTY/ASCII/CW COMPUTER INTERFACE



Free MFJ RTTY/ASCII/CW software on tape and cable for VIC-20 or C-64. Send and receive computerized RTTY/ASCII/CW with nearly any personal computer (VIC-20, Apple, TRS-80C, Atari, TI-99, Commodore 64, etc.). Use Kantronics or most other RTTY/CW software. Copies both mark and space, any shift (including 170, 425, 850 Hz) and any speed (5-100 WPM RTTY/CW, 300 baud ASCII). Sharp 8 pole active filter for CW and 170 Hz shift. Sends 170, 850 Hz shift. Normal/reverse switch eliminates retuning. Automatic noise limiter. Kantronics compatible socket plus exclusive general purpose socket. 8x11/4x6 in. 12-15 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.

## RX NOISE BRIDGE

#### Maximize your antenna performance!

\$59.95 MFJ-202B

Tells whether to shorten or lengthen antenna for minimum SWR. Measure resonant frequency, radiation resistance and reactance.

New Features: individually calibrated resistance scale, expanded capacitance range (±150 pf). Built-in range extender for measurements beyond scale readings. 1-100 MHz. Comprehensive" manual. Use 9 V battery. 2x4x4 in.

INDOOR TUNED ACTIVE NEW! IMPROVED! ANTENNA with higher gain "World Grabber" rivals

or exceeds reception of outside long wires! Unique tuned Active

Antenna minimizes intermode, improves selectivity, reduces noise outside tuned band, even functions as preselector with external antennas.

Covers 0.3-30 MHz. Tele scoping antenna. Tune, Band, Gain, On-off bypass controls. 6x2x6 in. Uses 9V battery, 9-18 VDC or 110 VAC with



ORDER ANY PRODUCT FROM MFJ AND TRY IT-NO **OBLIGATION. IF NOT DELIGHTED, RETURN WITH-**IN 30 DAYS FOR PROMPT REFUND (LESS SHIPPING). · One year unconditional guarantee · Made in USA. · Add \$4.00 each shipping/handling · Call or write for free catalog, over 100 products.

NEW FEATURES

#### POLICE/FIRE/WEATHER **2 M HANDHELD CONVERTER**

Turn your synthesized scanning \$39.95 2 meter handheld into a hot Police/ MFJ Fire/Weather band scanner! L-313

144-148 MHz handhelds receive Police/Fire on 154-158 MHz with direct frequency readout. Hear NOAA maritime coastal plus more on 160-164 MHz. Converter mounts between handheld and rubber ducky. Feedthru allows simultaneous scanning of both 2 meters and Police/Fire bands. No missed calls. Crystal controlled. Bypass/Off

switch allows transmitting (up to 5 watts). Use AAA battery, 21/x11/2 in BNC connectors.

#### MFJ/BENCHER KEYER COMBO MFJ-422 \$109.95

The best of all CW worlds-



a deluxe MFJ Keyer in a compact configuration that fits right on the Bencher lambic paddle! MFJ Keyer - small in size, big in features. Curtis 8044-B IC, adjustable weight and tone, front panel volume and speed controls (8-50 WPM). Builtin dot-dash memories. Speaker, sidetone, and push button selection of semi-automatic/tune or automatic modes. Solid state keying. Bencher paddle is fully adjustable; heavy steel base with non-skid feet. Uses 9 V battery or 110 VAC with optional adapter, MFJ-1305, \$9.95

### VHF SWR/WATTMETER

Low cost VHF SWR/

Wattmeter! Read SWR (14 to 170 MHz) and forward/



reflected power at 2 meters. Has 30 and 300 watts scales. Also read relative field strength. 4x2x3 in.



MFJ ENTERPRISES, INC. Box 494, Mississippi State, MS 39762

#### MFJ's fastest selling tuner packs in plenty of new features!

· New Styling! Brushed aluminum front. All metal cabinet. · New SWR/Wattmeter! More accurate. Switch selectable 300/30 watt ranges. Read forward/reflected power

· New Antenna Switch! Front panel mounted. Select 2 coax lines, direct or through tuner, random wire/balanced line or tuner bypass for dummy load.

· New airwound inductor! Larger more efficient 12 position airwound inductor gives lower losses and more watts out. Run up to 300 watts RF power output. Matches everything from 1.8 to 30 MHz: dipoles, inverted vee, random wires, verticals, mobile whips, beams, balanced and coax lines. Built-in 4:1 balun for balanced lines. 1000V capacitor spacing. Black. 11x3x7 inches. Works with all solid state or tube rigs. Easy to use, anywhere.

### **1 KW DUMMY LOAD**

Tune up fast, extend life of finals, reduce **ORM!** Rated 1KW CW or 2KW PEP for 10 minutes. Half rating for 20 minutes, continuous at 200 W CW, 400 W PEP VSWR under 1.2 to 30 MHz, 1.5 to 300 MHz. Oil contains no PCB.



50 ohm non-inductive resistor. Safety vent. Carrying handle. 71/2x63/4 in.

24/12 HOUR CLOCK/ ID TIMER

\$19.95 NEW Switch to 24 hour UTC or 12 hour format! Battery backup

**MFJ-106** 



maintains time during power outage. ID timer alerts every 9 minutes after reset. Red LED .6 inch digits. Synchronizable with WWV. Alarm with snooze function. Minute set, hour set switches. Time set switch prevents mis-setting. Power out. alarm on indicators. Gray and black cabinet, 5x2x 3 inches. 110 VAC, 60 Hz.

UAL TUNABLE SSB/CW/RTTY FILTER MFJ-7528 \$99.95



Dual filters give unmatched performance! The primary filter lets you peak notch low pass or high pass with extra steep skirts Auxiliary filter gives 70 db notch 40 Hz pea-Both filters tune from 300 to 3000 Hz with variable bandwidth from 40 Hz to hear v flat Constant output as bandwidth is varied linear frequency control. Switchable holse imiter for impulse noise. Simulated stered sound for CW lets ears and mind reject GRM inputs for 2 rigs Plugs into phone jack Two watts for speaker Off bypasses filter 9-18 VDD or tho warts Off bypasses filter 9-18 VC LAC A IN optional adapter MF2+312 \$9.95 r 107



the pins except the 5-volt supply pins to about 1/4 inch, leave these longer (about 1/2 inch) so that the 5-volt bus can be run straight across.

There are no grounds on the digit board. Each segment "grounds" through its driver connection when activated; these are common anode devices.

The two decimal point positions are grounded through 330-ohm resistors over to the front ground bus on the bottom board. These decimal points divide the six digits into MHz and KHz separations.

#### the bottom board

The bottom board contains multiplexer chips U13 through U16, decade counters U17 through U22, latches "U23-U28, and decoder/driver chips U29 through U34, plus sockets (**Photo D**).

You'll have to offset three chips to fit all the parts on the board, but this poses no problem. In fact, it actually helps; because the column of offset chips represents the most-significant-digit position, you'll have a handy reference point to which you can refer as you add parts to the board.

Photo E shows the location of the two ground buses,


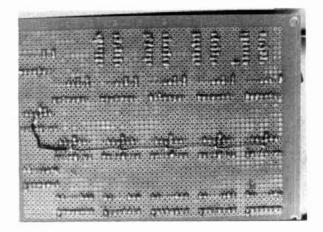


Photo E. Rear view of bottom board shows closeness of solder points and bus for latches that transfer pulse feed.

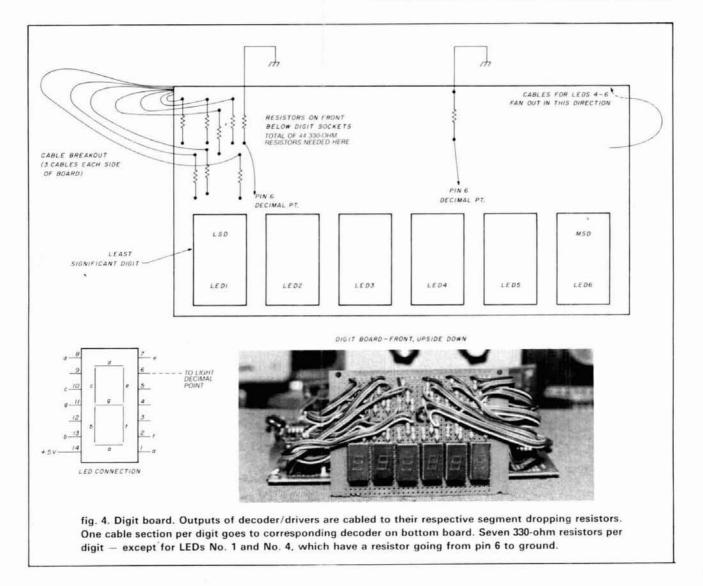

## When we set out to make the best amateur radio equipment in the world, we had some pretty tough standards to live up to ...



So we designed the **RC-850 Repeater Controller**, the industry's top of the line repeater control system. Now in it's "third wave" of innovation, thanks to its designed for the future architecture and new software releases. The '850 defines the industry standard in repeater control systems.

- Fully remotely programmable with Touch-Tone commands.
- Front panel LED display
- Over 300 word customized male and female speech synthesis vocabulary
- Time/day of week Scheduler with 10 set-up states, 30 changeovers and events, over 100 scheduled items for hands off operation and automatic reminders.
- Full or half duplex autopatch, autodial (250 numbers), emergency autodial, reverse autopatch, antidialer, toll restrict including telephone exchange tables, supports remote and multiple phone lines
- Informative remotely programmable ID's (17), tail messages (13), bulletin boards (5)
- 16 channel voice response analog metering, automatic storage of min/max values on each channel, values may be read back on command or may be included in any programmable messages
- Supports synthesized remote base transceivers and full duplex links
- Individual user access codes to selectable features
- Mailbox for user-to-user, and system-to-user messages
- Paging two-tone, 5/6 tone, DTMF, CTCSS, HSC display, user commandable and may be included in programmable messages (i.e. alarms)
- Easy hookup to any repeater


Our new Digital Voice Recorder lets you remotely record ID's, tail messages, and various other response messages for automatic playback through your repeater. Audio is stored digitally with no-compromise reproduction quality in up to eight megabits of memory. The DVR can support up to three independent repeaters for a low per-channel cost. Its Touch-Tone activated voice mailbox lets your users easily record messages for other users when they aren't around.

#### QST: Attention All Hams If you own a shack, you should know about ShackMaster\*

ShackMaster lets you carry your home station with you in the palm of your hand. It acts as your gateway to the world, linking your handheld transceiver to your high performance HF station. Now, instead of your valuable home equipment being available to you 1% of the time, it's available 99% of the time! Whether around the house, in the yard, or across town, ShackMaster let's you take it with you.

But that's just part of ShackMaster's story. It lets you communicate with the family by handling third party traffic – its electronic mailbox and intercom let you keep in touch. And a simplex patch lets you place important calls directly through your home phone.

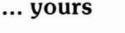Crossband linking – VHF/UHF to HF Telephone access to your home station BSR Home Control interface Electronic Mailbox ShackPatch<sup>®</sup> intercom into the shack PersonalPatch<sup>®</sup> simplex autopatch



### ... and ours.

If your repeater budget can't afford the '850, we offer the **RC-85 Repeater Controller**, which we like to call the "second best repeater controller in the world". It's a scaled down, simplified version of our '850, but overall, it offers more capability and higher quality than anyone elses control equipment at any price.

- Remotely programmable with Touch-Tone commands
- Over 175 word customized male speech synthesis vocabulary
- Selectable "Macro sets" for easy control operator selection
- Autopatch, autodial (200) numbers, emergency autodial, reverse patch
- Remotely programmable informative ID's (7), tail messages (3), bulletin board (2)
- Supports synthesized remote base transceiver, control receiver, alarm
- Selectable, informative courtesy tones
- Talking S-meter, Two-tone paging
- Easy hookup to any repeater

For those who like to "roll their own", we can get you off to a rolling start with our **ITC-32 Intelligent Touch-Tone Control Board**. Much more than just a decoder, it's a mini-control system of its own, with the basic repeater and remote base functions built-in. And it can be tailored by you with its Personality Prom.

- 28 remotely controllable latched or pulsed logic outputs
- 4 alarm or remote sensed logic inputs
- Response messages to confirm command entry
- Repeater functions including COR, IDer, timers, courtesy tone, etc.
- Remote base functions including control of synthesized transceiver
- Remotely recordable, variable length audio tracks, accessed from controller messages
- Top quality, no compromise audio reproduction
- Supports up to three repeaters for cost effective installation
- Expandable to roughly 6 minutes of speech in 8 megabits of memory
- Easy interface to RC-850, RC-85 controllers, or to any stand-alone repeater

All our products are documented with high quality, easy to read manuals. Our goal is to advance the state of the repeater art. But most of all, our products put the FUN back into the FUN MODE!



To order one of these advanced control products, call 408-727-3330. Technical manuals are available for purchase and the amount paid is applied as a deposit on the equipment. For specifications and a copy of our ACC Notes newsletter, just write or send in your QSL card to



Visa and Mastercard accepted.

108

2356 Walsh Avenue 

Santa Clara, CA 95051

(408) 727-3330

## Under New Ownership

The **BEST** is still

'made in U.S.A."

## American made RF Amplifiers and Watt/SWR Meters of exceptional value and performance.

•5 year warranty • prompt U.S. service and assistance

#### **RF AMPLIFIERS**

MILLION DEL

#### **2 METERS-ALL MODE**

B23 2W in = 30W out (useable in: 100 mW-5W)

B108 10W in = 80W out (1W=15W, 2W=30W) RX preamp B1016 10W in = 160W out

(1W=35W, 2W=90W) RX preamp B3016 30W in = 160W out (useable in: 15-45W) RX preamp (10W = 100W)

#### **220 MHz ALL MODE**

C106 10W in = 60W out (1W=15W, 2W=30W) RX preamp

C1012 10W in = 120W out (2W=45W, 5W=90W) RX preamp

C22 2W in = 20W out (useable in: 200mW-5W)

**RC-1 AMPLIFIER** REMOTE CONTROL Duplicates all switches, 18' cable

#### WATT/SWR METERS

 peak or average reading direct SWR reading MP-1 (HF) 1.8-30 MHz MP-2 (VHF) 50-200 MHz

430-450 MHz ALL MODE

D24 2W in = 40W out (1W = 25W)


D1010 10W in = 100W out (1W = 25W, 2W = 50W)

Available at local dealers throughout the world.

- 109



16890 Church St., Morgan Hill, CA 95037, (408) 779-7363

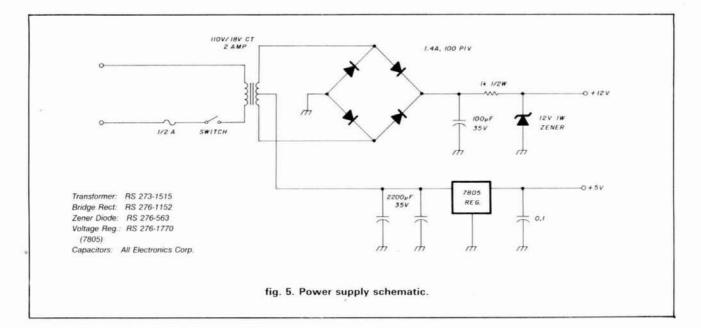

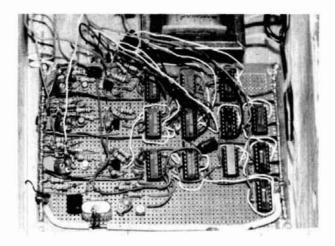


Photo F. Clock oscillator has prominent location in lower left corner of top board view.

made from No. 12 wire and secured by lugs to the board mounting bolts. (While not an ideal ground, it works.) The photo also illustrates the closeness of the solder points on the pins. This was the part of the whole project that most concerned me. I tried to cut each wire so that after inserting it through the top of the board there would be just the right amount of bare wire left to bend over flat against the pin and spin around with a wiring tool so that no further wire cutting would be necessary. I'd crimp it slightly with my long-nose pliers to assure a tight fit and then solder very carefully. In the counter section of the board I soldered corresponding wires or corresponding cabled ABCD data runs. Then I verified both continuity and the absence of adjacent pin shorts before continuing. This approach paid off. I found two adjacent pin shorts and one cold solder joint that I fixed immediately, saving years of anguish. As I went along I also

aligned any bent pins.

In this same photo you can see a bus running under the center line of the latch sockets. This bus carries the transfer pulse to pins 4 and 13 of each latch, which are connected together on the bottom of the board (shown by dotted lines in **fig. X**). There simply wasn't room for this run on the top side.

Because the local Radio Shack was out of small 0.1-pF tantalum capacitors, I used their larger, standard PC-type for transient bypass and fitted them as best I could.

Most of the wiring of the multiplexer chips — on both bottom board and top board — is in the form of interconnection of gates in the same chip or in other multiplexer chips. On the bottom board I started at pin 1 on the top left side of chip U13 and went numerically pin-by-pin, finishing out each chip before going to the next. I made a color-coded tabulation of the off-board wires, leaving these about six inches long for later connection to the top board.

#### top board

The top board (**fig. 2** and **Photo F**) contains the input preamp/pulse-shaper circuits, the clock oscillator U5, and associated time-division chips U6 through U12, as well as multiplexer chips U1 through U4.

Friends, I didn't know how many of life's simple pleasures I'd missed until I started working on the top board. As with the other board, I determined the layout on a board-size piece of quad paper. In an attempt to keep the input wires short, I crowded the preamp stages. Besides giving the whole thing the look of last year's campfire, it began to look as if I might have an interstage coupling problem on my hands. Actually, the only place such coupling ever did occur was between the wires from the input jacks. After I no longer had to remove the top board for anything, I changed these to coax. I installed the 40673 preamp and 2SC945 pulse shaper circuits first, using 1/8-watt trim pots as the input impedance for each preamp, but I just tacked on the wires from the input jacks. I expected to have to experiment with the resistance to get it in the right range for the input circuits. (The samples from the transceiver have to develop a voltage across a load at their respective input stages to apply to the MOSFET gate inputs. There is a limit as to the amount of current flow through this load. The optimum resistance worked out to be about 2 k (which is the input impedance listed on the spec sheet for the SB-650).

Radio Shack couldn't help with 2-k pots, so I replaced the original 1-k units with 5-k, 1/2-watt trim pots, paralleled with a 3.3-k resistor under the board. This arrangement works perfectly. (**Figure 4** shows only a 2-k variable resistance.)

Though the 40673 **MOSFET** circuit is similar to that used in the SB-650, I first saw it in an article in *QST*.<sup>1</sup> The crystal clock oscillator design was also taken from this article.

The components of the 2SC945 pulse-shaping circuits were determined by experiment because I couldn't find any characteristics curves to determine the proper parameters for saturation.

Rather than worry about socket contact resistance and corrosion, I direct-wired the transistors. To minimize the danger of static blowout of the MOSFETs, I borrowed a dc-operated isolation-type iron from Bobby Hobby, KA4DPF, the friend who took the photo for this article.

Next I wired the clock oscillator, which was almost a vacation by comparison. I then mounted all the sockets for the IC chips. I wired miltiplexer chips U1 through U4 and the oscillator chip, U5, first. I followed the same wiring scheme on this multiplexer section as on the bottom board (starting at pin 1, upper left, etc.).

Then I wired time-division chips U6 through U12. Except for the divide-by-four flip-flop U6, the wiring almost duplicates itself from chip to chip. Chips U7 through U12 require that pins 2, 3, 6, 7, and 10 all be grounded. To prevent chaos, I first connected these pins on each chip together on the underside of the board, then connected them to a ground bus. I had to use a little spaghetti here and there to avoid other pins.

#### final assembly

Connecting the digit board to the bottom board is the first step in the final assembly.

**Figure 4** shows a section of seven-conductor cable going to each digit resistor area. The cable is split into two sections each to allow for more flexibility in positioning the board against the window. Using the color coding of the various wires, I tabulated a wiring plan that made it quick and easy to connect the cable ends to the proper pins on the decoder/driver sockets. When I first planned this arrangement I was concerned that the digit board might not be secure enough without direct mounting on the chassis. Not to worry — you couldn't knock it loose with a baseball bat. Finally I connected those almost-forgotten off-board wires from the bottom board to their top-board destinations.

The main boards are mounted on four 11/2-inch, 6/32 bolts protruding downward from the top of the chassis (viewed in normal operating position). A 3/8-inch nylon spacer on each bolt separates the chassis from the bottom board, which is secured with washers and nuts. (The ground lead from the 2200  $\mu$ F filter combination connects to a lug at the nearest bolt.) Three-quarter-inch aluminum spacers on the bolts support the top board, which is secured by nuts. Lugs carrying the top board ground buses go under these nuts.

#### adjustments and calibration

Proper sampling levels are adjusted by placing the transceiver on the 29.5-MHz band, in the receive mode, and adjusting the three input trim pots to just slightly more than the level needed to cause a 29.5<sup>s</sup> MHz reading to lock on the display.

First I adjusted the 1-MHz clock oscillator trimmer to zero beat with WWV, using a portable receiver loosely coupled to the oscillator gate section by an insulated wire wrapped around the receiver's telescope antenna. Even with the economy-type trimmer the frequency stays within a few Hz after several hours of warmup, varying no more than about 100 Hz after 24 hours of continuous operation.

With the trim pots set at minimum, I switched the transceiver to the 29-MHz range; the heterodyne oscillator is at its highest frequency here, and losses through the sampling circuitry are greatest. (In other words, if it works here it should work anywhere.) At this point the display read all zeros, as was appropriate. Then I advanced the heterodyne oscillator trim pot until a firm reading in the region of 38 MHz was showing (this is the frequency of the heterodyne oscillator crystal on this band).

Then I adjusted the carrier oscillator trim pot for a marked drop in frequency reading, to about 34 + MHz; I adjusted the VFO trim pot for a further drop to 29 + MHz. I advanced each trim pot slightly and closed up the chassis.

Naturally the first thing I did was to tune down to 7335.0 USB. As I brought up the audio gain, I heard, with perfect clarity, "This is CHU, Canada. The time is . . . " - one of the sweetest sounds I have ever heard.

This readout can be adapted to some other rigs. By using the heterodyne oscillator input only, it can be used for low-voltage level frequency counting, with 100-Hz resolution.

If you have any questions, write (please enclose SASE) and I'll try to help.

#### reference

1. Philip S. Rand, W1DBM, "The BEEPER: An Audible Frequency Readout for the Blind Amateur," *QST*, September, 1983, page 19.

ham radio



P.C. ELECTRONICS 2522 S. PAXSON LN. ARCADIA CA 91006 (818) 447-4565 TOM W6ORG MARYANN WB6YSS Compuserve 72405,1207





#### ATV MADE EASY WITH OUR SMALL ALL IN ONE BOX TC70-1 TRANSCEIVER AT A SUPER LOW \$299 DELIVERED PRICE! CALL 1-818-4474565 AND YOURS WILL BE ON ITS WAY IN 24 HRS (VIA UPS SURFACE IN CONT. USA).

#### TC70-1 FEATURES:

- \* Sensitive UHF GaAsfet tuneable downconverter for receiving
- \* Two frequency 1 watt p.e.p. transmitter. 1 crystal included
- \* Crystal locked 4.5 mHz broadcast standard sound subcarrier
- \* 10 pin VHS color camera and RCA phono jack video inputs
- \* PTL (push to look) T/R switching
- \* Transmit video monitor outputs to camera and phono jack
- \* Small attractive shielded cabinet 7 x 7 x 2.5"
- \* Requires 13.8vdc @ 500 ma. + color camera current

Just plug in your camera or VCR composite video and audio, 70cm antenna, 12 to 14 vdc, and you are ready to transmit live action color or black and white pictures and sound to other amateurs. Sensitive downconverter tunes whole 420-450 mHz band down to channel 3. Specify 439.25, 434.0, or 426.25 mHz transmit frequency. Extra transmit crystal add \$15.

Transmitting equipment sold only to licensed radio amateurs verified in the Callbook. If recently licensed or upgraded, send copy of license.


#### WHAT ELSE DOES IT TAKE TO GET ON ATV?

Any Tech class or higher amateur can get on ATV. If you are now on SSTV, or have a home camera or VCR & TV set, your cost will just be the TC70 and antenna system. If you are working the AMSAT satellites you can use the same 70cm antennas on ATV.

DX with TC70-1s and KLM 440-27 antennas line of sight and snow free is about 22 miles, 7 miles with the 440-6 normally used for portable uses like parades, races, search & rescue, damage accessment, etc. Add one of the two ATV engineered linear amps below for greater DX or punching thru obstacles.

The TC70-1 has full bandwidth for color, sound, like broadcast. You can show the shack, home video tapes, computer programs, repeat SSTV, weather radar, or even Space Shuttle video if you have a home satellite receiver. See the ARRL Handbook for more info & Repeater Directory for local ATV rptrs.

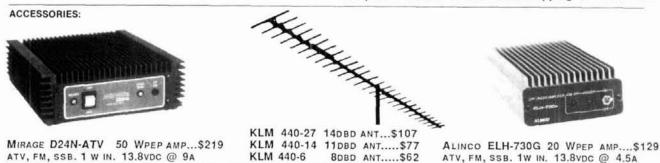PURCHASE AN AMP WITH THE TC70-1 & SAVE! 20 WATT WITH ELH-730G....\$412 50 WATT WITH D24N-ATV....\$499 All prices include UPS surface shipping in cont. USA



HAMS! Call or write for full line ATV catalog .... downconverters start at only \$59

## Wide Dynamic Range and Low **Distortion – The Key to Superior HF Data Communications**

- Dynamic Range > 75 dB
- 400 to 4000 Hz
- BW Matched to Baud Rate
- BER < 1 X 10<sup>-5</sup> for S / N = 0 dB
- 10 to 1200 Baud
- Linear Phase Filters



## ST-8000 HF Modem

#### Real HF radio teleprinter signals exhibit heavy

fading and distortion, requirements that cannot be measured by standard constant amplitude BER and distortion test procedures. In designing the ST-8000, HAL has gone the extra step beyond traditional test and design. Our noise floor is at -65 dBm, not at -30 dBm as on other units, an extra 35 dB gain margin to handle fading. Filters in the ST-8000 are all of linear-phase design to give minimum pulse

- 8 Programmable Memories
- Set frequencies in 1 Hz steps
- Adjustable Print Squelch
  - Phase-continuous TX Tones
  - Split or Transceive TX/RX
  - CRTTuning Indicator
  - RS-232C, MIL-188C, or TL Data
     Mark or Space-Only Detection
     Receive Clock Recovery
  - 8,600, or 10K Audio Input
- Signal Regeneration
- Variable Threshold Diversity
- RS-232 Remote Control I/O
- 100-130/200-250 VAC, 44-440 Hz
   8 or 600 Ohm Audio Output
- AM or FM Signal Processing
- 32 steps of M/S filter BW
- Digital Multipath Correction
- · FDX or HDX with Echo

distortion, not sharp-skirted filters with high phase

avoids distortion due to frequency conversion or

Bandwidths of the input, Mark/Space channels, and

post-detection filters are all computed and set for

the baud rate you select, from 10 to 1200 baud. Other

tone frequency; heterodyning is NOT used. This

introduced by abnormally high or low filter Q's.

standard features of the ST-8000 include:

distortion. All signal processing is done at the input

- Spectra-Tune and X-Y Display
- Transmitter PTT Relay
- Code and Speed Conversion
- Signal Amplitude Squelch
- · 3.5" High Rack Mounting

### Write or call for complete ST-8000 specifications.



### HAL Communications Corp.

Government Products Division Post Office Box 365 Urbana, Illinois 61801 (217) 367-7373 TWX 910-245-0784

## 2.3-GHz prescaler

## Extend your digital counter's dynamic range

**Some years ago, I built a prescaler** for my rf frequency counter which extended its operating range from 550 MHz to above 1300 MHz.<sup>1</sup> While this prescaler provided a means of measuring the frequency of 1296-MHz equipment accurately, it was never easy to use because of its limited input sensitivity.

Recently I built a prescaler for my present counter which virtually eliminates most of the shortcomings of that earlier model. This prescaler is based on a divide-bytwo integrated circuit, the Telefunken U822, which operates well beyond 2000 MHz. Unlike my earlier design, this prescaler incorporates a preamplifier to increase the useful dynamic range so that the input signal level does not need to be closely controlled.

#### circuit development

The U822 is a low-cost silicon monolythic IC designed for the consumer market in such applications as cable TV tuners and satellite TV downconverters. Packaged in a four-lead plastic housing similar to those used for low-cost RF transistors such as the MRF 901, the U822 operates from several hundred MHz up to at least 2.0 GHz and produces a low-level output at one-half the input frequency. A similar device, the U824, is useful as a prescaler for 600-MHz counters and electrically quite similar to the U822. The only major difference between the two is that the U824 divides by four rather than two. Although this article describes the U822, the U824 can be installed in its place without circuit changes if a divideby-four prescaler is desired.

#### dynamic range limitations

One problem with using the U822 to extend the operating frequency range of a digital counter is that the input power range (dynamic range) of the divider is quite limited. This means that the power level of the input signal must be held within close limits. If this is not done, the divider may not produce an output — or worse, it may produce a spurious output not at the correct frequency.


Generally the signals we wish to measure with a frequency counter aren't available at an optimum power level. Therefore it's more than a small nuisance to have to deal with the limited dynamic range of a divider in a prescaler used as a piece of test equipment. One solution to this problem is to increase the dynamic range of the prescaler. Then, we can be more confident that the output frequency is at exactly half the input frequency, and we'll be able to use the prescaler for a wide range of signal power levels.


#### limiting amplifier

One good way to increase the dynamic range of the prescaler is to place a limiting amplifier ahead of the divider. A limiting amplifier provides a constant output power over its entire input power range. Of course, all real amplifiers are limiting amplifiers in some sense, because there's a limit to their output power, but we usually don't try to operate them this way. The key point is this: a limiting amplifier will compress the dynamic range of the input signal to a much narrower output range, and this narrower output power range can be more suitable for the input of the digital divider. The question now is, what is the "suitable" range for the U822?

The data sheet for the U822 lists a minimum input signal power and frequency over which the divider is guaranteed to function properly. The input signal level must be greater than 150 millivolts RMS, and the divider will operate to a minimum of 2000 MHz. The maximum input signal power for operation isn't listed, but the maximum survival power (higher power may damage the device) is listed. In addition, the data sheet doesn't provide operational data on "typical" devices nor on operation *above* 2000 MHz. So, to design a limiting amplifier input for the prescaler, we need more detailed information on how the divider performs over a wide range of input power levels, and at various frequencies.

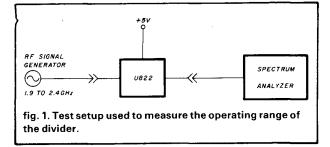**By Jerry Hinshaw, N6JH**, 142 Kensington Place, Frederick, Maryland 21701



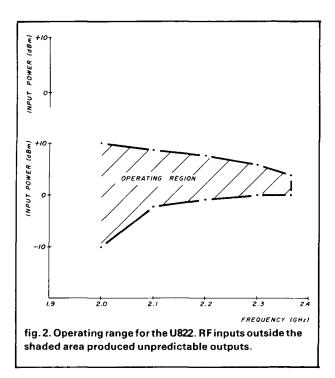

#### tests determine operating range

To get this data, a U822 divider was tested using the setup shown in fig. 1. The input frequency and power level were adjusted while the output signal frequency was monitored using a spectrum analyzer. (The spectral display gives a more sensitive indication of when the divider is beginning to malfunction than does a frequency counter. This is because the spectrum analyzer shows when the divider output signal starts to break up or develop nonharmonic spurious products more quickly than these problems would appear on a digital counter display.) The divider was monitored from about 1800 MHz, where it has a fairly wide dynamic range, to about 2400 MHz, where the operating range is very narrow. The results of these measurements are plotted graphically in fig. 2. The supply voltage to the U822 was held constant at 5.0 volts for these measurements. It is probable that by carefully tuning the supply voltage slightly over the range of 4.8 to 5.2 volts, the maximum operating frequency could be increased. However, it's clear that we're near the limits of the device already, and

further tuning would probably yield only marginal improvements.

#### U822 operating parameters

**Figure 2** clearly shows that the maximum and minimum input power limits converge to a point at which only one unique power level can produce a reliable output signal from the divider. Pilots call such a region in a flight performance curve the "coffin corner;" although the consequences for us are fortunately not fatal, the convergence does indicate the practical limit for the device. To the left of this limit is the operating range, and the "window" of permissible powers increases rapidly as the input frequency is reduced. Also, we can see by inspection of the curve that a power level of +5 dBm will provide satisfactory operation to above 2300 MHz. This information on the operating power ranges of the divider is what's needed to design a limiting preamplifier for the prescaler.

Figure 2 also shows the minimum signal level needed to deliver good divide-by-two outputs. The required level ran from  $-12 \, dBm$  at 1800 MHz up to the  $+5 \, dBm$  intersection at 2400 MHz. Thus, the dynamic range of the input decreases from 20 dB at 1800 MHz to 11 dB at 2100 MHz, down to only 6 dB at 2300 MHz. This means that to measure the frequency of an unknown signal, its power would have to fall within this narrowing region. If a limiting preamplifier stage were placed in front of the divider, the operating dynamic range could be increased both above and below the limits of the divider alone.

#### preamplifier design

By testing a U822 divider, I discovered that the desired preamplifier should provide ample gain up to at least 2400 MHz and should have an output power limit of about +5dBm. Naturally, it also would be nice to have wide bandwidth, low cost, small size and low power drain. Such a list of requirements would have been difficult to satisfy a few years ago, but monolythic silicon rf amplifiers that provide nearly all of these desired attributes are now available. They're small, have very wide bandwidth, and are less expensive than most low-noise rf transistors. Because they draw a fair amount of current, they do fall a bit short of our ideal, but only in terms of power drain. These "monolythic microwave integrated circuits" (MMICs) have been described recently in Amateur publications<sup>2,3</sup> and are available from stock at a number of distributors.


#### the MMIC


The MMICs described in References 2 and 3 are available from the manufacturer, Avantek, in four types. The data sheets for these devices list a number of operating characteristics, including the 1-dB compression point, which is the output power level where the gain has been reduced by 1 dB from the small-signal value. This compression point information is what we need to choose a device to limit near the +5 dBm point, which the U822 divider requires for best operation. In fact, the MMIC data sheets contain curves of output compression point versus bias current, which can help us choose an operating point most appropriate for this application.

Of the four devices, the MSA03 seems best suited for use as the prescaler amplifier because it has an output compression point of about + 5 dBm at 2000 MHz when operated at 25 to 30 mA bias. This compression point decreases with frequency, which matches the U822 operating window even better than if the compressed power level remained constant as the signal frequency increased. An MSA03 amplifier was assembled and tested for compressed power; the results are shown in **fig. 3**.

In addition to compressing input signals to the constant output power required at the U822 divider's input, the MMIC amplifier also provides gain to small signals, which would otherwise be below the operating range of the divider. Thus, if the preamplifier does its job properly, the dynamic range of the prescaler will be extended at both ends. The MSA03 will provide about 12-dB gain to small signals so that the bottom of the curve in fig. 2 should be lowered by about this much. The top end of the curve will also be raised, but there's a limit to how high it can go; the MSA03 amplifier itself has a "never exceed" input power specification of 100 mW. Thus, with just one stage of amplification using the MSA03 we can expect a greater than 20-dB increase in dynamic range, which is enough to transform what otherwise would be a temperamental prescaler into a useful test device.

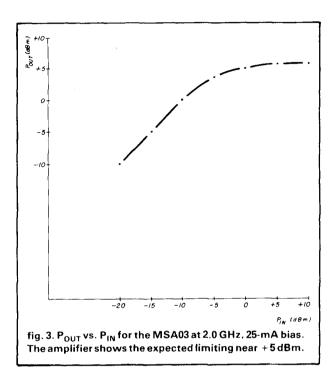The output power level from the U822 is about -20 dBm when driving 50 ohms. If this level isn't sufficient to drive the frequency counter, a second MSA amplifier could be installed on the same board following the divider to increase the output power. A single MSA03 will bring the divider's output up to at least -8 dBm (90 mV RMS), which should drive all but the least sensitive frequency counters.



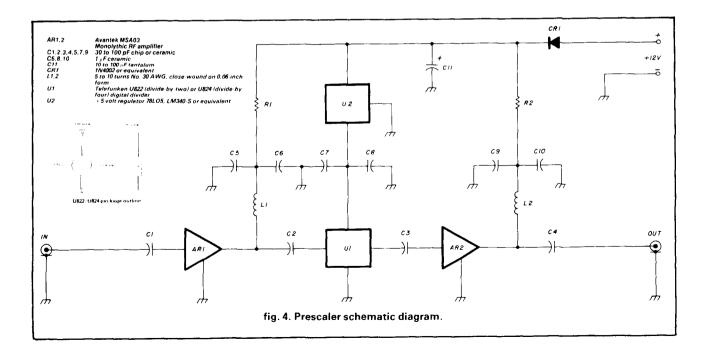

**New From** Spectronics!

## **The SONY AIR-8 is Here!**

Hand-Held Programmable PLL Scanner/Receiver For





#### HERE ARE SOME OF THE AIR-8's OUTSTANDING FEATURES!

· Computer controlled PLL tuning system · 40 memory presets · Multi scan system (manual and auto) • 11" Helical antenna w/BNC connector • Priority channel . Squelch (auto and manual) . Direct tuning

HERE'S TRUE SONY QUALITY! Feel the rugged construction, and listen to the high quality sound, and you'll know it's a Sony! The new Air-8 can scan four different frequency ranges in either direction and can store a total of forty frequencies in its four memory banks. You can recall any memorized frequency with the touch of a key, and can scan the ten channels in each of its four memory banks in any order. The Air-8 also has a delay function that prevents dropout enabling you to hear both sides of a conversation, and also a priority feature that samples a chosen frequency every three seconds for a signal. The guick-disconnect BNC connector allows different types of antennas to be easily coupled to the Air-8 for maximum performance. The Air-8 measures  $3\frac{1}{2} \times 7\frac{1}{2} \times 2^{\circ}$ , and weighs just 21 oz. This is truly a sturdy little compa-


nion that will give you years of dependable performance wherever you go.

8	bos	Frequency range	Tuning interval	1	frequency	The large black dol
PS8 AIR		144 174 MHz	5#Hz		Period sponses	indicates that the frequency
		108 136 MHz	25 kHz			is memorized to the 3 key
	M	76 108 MH2	50 kHz	N		15 75 V The small black
	SW	1601 2194 kHz (1603 - 2194 kHz)	1 kH2	AIR E	28.800.	the detail dot indicates that the To To To To the detay function as a chicated for th
АМ	MW	530 1600 kHz (531 1602 kHz)	10 kHz (9 kHz)	proticates that the implit Regimes in put of range	reducates that the	indicates that the program function is activated
	LW	150 529kHz (150 530kHz)	1 KH2			


#### THOUSANDS IN **USE WORLDWIDE!**


#### PACKED WITH SONY STATE OF THE ART TECHNOLOGY

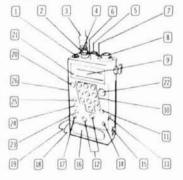(1) POWER Switch (2) Volume Control (3) 11" Helical Antenna (4) BNC Antenna Connector (5) Squelch Control. Features both manual and automatic modes. (6) Earphone Jack (7) AM External Ant Jack (8) Band Selector, Selects Air, PSB, AM, or FM. (9) LCD Display (See detailed illustration above) (10) Counter Keys. Used to program frequencies for direct tuning and memories, and also to recall memories. (11) EXECUTE Key (12) SCAN Keys. Used for scan tuning and manual tuning. (13) LIGHT Switch (14) KEY PROTECT. Locks out all keys on front face. (15) EXTERNAL DC INPUT (16) High Quality Speaker (17) ENTER Key. Used to memorize frequencies. (18) Battery Compartment (rear) (19) 9kHZ/10 kHZ Selector (Inside battery compartment). Used to change MW tuning interval. (20) DIRECT Key. Used for direct tuning. (21) LED Receive Indicator (22) MEMORY Scan Key. Used for scan tuning each memory bank. (23) PROGRAM Key. Used to initiate the program function. (24) DELAY Key (25) PRIORITY Key. Used for sampling a priority channel every 3 seconds. (26) Heavy Duty Body. Rugged military/industrial grade construction, AND DON'T FORGET... IT'S A SONY!





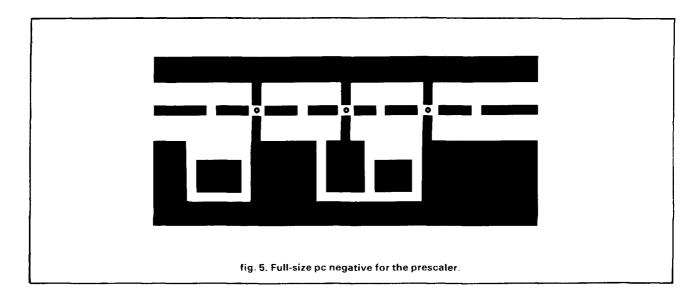

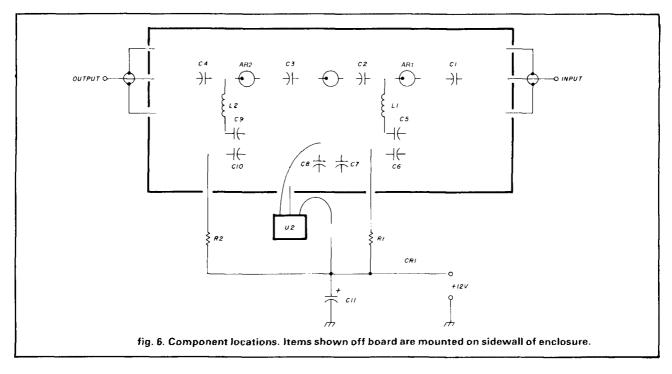

#### prescaler operation

Figure 4 shows the schematic diagram of the prescaler. The rf signal enters at the left and is coupled to the MSA03 amplifier through a small capacitor. The capacitor can be a small mica type — but for more uniform results and flatter gain response, I recommend using a chip capacitor. Reference 2 describes the selection of capacitor type and value in detail. Any capacitance from about 30 to 300 pF is a fair choice here, and will work for the 1- to 2.5-GHz range. At the output of the MSA amplifier, a second capacitor of the same type is used to isolate the DC supply, which reaches the amplifier through a small, hand-wound choke. Resistor R1 biases the am-

plifier, and for a 12- to 15-volt supply 200 to 240 ohms is appropriate.

The U822 requires + 5 volt bias, which is just a bit too low to be used on the MSA amplifier. Rather than run two separate power supply leads to the prescaler, a small voltage regulator is used to drop the 12-volt to 15-volt input to the 5 volts needed by the divider. Because the divider draws only about 30 mA, a small voltage regulator IC such as the 78L05 can be used. No heatsink is required at this power level.

Following the divider a second rf amplifier buffers the divider's output and increases the divided output signal to a higher power level. The U822 provides about +20

SPECIAL

#### SYSTEM #1 \$399.00

Motherboard with bios and first 64K of RAM. Upgradable to a full 640K of RAM. Flip top case. K8XT (at look alike) keyboard. 150 watt power supply with all the power needed to run extra drives and cards.

### SYSTEM #2 \$699.00

Motherboard with bios and first 256K of RAM. Upgradable to a full 640K of RAM. Flip top case. K8XT (at look alike) keyboard. 150 watt power supply. Dual Disk Drive card with cables. One floppy drive. DS DD 360K. A color graphics card with RGB and composite output.

(All you need is a monitor)

### SYSTEM #3 \$999.00

Motherboard with bios and first 256K of RAM. Upgradable to a full 640K of RAM. Flip top case. K8XT (at look alike) keyboard. 150 watt power supply. Color graphics card with RGB and composite outputs. Multi I/O card with two disk drive ports, one parallel port, one serial port and one serial port option, one game port, clock and calendar with battery backup. Two floppy disk drives DS DD 360K and a composite monitor.

SHIPPING INFORMATION: PLEASE INCLUDE 10% OF ORDER FOR SHIP-PING AND HANDLING CHARGES (MINIMUM \$2.50, MAXIMUM \$10), CA-NADIAN ORDERS, ADD \$7.50 IN US FUNDS, MICHIGAN RESIDENTS ADD 4% SALES TAX. FOR FREE FLYER, SEND 224 STAMP OR SASE.

HAL-TRONIX, INC. (313) 281-7773 12671 Dix-Toledo Hwy 12:00 - 6:00 EST Mon-Sat

P.O. Box 1101 Southgate, MI 48195

### MADISON WINTER SIZZLERS

\*NEW LUNAR AMPS......CALL FOR INFO\* \*NEW ICOM IC-275A + accessories......Call for Price



ICOM IC-28A List \$429.00 Yours for just \$369.00 \$AVE

"HAL" HAROLD C. NOWLAND W8ZXH 113

Kenwood TS-440.	Call for trade
ICOM R-7000 25-2000 MHz	
KDK FM 240	
B&W Viewstar Antenna Tuner	
Shure 444D	
Belden 9913 low loss coax	
Amphenol 831 SP-PL259 silverplate	
AEA Packet PK 232	
MFJ Packet 1270	
AEA 2 meter Isopole	
Diamond D-130 25-1300 MHz Discone	
Avanti AP 151.3G on glass	
Van Gorden SLA-1 160-80-40 sloper	
GE 6146B	

#### USED EQUIPMENT

All equipment, used, clean, with 90-day warranty and 30-day trial. Six months full trade against new equipment. Sale price refunded if not satisfied.

#### POLICIES

Minimum order \$10.00. Mastercard, VISA or COD. All prices FOB Houston except as noted. Prices subject to change without notice. Items subject to prior sale. Call any time to check the status of your order. Texas residents add sales tax. All items full factory warranty plus Madison warranty.

#### MADISON

Electronics Supply 3621 Fannin Houston, Texas 77004 (713) 520-7300 or (713) 520-0550 (800) 231-3057 dBm output into 50 ohms. Because this level is too low to drive many frequency counters, another MSA03 amplifier brings the signal up to about -8 dBm. If the second amplifier isn't needed, it can be omitted. Install jumpers over the cuts in the microstripline to complete the circuit from C3 to the output connector. If AR2 isn't installed, then C4, C9, C10, R2, and L2 may also be removed.

At the right, the divide-by-two output leaves the output connector. The U822's output is direct-coupled, so a coupling capacitor is used to prevent unwanted biasing of the divider by external voltage sources.

#### construction


The prescaler is built on a circuit board that can be etched from the full-sized negative artwork shown in fig. Alternatively, a prototype board can be made using the same artwork, and handcutting the traces with a sharp knife and peeling away the undesired pieces of copper. With either technique, leave the far side of the board as unbroken ground to form a ground plane for the microstrip circuit traces. Wrap the edges of the board with copper tape or thin brass shim stock. Solder both edges so that the top ground areas are well-connected to the bottom ground plane. The two ground leads from the MSA are run through the 0.15-inch hole in which the MSA amplifier is mounted. Then they're soldered to the ground plane on the far side of the circuit board. The output of the amplifier MMIC device is identified by a small bump on the top of the package next to the output lead.

The U822 divider is also mounted to the board in much the same way. A 0.2-inch hole is drilled in the board to clear the circular plastic package. The leads are then soldered flush to the traces, which connect them to the rest of the circuit. The U822 has four leads, as **fig. 6** shows. One lead each is used for the rf input, the divideby-two output, ground, and + 5 volt bias. The longest of the four leads is the output. The bias lead of the U822 should be well decoupled to ground. I used a chip capacitor, a small ceramic disk capacitor, and a tantalum slug capacitor. This combination, I hoped, would provide good RF decoupling at frequencies from a few Hz up to several GHz.

The biasing circuitry for the MSA and the voltage regulator are hooked up point-to-point along the edge of the circuit board and to the mounting points of the enclosure. Their locations are not critical if the rf amplifiers and the divider have been effectively decoupled on the board.

#### performance

Figure 7 shows the performance of the prescaler with its preamplifier in place. The improved dynamic range is markedly different from the operating window seen in fig. 2. With its preamplifier, the prescaler now has a much better input signal range, both above and below

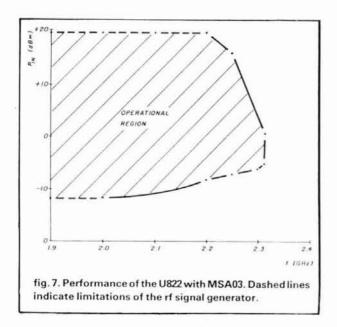

the levels which the divider alone could handle.

In recent years, digital integrated circuits have made it possible to build digital frequency counters for microwave frequencies. Just ten years ago, the fastest available counters operated at about 1200 MHz, but silicon bipolar dividers now on the market operate more than twice as fast. New Gallium Arsenide (GaAs) digital chips are in limited production, and although they're still too expensive for Amateur use, they promise yet another leap in performance in the near future.

#### references

1. Jerry Hinshaw, N6JH, ''1.5-GHz Divide-by-four Prescaler,'' ham radio, December, 1978, page 84.

2. Jerry Hinshaw, N6JH, "Monolithic RF Amplifiers," *ham radio*, March, 1986, page 22.

B. Atkins, KA1GT, "Microwave Amplifiers," QST, January, 1986, page 78.
 J. Browne, "GaAs IC Complements Budget 3-GHz Counter," *Microwaves and RF*, January, 1986, page 221.

5. JA6BI, "High Frequency Dividers," CQ Ham Radio, August, 1985, page 355 (in Japanese).

ham radio

#### short circuits rewinding transformers

#### SSTV with C-64

The address of the Journal of the Environmental Satellite Users' Group was shown incorrectly in the October article, "Get on SSTV with the C-64" (page 43). The correct address is 2512 Arch Street, Tampa, Florida 33607. (TNX WD4MRJ)

ham radio



### UNADILLA REYCO/INLINE<sup>™</sup>

## **Amateur Antenna Baluns**


For 20 years, preferred by Amateur, Commercial and Military Operators. First with built-in lightning arrester—minimizes TVI, maximizes power.

W2AU 1:1 & 4:1 \$17.95 W2AU 1:1 & 4:1 W2DU-HF \$19.95 W2DU-VHF \$19.95

#### W2AU Broadband Ferrite Core Baluns

For medium power (1000 watts RF min.) and broadband operation 3-40 MHz
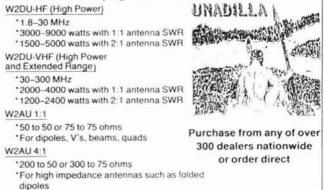
#### W2DU Non-Ferrite Very High Power Baluns




To request informational brochure, call

#### 617-475-7831 write

ANTENNA'S ETC.

PO Box 215 BV, Andover, MA 01810-0814
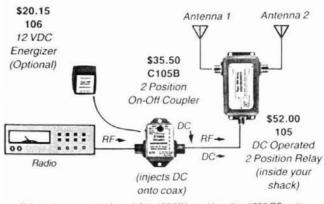
### Switch All Your Antennas Over One Coaxial Feedline



This system operates from 1.5 to 180 MHz and handles 1250 RF watts. Use our antenna switching kit and eliminate excess coax runs. With this kit and a single run of coax, you can switch between your antennas remotely. Use to add an antenna at modest cost, or change array direction.

Other types and combinations of relays are available. Please call or write us for more information, and save on your coax runs!

30 day MONEY BACK GUARANTEE on all products Unadilla/Reyco/Inline is now a Division of ANTENNA'S ETC.

115



## X-band beacons

A practical guide to component selection, installation, and operation

On the low bands, distant signals are almost always available to aid in adjusting antennas, checking out equipment, and investigating propagation. This isn't so on the microwave bands, where contests may provide the only microwave signals you're likely to hear. By the time the contest arrives, however, it's much too late for extensive testing of any kind.

One way of solving this problem is through use of a beacon that provides an ever-present, stable (but distant) signal. Fortunately, microwave beacons aren't particularly difficult or expensive to build.

Part 97, section 97.87 of the FCC regulations provides for Amateur beacons. All frequencies above 450 MHz — and some below 450 MHz — are available for automatically controlled beacons. Although no special authorization is required, some form of control is necessary.

I've had a X-band (10 GHz) beacon operating from a 2000-foot mountain near Ventura, California, for several years (see **fig. 1**). Coastal southern California is its intended coverage area.

The heart of the beacon is a 140-mW Gunn diode source operating on 10.256 GHz. The Gunn diode is fm-modulated with the repeating Morse message: "WA6EJO/B Ventura X band beacon." Control is provided by the W60RE remotely controlled station (fig. 2),' which simply turns the beacon's power supply on and off. Although this article pertains to building an X-band beacon, the same techniques can be applied to any microwave band where simple rf sources are available.

An X-band beacon consists of a signal source, an antenna, an IDer, a power supply, a weatherproof housing, and a control unit.

#### signal sources

A Gunn diode oscillator is a typical X-band source.

The Gunn diode itself\* is usually packaged in a small metal box or casting. There's a terminal for dc bias and an opening for the rf output. Pre-packaged Gunn diode oscillators used in intrusion alarms and police radars often appear on the surplus market.

The dc requirement ranges from about 5 volts to 15 volts, at a current level of tens to hundreds of milliamps, depending on the particular unit. This power should be well regulated because voltage fluctuations will result in fm-ing the frequency of the output (which comes in handy for modulation).

The power output is in the tens to hundreds of milliwatts — not levels capable of inducing rf burns, *but eye damage is a possibility*. Keep microwave sources, even weak ones, away from your head!

The frequency can usually be adjusted over a wide range, often hundreds of MHz, with a mechanical tuning screw. These are free-running, not crystalcontrolled, oscillators. Nevertheless, they're surprisingly stable after a few minutes warm-up. Sources from intrusion alarms and speed radars are usually tuned to 10.525 GHz, slightly above the Amateur band.

The Gunn diode oscillator used in my beacon is a surplus police radar unit purchased from Lectronic Research Laboratories for \$50.\*\* While that may not seem to be a bargain -1 have picked up Gunn oscillators at swap meets for \$5 - the power output is quite high. The unit is rated at 100 mW and, when measured, produced 140 mW.

Equally usable are IMPATT (IMPact ionization Avalanche Transit Time) diode sources, which take more voltage (70 to 90 volts), and Dielectric Stabilized Oscillators (DSO). Klystrons are definitely passé. Solidstate sources are generally cheaper, longer lasting, and safer (no high voltage).

When purchasing surplus microwave hardware, it's

By Steve J. Noll, WA6EJO, TiC Scientific, 1288 Winford Avenue, Ventura, California 93004-2504

<sup>\*</sup>Actually, the Gunn diode is not a true diode. It has no PN junction, but does have a designated anode and cathode.

<sup>\*\*</sup>Lectronic Research Laboratories, Atlantic and Ferry Avenue, Camden, New Jersey 08104.


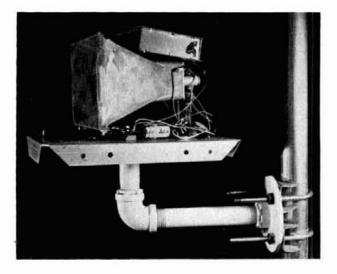


fig. 1. Beacon with cover removed.

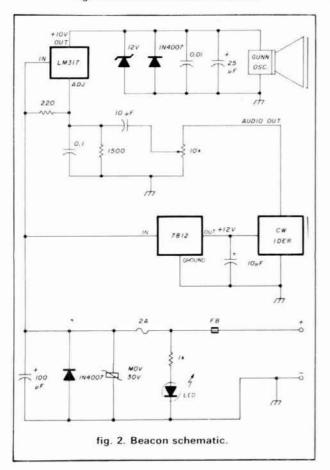

important to make sure you're getting the correct frequency range. The designation "X-band" actually covers a very wide range of frequencies, from 5.2 GHz to 10.9 GHz, with several different sizes of waveguide available. Rectangular waveguide is the transmission line of choice because sources, antennas, and other hardware are usually built to mate with rectangular waveguide flanges. The Amateur Radio Service portion of X-band is 10.0 GHz to 10.5 GHz, which includes the  $X_F$  and  $X_K$  sub-bands. The waveguide we are interested in measures 0.9 x 0.4 inches inside, and 1 x 1/2 inches outside. The designations for such guide are WR-90 (EIA) and RG-52/U (MIL). The flanges of interest are UG-39 and UG-40.

The waveguides for the frequencies just above and below the Amateur band differ only slightly in dimension; it's easy to pick the wrong one. When shopping at electronic swap meets, hamfests, or surplus stores, it's wise to carry a ruler or a waveguide flange of the correct dimensions for comparison.

Note that sources may actually have smaller rf output openings than the standard waveguide inside dimensions. In fact, the rf port may be just a round hole. Because of this, it's more important to judge surplus source frequency range by checking the spacing of the four No. 8 mounting holes at the flange corners. The spacing for UG-39 and UG-40 flange holes is 1-7/32 x 1-9/32 inches.

Let's say you've picked up a purported Gunn diode oscillator at the local swap meet or surplus emporium, but its voltage requirement isn't marked. Now what? Fortunately, it's not difficult to determine the optimum bias for a Gunn diode. An adjustable power supply, an attenuator, and a detector — or preferably, a power meter — are required.

Connect the source to the detector/power meter through the attenuator (10 or 20 dB, for protection). Run the supply voltage up, starting from 5 volts, and monitor the power output. It should peak somewhere between about 6 to 14 volts and then decline. *The peak is the operating point*.

I've applied this technique to three different X-band Gunn sources (**fig. 3**). A Solfan source started oscillating at 4 volts and had a broad peak at 8 volts with 8.5 mW out. A Racon source started oscillating at 4.5 volts and peaked at 9 volts with 30 mW out. A Greenray source started oscillating at 9 volts and peaked at 12 volts, with a 130-mW output.

A couple of important details: spurious low frequency oscillations can destroy a Gunn diode. (This can be prevented by connecting a 15- to 35- $\mu$ F capacitor and a 0.01- $\mu$ F capacitor across the diode.) Also, Gunn diodes can be damaged by reverse polarity. Usually the case of the Gunn oscillator is negative.

#### antennas

Although there are other kinds of microwave antennas, horns (fig. 4) are probably best for most beacon applications. They're commonly found on the surplus market, but if you can't find one, it's not difficult to make one from a short piece of brass waveguide, a brass flange, and some sheet brass (figs. 5A, 5B) available from hobby shops.\* Horns are also reasonably efficient and don't require tuning.

Where to get waveguide and flanges? Check surplus stores and swap meets for miscellaneous waveguide assemblies that have salvageable parts. But avoid aluminum waveguide and brazed brass waveguide unless it's already in a usable form. Soldered brass waveguide and flanges are best because they can be taken apart with a torch. Another source is Lectonic Research, which sells brass flanges (in the \$3 to \$6 range) and waveguide (at about \$4 per foot).

A horn is a directional antenna and essentially a flared, open waveguide. Short, small horns have wide, low-gain patterns; long, large-aperture horns have more gain and less beamwidth. Ideally, a microwave beacon should be positioned so that all users are situated in one direction from it. Power is hard to come by at X-band, so it's a shame to waste it on a widebeamwidth antenna.

What sort of gain and beamwidth is available from horns? The small horn used on the Microwave Associates Gunnplexer transceiver, for example, measures 3 inches long and has an aperture measuring about 3 inches by 3-1/2 inches; the gain is approximately 17 dB, with a beamwidth of 30 degrees. The Microlab/FXR X638A, a large X-band horn, measures 15 inches long and has a 7-5/8 by 5-5/8 inch aperture; the gain is 22 dB, with a beamwidth of about 12 degrees. As you see, as gain rises, horns get longer.

#### identifying

Part 97.84d3 requires that beacons be identified at intervals not to exceed 1 minute. If ID is by voice, the word "beacon" must follow the call sign. If ID is by CW, the call sign must be followed by the fraction bar DN and the letters "BCN" or "B." Although speech synthesis and speech recording chips are available, it's probably still cheaper and better to identify with CW. Commercial CW IDers are available. GLB and Autocode\*\* are two manufacturers of IDers in the \$50 price range. An IDer can be built, of course, and few parts are required. The WB2BWJ IDer is quite popular.<sup>2,3,4</sup>

Although SSB is on the way, most 10-GHz stations still use fm because the popular Microwave Associates Gunnplexer was designed to work on fm. Therefore, fm modulation of the beacon is in order, and it's fortunately quite easy to accomplish. As noted, power supply fluctuations will fm the rf output of a Gunn diode. So all that needs to be done is to inject a little modulated CW audio into the diode via a coupling capacitor.

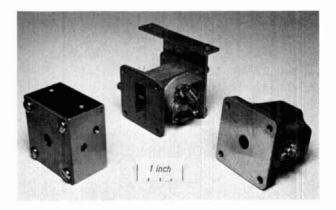


fig. 3. Surplus X-band Gunn Oscillators.

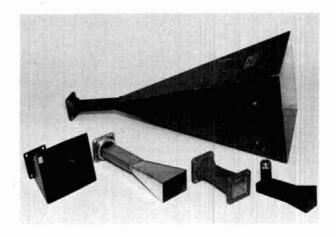


fig. 4. Examples of X-band horn antennas.

How much audio must be injected? That depends on the fm bandwidth of the receivers that will be monitoring the beacon. Probably the easiest way to determine the best amount is to adjust the IDer level while listening to the beacon output with a receiver typical of the type that will be monitoring the beacon.

In the case of my beacon, 100 mV peak-to-peak was required for a good signal as heard on a Microwave Associates Gunnplexer with a 3-dB-i-f bandwidth of 25 kHz. This voltage was measured at the Gunn diode. The IDer audio is actually coupled into the ADJ pin of the LM317 voltage regulator powering the Gunn diode.

#### power supply

Nothing's critical here. My beacon, including regulators, 140-mW rf source, IDer, and pilot light, draws a total of 400 mA from an unregulated 20-volt power supply. The unregulated supply is located in a cabinet, some 70 feet below the tower-mounted beacon. The supply consists of a 6-amp transformer, full-wave bridge rectifier, capacitive filtering, fuse protection of the line side, circuit breaker protection of the load side, and a solid-state relay for control. The raw dc is piped

<sup>\*</sup>See the RSGB VHF-UHF Manual for horn construction details.

<sup>\*\*</sup>GLB Electronics, 151 Commerce Parkway, Buffalo, New York 14224; Au tocode, P.O. Box 7773, Westlake Village, California 91359.

## TELEWAVE ANTENNAS

#### HAVE YOU EVER SEEN A MILLENNIUM SEAL?

The Land Mobile Communication recognizes the open dipole industry base station antenna, with a direct feed to each element, as the most versatile and efficent gain antenna available. Why doesn't everyone use this type of antenna? The answer is obvious; DURABILITY. The antennas supplied by major manufacturers of Open Dipole Antennas to the communications market today, have one common fault. After a short period of time, contaminants leak into the cable harness junctions and destroy the performance of the antenna. Finally, the problem has been solved by Telewave's new MILLENNIUM-SEAL<sup>TM</sup>. This space-age compound forms a permanent protective bond on the cable junctions that long outlasts all previous protective methods. Using our new MILLENNIUM-SEAL™ enhances the time proven design and by the application of our black epoxy coating over the alodined aluminum surface sets a new standard for the communications industry. Telewave is a full line supplier of all types of for antenna systems, including end fed fiber glass, and yagi antennas. We also offer 2 full compliment of communications cables and connectors for land mobile and microwave that meet every installation requirement.

INC.

POWER AMPLIFIERS

PREAMPLIFIERS GaAsFET

ATV

PREAMPLIFIER BUILT-IN

MML 144/100-LS 144 MHz 100 Watt HT AMP

MML 144/200-S 144 MHz 200 Watt GaAsFET

MML 432/100 432 MHz 100 Watt ATV/SSB/FM

MML 432/30-L 432 MHz 30 Watt HT AMP

MML 432/50 432 MHz 50 Watt / 10 Watt in

MML 1296/15 1296 MHz 15 Watts

MMC 435/600 70 cm Block Converter

MMG 144V 2 m BE Switched

MTV 435 20 Watt 70 cm xmtr

MMG 1296 23 cm

MML 144/30-LS 144 MHz 30 Watts HT AMP

1155 TERRA BELLA, MOUNTAIN VIEW, CALIFORNIA 94043 (415) 968-4400 • TWX 910-3795055

✓ 120

PX PRICE

\$129.00

242.00

429.00

232.00

429.00

219.00

CALL

65.00

111.00

69.00

299.00

### MICROWAVE MODULES Ltd.

LINEAR TRANSVERTERS	
SSB-CW-AM-FM	PX PRICE
MMT 50/28-S 50 MHz 20 Watts	\$342.00
MMT 50/144 50 MHz 20 Watts	342.00
MMT 144/28 144 MHz 10 Watts	186.00
MMT 144/28-R 144 MHz GaAsFET 25 Watts	342.00
MMT 220/28-S 220 MHz 15 Watts	242.00
MMT 432/28-S 432/435 MHz 10 Watts	285.00
MMT 1296/144-G 1296 MHz GaAsFET 2 W	362.00
MMT 1268/144 OSCAR Mode-L 2 Watt xmit	278.00
CONVERTERS	
MMC 144/28-HP 2 m GaAsFET	74.00
MMC 432/28-S 70 cm Down to 10 m	83.00
MMK 1296/144 23 cm Down to 2 m	186.00
CALL FOR CATALOG AND OSCAR SYSTEMS	C #

CALL FOR CATALOG AND USCAN STOLMS PRICES SUBJECT TO CHANGE WITHOUT ADVANCE NOTICE VISA MASTERCARD ACCEPTED








32 January 1987

up to the beacon via coax cable. The voltage regulators, a 7812 for the IDer and an LM317 for the Gunn diode, are located in the beacon housing.

Why not regulate the dc at the base of the tower? There are several reasons: voltage drop is one. The 20-volt supply allows for plenty of voltage drop in the trip up the tower. This also allows for more beacons to be added later by tee-ing power off the coax. Regulation right at the load also avoids hum and rf pickup that could occur through 70 feet of line.

#### lightning protection

Nothing but luck will save equipment actually struck by lightning. Serious damage from near strikes, however, can be avoided. A near strike took its toll on my beacon once and the result was blown fuses, a tripped circuit breaker, a blackened neon pilot light, a destroyed voltage regulator, and burned paint on the

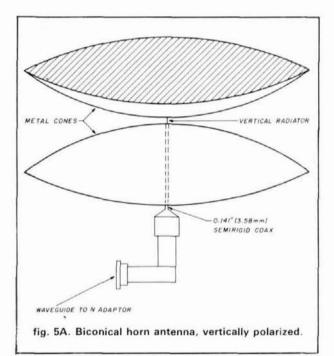

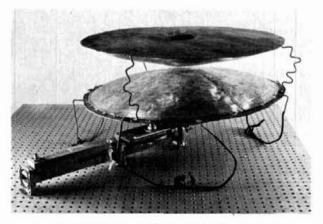


fig. 5B. Prototype X-band biconical horn.

power supply. But there was no damage to the valuable parts, the IDer, or the Gunn diode! This fortunate outcome wasn't entirely attributable to chance. The beacon and its power supply were judiciously designed using fuses, Metal Oxide Varistors (MOVs), polarity protection diodes, ferrite beads, and surge-absorbing capacitors. The three terminal voltage regulators have an innate capacity for load protection. And using coax instead of a pair of open wires for supplying power helps reduce induced voltage. Design as much protection in as possible; it just might pay off!

#### beacon enclosure

Presumably the horn antenna, rf source, and IDer will be mounted on a tower or pole of some sort. All are small enough to fit inside an enclosure less than a half cubic foot in volume. The horn needs to "look" into the atmosphere through an rf-transparent window, so at least one wall of the enclosure has to be made from a suitable dielectric.

Finding an appropriate plastic box is no small feat. Sunlight can be quite destructive; it will disintegrate some plastics in a very short period of time. (For example, polyethylene trash bags left in sunlight will deteriorate in a few weeks. White nylon cable ties crumble in a few months.) Plastics often contain ultraviolet stabilizers to improve their sunlight resistance, but you can't tell by looking if a given piece of material contains UV stabilizers or microwaveabsorbing additives.

Some have suggested testing the rf absorption of a material by placing it in a microwave oven, saying that if the material gets hot, it shouldn't be used. This sounds reasonable, but I really don't know how valid it is. Another test involves placing a piece of the proposed rf window material in front of a Gunnplexer and noting if much frequency "pulling" occurs, or if there's a change in mixer current caused by reflection. In the absence of any actual rf attenuation measurement capabilities, this method seems more reliable.

Some possible enclosures include plastic food storage containers, small plastic trash cans, computer diskette storage tubs, or wood or metal boxes with glass or Fiberglas<sup>™</sup> windows. Styrofoam<sup>™</sup>-type materials might not be advisable because birds would be able to peck through them readily.

I was lucky to find a plastic box perfect for this application (**fig. 6**). It once housed a roof-mount Multipoint Distribution Service (MDS) 2-GHz receiver and antenna, so its microwave transparency and weather resistance were already proven. I further protected the box from sunlight by covering all sides except the one that the horn shot through with adhesive aluminum tape.

I covered the Gunn oscillator with building insulation to slow temperature changes, and thus, frequency

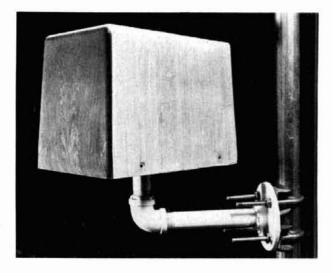


fig. 6. Beacon with cover in place.

drifting. You can cover the horn opening with plastic food wrap (such as Saran Wrap<sup>™</sup>) to slow air migration-induced temperature changes. For perfectionists who want to provide active temperature control, several circuits are described in the *Gunnplexer Cookbook*.<sup>5</sup>

#### control circuitry

Part 97.87b says, "A station in beacon operation, either locally controlled or remotely controlled, may also be operated by automatic control when devices have been installed and procedures have been implemented to ensure compliance with the rules when the duty control operator is not present at a control point of the station."

One can't just park a beacon on a hilltop and forget about it; control is required. This would presumably mean simply being able to turn it on and off. Ideally, a beacon would be located at an existing repeater or remotely controlled station (Remote Base) site and share the control link.

My beacon, or more specifically, its power supply, is operated by the control link of a remotely controlled station. If a control receiver must be built for your beacon, remember that Part 97.86d allocates all frequencies above 220.5 MHz, except 431-433 MHz and 435-438 MHz, for controlling ("auxiliary operation").

#### choosing a frequency

The Amateur X-band covers 10.0 GHz to 10.5 GHz. Considering the possibility of drift, it would be wise to stay clear of the band edges. The rigs most likely to use the beacon, the Microwave Associates Gunnplexers, are usually operated around the middle of the band anyway.

How do you find the middle – or for that matter, any portion of the band? If you don't have access to



fig. 7. Measuring beacon frequency with an HP-540B transfer oscillator.

a microwave frequency counter or wavemeter, one way is to use a Gunnplexer for a receiver and tune the beacon until it's heard. But how do we know where the Gunnplexer really is? You could build up a calibrator from a crystal oscillator and multiplier chain, hit a snap diode (an SRD) with a few hundred MHz of rf and generate a wee bit of X-band. Or, you could just hit a diode with a hundred mW or so of 146.52 MHz from a common 2-meter handheld.<sup>6</sup> The 70th harmonic will be 10.2564 GHz, close enough to the middle of the band.

Another affordable method of microwave frequency measurement involves using a surplus Hewlett-Packard 540B transfer oscillator (fig. 7). This instrument consists of a tunable 100- to 220-MHz oscillator, a diode mixer, and a small oscilloscope. The oscillator output and the signal to be measured are both applied to the diode mixer, which serves as a combination harmonic generator and mixer. The oscillator is tuned until a zero beat is observed on the oscilloscope. If we know, for example, that the source is somewhere between 10.1 GHz and 10.4 GHz, and tuning the 540B oscillator yields a zero beat at 205 MHz, the source is at 10,250.0 GHz (205 MHz x 50th harmonic). There are procedures given in the 540B manual for figuring the source frequency if the possible range is wider (approximate source frequency unknown). A frequency meter output is provided on the 540B for connection of a counter to obtain higher resolution than is provided by the oscillator dial. The source signal can be picked up by connecting a small horn antenna to the 540B mixer input with a waveguide to a type N adapter. The 540B will measure frequencies from 10 MHz to at least 12.4 GHz.

Remember, the packaging, and anything else near the front of the horn will "pull" the frequency somewhat. So whatever method is used for determining the beacon frequency, be sure that the final measurements are made with the beacon in its finished, packaged form.

# SAVE \$7.05 with HOME DELIVERY (one year newstand cost \$30.00)




2 years	12 issues 24 issues 36 issues (U.S. ONLY	\$38.95 \$49.95
Bill me la		
Check h	ere if this is	a renewal

Name	
Address	
City	
State	Zip

Please allow 4-6 weeks for delivery of first issue.

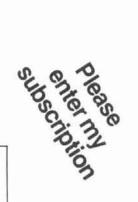FOREIGN RATES: Europe, Japan and Africa, \$37 for one year by air forwarding service. All other countries \$31 for one year by surface mail.



# \_\_\_\_

# **BUSINESS REPLY MAIL**


First Class Permit No 1 Greenville, NH

Postage Will Be Paid By Addressee



Greenville, NH 03048-9988

III.....Ihllandalladaladadadadadalli

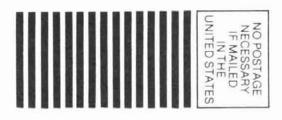

## expected range

How far away can you expect to hear an X-band beacon? Assuming a line-of-sight path, a 15-mW beacon, a Gunnplexer receiver with a very narrow (15 kHz) i-f, and small 17-dB horns on both beacon and Gunnplexer, you can expect a range of about 100 miles. With an 80-mW beacon and the same set-up, you can expect a range of about 200 miles. For a wide (200 kHz) i-f, 15-mW beacon, and two 17-dB horns, expect a range of about 30 miles, and about 60 miles for an 80-mW beacon.

If you use a 2-foot dish at the receiver and a 17-dB horn at the beacon, figure about 150 miles for a 15-mW beacon and wide i-f, 300 miles for an 80-mW beacon and wide i-f, 600 miles for a 15-mW beacon and narrow i-f, and a whopping 1200 miles with an 80-mW beacon and narrow i-f.

#### improvements

The best improvement you could make to the simple beacon presented here would be to increase the frequency stability. This would make the beacon not only an excellent tool for checking propagation, but also a frequency standard.

The easiest way to achieve better stability is through temperature control; proportional temperature control methods are discussed in the *Gunnplexer Cookbook*. <sup>5</sup> Better yet is to phase lock the Gunn oscillator to a crystal-controlled signal. Techniques for doing this with Gunnplexers, also described in the *Cookbook*, could probably be adapted to simple Gunn diode sources.

One might consider impressing telemetry on the beacon's signal. For example, it would be interesting to monitor the air temperature at the beacon site (as well as at the receive site) and see if there's any correlation between air temperature and signal strength. Ducting or inversions might be detected in this way. One possible method would be to connect an LM34 Fahrenheit temperature sensor IC\* to a 566 voltage-controlled oscillator IC. The resulting temperature-dependent tone would be used to modulate the Gunn source between IDs. A frequency counter on the X-band receiver would measure the tone frequency and yield the corresponding temperature.

Another telemetry candidate is relative humidity. Humidity sensors haven't been commonly available, but now Mepco/Electra (Philips) makes one that changes capacitance with humidity.\*\*

Still another option would be the ability to pipe the audio from the control link through the beacon. This would allow one-way X-band QSOs.

For better coverage, one might be tempted to install several Gunn sources on the same tower, each pointing in a different direction. Unfortunately, this is prohibited by 97.87a: "A station in beacon operation shall not concurrently operate on more than one frequency in the same amateur frequency band, from the same location."

Though it's not practical to get several free-running Gunn oscillators on exactly the same frequency, there may be other ways around this restriction. For example, each Gunn source could be served by a different IDer bearing the call of an Amateur responsible for that particular source. Or, each source could be switched on, IDed, and then switched off in succession so that none were operating concurrently.

#### operation

Although the 140-mW beacon is only 11 miles from my QTH, I've never been able to copy it there because of a small peak located in the middle of the path. It's estimated that the peak blocks the path by about 50 feet; even a Gunnplexer with a 2-1/2-foot dish won't pick up any knife-edging, although 1296-MHz signals over the same path are very strong. Other knife edgedependent shots have been tried without success.

When the path is truly line-of-sight, the beacon signal is, of course, quite strong. It has even been picked up around town, while mobile! In this case, the receive antenna was a vertically polarized, omnidirectional gain biconical horn fashioned from two pizza pans; the flat pans were beaten into cones and mounted with their apexes almost touching. A tiny driven element between the apexes was connected to the Gunnplexer with a waveguide-to-coax adapter. The whole works — essentially a horn spun about the vertical axis was then mounted on the top of a truck camper shell. (The biconical horn might make a good beacon antenna if an omnidirectional pattern is necessary.)

#### conclusion

A microwave beacon is a worthwhile project that can benefit many Amateurs. It isn't particularly difficult to build; perhaps the most difficult part is simply finding a site at which it can be installed. Might a beacon be just the catalyst you need to spark microwave activity in your area?

#### references

1. Steve Noll, WA6EJO, "Remotely Controlled Stations: A Look at A Successful Remote Base," *ham radio*, September, 1986, page 48.

2. Michael J. DiJulio, WB2BWJ, "Versatile CW Identifier," ham radio, October, 1980, pages 22-25.

3. Michael J. DiJulio, WB2BWJ, "An Improved Memory For the Versatile CW Identifier," *ham radio*, February, 1982, pages 24-26.

#### ham radio

<sup>\*</sup>Digi Key Corporation, P.O. Box 677, Thief River Falls, Minnesota 56701.

<sup>\*\*</sup>Goldsmith Scientific Corporation, 720 East Industrial Park Drive, Manchester, New Hampshire 03103.

<sup>4.</sup> Michael J. DiJulio, WB2BWJ, "Short circuits," ham radio, February, 1982, page 70.

<sup>5.</sup> Bob Richardson, W4UCH, "Gunnplexer Cookbook," Ham Radio Publishing Group, Greenville, New Hampshire 03048 (Chapter 5)(out of print).

Steve Noll, WA6EJO, "X-band Calibrator", ham radio, April, 1981, page 44.



# **1987 CALLBOOKS NOW AVAILABLE**

The 1987 CALLBOOKS are in! Place your order now so you can get full use out of your valuable investment. All the latest names, callsigns and addresses make these two books invaluable operating aids.

# NORTH AMERICAN CALLBOOK

Fully updated with all the latest up-to-date callsigns and addresses for all North American Hams. Includes handy operating aids such as; time charts, QSL bureaus, census information and much more. With calls from Panama to Greenland, every ham should have one in their shack. © 1986.

# INTERNATIONAL CALLBOOK

Callsigns and addresses for all Amateur Radio operators outside of the North American continent. Invaluable aid to getting QSL cards from foreign DX'ers. Includes plenty of extra information too! Universally recognized as the source of QSL information. © 1986. CB-F87 Softbound \$24.95

CB-US87 Softb

Softbound \$24.95

Order Both and SAVE. SPECIAL PRICE

\$44.95



# Only NRI teaches you to service all computers as you build your own fully IBMcompatible microcomputer

With computers firmly established in offices—and more and more new applications being developed for every facet of business—the demand for trained computer service technicians surges forward. The Department of Labor estimates that computer service jobs will actually *double* in the next ten years—a faster growth rate than for any other occupation.

# Total systems training

No computer stands alone... it's part of a total system. And if you want to learn to service and repair computers, you have to understand computer systems. Only NRI includes a powerful computer system as part of your training, centered around the new, fully IBM-compatible Sanyo 880 Series computer.

As part of your training, you'll build this highly rated, 16-bit, IBM-compatible computer system. You'll assemble Sanyo's "intelligent" keyboard, install the power supply and disk drive and interface the highresolution monitor. The 880 Computer has two operating speeds: standard IBM speed of 4.77 MHz and a remarkable turbo speed of 8 MHz. It's confidence-building, real-world experience that includes training in programming, circuit design and peripheral maintenance.

# No experience necessary— NRI builds it in

Even if you've never had any previous training in electronics, you can succeed with NRI training. You'll start with the basics, then rapidly build on them to master such concepts as digital logic, microprocessor design, and computer memory. You'll build and test advanced electronic circuits using the exclusive NRI Discovery Lab<sup>®</sup>, professional digital multimeter, and logic probe. Like your computer, they're all yours to keep as Your NRI total systems training includes all of this: NRI Discovery Lab to design and modify circuits • Four-function digital multimeter with walk-you-through instruction on audio tape • Digital logic probe for visual examination of computer circuits • Sanyo 880 Series Computer with "intelligent" keyboard and 360K double-density, double-sided disk drive • High resolution monochrome monitor • 8K ROM, 256K RAM • Bundled software including GW BASIC, MS DOS, WordStar, CalcStar • Reference manuals, schematics, and bite-sized lessons.



NRI is the only technical school that trains you on a total computer system. You'll install and check keyboard, power supply, disk drive, and monitor, following step-bystep directions.

part of your training. You even get some of the

most popular software, including WordStar, CaleStar, GW Basic and MS DOS.

# Send for 100-page free catalog

Send the coupon today for NRI's 100page, full-color catalog, with all the facts about at-home computer training. Read detailed descriptions of each lesson, each experiment you perform. See each piece of hands-on equipment you'll work with and keep. And check out NRI training in other high-tech fields such as Robotics, Data Communications, TV/Audio/ Video Servicing, and more.

SCHOOLS SCHOOLS McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue, NW, Washington, We'll give you tomorrow.  Computer Electronics Satellite Electronics Robotics & Industrial Control Data Communications	DC 20016 Industrial Electronics Communication Electronics Electronic Design Technology Telephone Servicing Digital Electronics Servicing Basic Electronics Electricians	For Career courses approved under GI Bill check for details Appliance. Servicing Small Engine Repair Air Conditioning, Heating, & Refrigeration Locksmithing & Electronic Security Building Construction Automotive Servicing Photography Bookkeeping & Accounting
Name (Please print)		Age

# AAIRAGE /KLM

# ANTENNA POLARITY SWITCHER MODEL APS-1

The APS-1 is a self-contained control head designed to allow remote polarity switching of circular antennas such as the Mirage/KLM range of crossed yagis.



The APS-1 may be powered by the power adaptor (included) or may alternately be powered from a vehicle or other 13-17 VDC source.

In addition to switchable outputs for two antennas, the APS-1 also contains a 6-13 volt regulated DC power supply. This feature is designed for powering items such as preamplifiers, VHF/UHF converters, etc., but may also be used whenever a low-current stabilized variable voltage source is required.

## SPECIFICATIONS:

Power Requirement (AC)	$\dots$ 117V $\pm$ 10% AC 50/60 Hz 15 Watt
Power Requirement (DC)	

Total output current 500 mA with AC transformer that is included, 1 amp with optional high current transformer or external DC supply. This unit has our popular five (5) year warranty.

- 126

P.O. BOX 1000

MORGAN HILL, CALIFORNIA 95037

(408) 779-7363



# top-down filter design

# Structured programming guides ladder filter design using real components

The design and construction of filters is a topic of increasing importance to Radio Amateurs. Mathematical advances in filter theory — from the simple m-derived filters so common two decades ago to those of today — have been paralleled by an increasing sophistication in the design of Amateur equipment requiring such filters. This trend can be seen by comparing the mere two pages of filter design information in the 1957 edition of the *ARRL Radio Amateur's Handbook* to the multiple pages, complete with design tables and an extensive bibliography, in the 1986 *Handbook*.<sup>1</sup>

However, it's one thing to design such a filter and an entirely different thing to construct one that works, especially at radio frequencies. Filters are designed assuming purely resistive terminations with perfect inductors and capacitors. Real filters are built with lossy reactive components, often with reactive terminations, and always with additional "components" in the form of lead inductances and stray capacitances. Sometimes, also, a series "trap" is added in parallel with the output of a filter to remove a particularly troublesome signal. These factors, then, may cause the frequency response of a real filter to be considerably different from the desired design response.

This article describes a computer program which will calculate the frequency response of a filter made from *real* components. Many Amateurs now have access to personal computers and can therefore "measure" the response of a real filter without building it and without the laboratory equipment that would be necessary to actually measure the response. The program is particularly useful for evaluating the response of a filter which is not terminated in its design load, but instead in some other impedance — for example, a tuned circuit.

The program is designed to analyze ladder filters (fig. 1). Most common filters are of this form.

# software design requires planning

It's a sad fact that most engineers and scientists are self-taught programmers. As such, they may not realize that a program must be "engineered" just as thoroughly as any hardware project. All too often, they may just start in writing code without having thought through the overall structure of the program. This is the software equivalent of starting the design of a receiver by calculating the values of resistors in an i-f amplifier.

Just as hardware design is approached from the overall to the specific — starting with block diagrams and desired stage characteristics — so must a program be designed from the outside inward. This is called "structured programming." Good programming techniques are important if the resulting programs are to be bug-free and robust. There are, alas, not many examples of this kind of software design in the Amateur literature, and many programs appearing in the Amateur literature are very poorly designed. The impetus to write this article came as much from a desire to help stamp out poor programming practices as a wish to share a very useful program.

This article, then, is a construction article. . . but it will be a program, not a piece of hardware, that is constructed.

The essence of structured programming is to describe the problem as clearly as possible. In this case, we want to analyze the attenuation vs. frequency response of a filter made with real components. The principal difficulty is that there is no simple way of characterizing a real component which is valid over a wide frequency range. Obviously, we can represent any component as a complicated, frequency-varying impedance. Such a representation is difficult to handle, and also presents the problem of somehow measuring real components in order to find out how they

**By J. A. Koehler, VE5FP**, 2 Sullivan Street, Saskatoon, Saskatchewan S7H-3G8

# The 1987 Handbook has it all!

The 1987 ARRL Handbook for the Radio Amateur is your source for the most up-to-date information on:

- Packet Radio and other forms
   Visual communication of digital communication
- ATV, SSTV, and FAX
- RF Circuits and design

Power amplifiers


Operating

Propagation

- Antennas and transmission lines
- Voice communication
- Space communication

The 64th edition has 40 chapters and over 1200 pages. It's packed with practical construction projects and there are many with printed-circuit board etching patterns. Every year the Handbook is updated to reflect changes in the state-of-the-art. Whether you are a radio amateur, engineer or technician you'll find the latest edition a must addition to your technical library. There is no change in price from last year! Paperbound: \$18 in the US, \$19 elsewhere; cloth: \$27 US, \$29 elsewhere. Payment must be in US funds. Add \$2.50 (\$3.50 for UPS) shipping and handling.

WA6P operated this solar powered packet station during 1986 Field Day as part of the McDonnell Douglas Amateur Radio Club and Southern California Amateur Club entry. The photographer was WA6AUF.

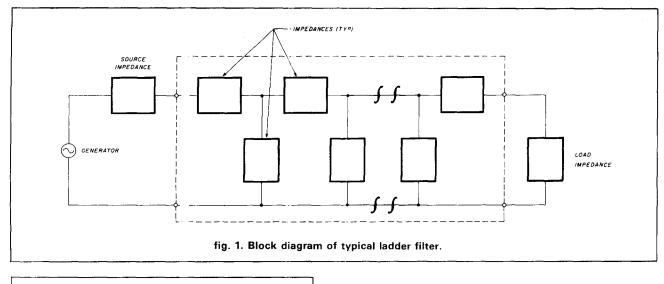

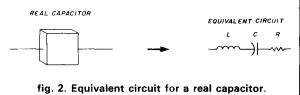


Table I. The quantities needed to specify a real compon-	
ent.	

Component	Quantities needed
Capacitor	Capacitance, lead inductance
Resistor	Resistance, lead inductance
Inductor	Inductance, Q, stray capacitance

vary with frequency. This approach is, in practice, unusable. The question is, how detailed should our model of a component be in order to give an adequate representation of its characteristics?

Consider a real capacitor, for example. The equivalent circuit of a real capacitor, as shown in **fig. 2**, can be represented by a series circuit consisting of a capacitor, an inductor, and a resistor. The problem arises because no single value for any of these components is completely valid for *all* frequencies.

Fortunately, for most real capacitors used in rf circuits (such as silver mica, polystyrene or small value NPO ceramic capacitors), the resistance value is close to zero and may be neglected. The inductance is due partly to the capacitor leads and partly to the internal construction of the capacitor, but can be fairly represented by just the lead inductance. We can therefore consider a real capacitor to consist of a capacitance in series with a lead inductance and have a model which is fairly good over a wide frequency range.

Similarly, real resistors have inductive and capaci-

tive elements. However, the stray capacitance across a resistor may usually be neglected and a real resistor can be represented as a perfect resistance in series with a lead inductance.

The most troublesome component is a real inductor. Real inductors have easily measurable losses as well as a stray capacitance which may be significant. The loss term is normally very frequency-dependent; one way of describing it is to use the *Q* value of the inductor according to:


#### $R = 2\pi f L Q$

where R is the equivalent resistance *in parallel* with the inductance. Unfortunately, this is only a first-order approximation. However, for filter responses over just a few decades in frequency, it's reasonably valid and provides a basis for computation. A real inductor, then, will be specified by an inductance, a Q value (valid for the frequency range of the desired filter response) and a stray capacitance. Fortunately, all these values may be fairly easily determined for a real inductor — the inductance and Q value by means of a bridge and the stray capacitance by measuring the selfresonant frequency of the inductor with, for example, a grid dip meter.

To summarize, real components of capacitors, resistors, and inductors may be specified by the quantities shown in **table 1**.

The basic circuit which is analyzed is that shown in **fig. 1**, but where every box is represented by a series or parallel combination of components with each component being described by values as listed in **table 1**. The whole filter consists of a regular structure of these boxes, alternately in series and in shunt between the source and the load.

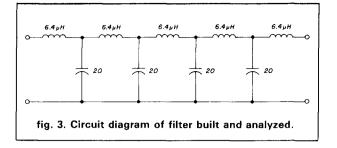For any frequency, the basic method of calculating the filter attenuation vs. frequency response (the ratio of load to source voltage) is what Hayward has called the "tackhammer" approach.<sup>2</sup> Each element has



a total impedance which can be calculated for that frequency. Then, the total impedance seen by the source can be calculated by starting at the load end and working towards the source. Assuming a source voltage of 1, the current from the source can be calculated and, working back towards the load, the voltage at each node of the network and the current into the succeeding leg can be calculated. The voltage at the last node will be the voltage across the load and this value, divided by 1 volt, will be the filter response at that frequency.

This is obviously a very tedious technique because it must be done for a number of frequencies if the overall filter response is to be evaluated. However, it's admirably suited to computer calculations.

Now for the construction portion of this article: the calculations needed for the filter response are sufficiently long that using an interpreted language such as BASIC would result in unacceptably long execution times. (BASIC also doesn't lend itself to structured programming techniques.) Instead, I used a compiled version of PASCAL, which is particularly well suited to this type of program because the programmer may define new variable types. In this program, I used this feature to define complex numbers and operations used in the calculations and in the definition of component "types" used to describe the real components.

Structured programming starts at the most general level and define the overall program flow, leaving the details for last. This is directly analogous to the best way of designing hardware, which is to start at the general and work down to the specific. If you were designing a receiver, for example, you would first determine all the features desired and then draw a block diagram showing all the major functional blocks needed to produce them. The software equivalent to the hardware block diagram would be a general outline of the program as a whole. Flow charts are often used for this, but many people, including myself, prefer to use "pseudo code." This is a description of the program in cryptic English sentences, in which each sentence describes a portion of the program that does a single, definable operation. For the filter analysis program, the general steps are, first, housekeeping (setting up the program variables, initializing the arrays to be used, and opening any files necessary) and second, repetitively describing the desired filter, calculating the response, and displaying the results until you're ready to quit.

The pseudo code description of the program I first wrote was the following:

INITIALIZE REPEAT GET ALL THE PARAMETERS DO THE CALCULATION DISPLAY THE RESULTS UNTIL DONE

Having the equivalent of a block diagram of the program, the next steps are to break each block (in this case, each sentence of pseudo code) successively into smaller and smaller pieces of pseudo code until each sentence is just a statement in the language being used. At this point, the program is complete.

Somewhere early on in this process, it's necessary to define the form of the data upon which the program will work. In this case, the data obviously consists of a description of the filter and the frequency limits of the calculations. So, part of the process of programming requires thinking carefully about how the data will be kept. Looking at **fig. 1** again, we see that there is a regular form to the shape of the filter. Starting at the source end, there are L-shaped sections consisting of a series section along the "top" and with a "leg" in shunt. The filter consists of a number of such pieces. The symmetry is broken only by the necessity of adding a source "element" in front of the filter and by having the last "leg" of the filter be the load element.

I chose, therefore, to describe the filter as an array of "arms" where each arm consisted of a "top" and "leg" pair of "elements." Each element could consist of a series or parallel combination of up to three "components." Each component would be either a resistor, inductor or capacitor and would be described by the values given in **table 1** for that particular kind of component.

Finally, having essentially written out the program in terms of operations on complex numbers, it was necessary only to write PASCAL code to describe how the operations were done. Normal good programming practices were followed throughout.

The object is to make the source code as readable as possible. The most common failing of beginning programmers is the omission of sufficient explanation in the source code to allow others to understand how the program works. Bear in mind that you're not really preparing these comments for others but rather, for yourself — next month or next year.

The program was written to handle ladder filters with up to nine "legs." Because frequency response is usually plotted on a logarithmic scale, the program

# KENWOOD

... pacesetter in Amateur radio

# **45 Affordable Watts!** TM-201B/401B SP-50B deluxe mobile speaker

# Super-compact mobile transceivers

The TM-201B boasts a powerful 45 watts output, easy-to-operate front panel controls, and ultra-compact size. The GaAsFET receiver front end provides high sensitivity and wide dynamic range. Receive and transmit characteristics are tailored for minimum distortion and excellent audio quality. Both the TM-201B and the TM-401B are supplied with a high-quality external speaker, 16-key DTMF microphone and mounting bracket.

- 45 watt output, with HI/LO power switch (TM-401B has 25 watts output.)5 W low.
- Dual digital VFOs TM-201B covers 142-149 MHz, includes certain MARS and CAP frequencies TM-401B covers 440-450 MHz
- 5 memories plus "COM" channel, with lithium battery back-up



- Programmable, multi-function scanning
- High guality external speaker supplied
- Audible beeper confirms operation

## **Optional accessories:**

- PS-430 power supply
- TU-3 or TU-3A two frequency tone encoder
- FC-10 frequency controller
- MC-55 (8-pin) mobile microphone
- SP-40 compact mobile speaker

- SW-100A/B SWR/power meters
- SW-200A/B SWR/power meters
- SWT-1 2 m antenna tuner
- SWT-2 70 cm antenna tuner
- PG-2N extra DC cable
- PG-3B DC line noise filter
- MB-201 extra mobile bracket



# **Optional FC-10 frequency** controller

Convenient control keys for frequency UP/DOWN, MHz shift, VFO A/B, and MR (memory recall or change memory channel).

More information on the TM-201B/401B is available from authorized dealers.



1M-401B is similar to the TM-2018, but covers 440-450 MHz and is 25 watts Specifications and prices subject to change without notice or obligation Complete service manuals are available for all Ino Kenwood transceivers and most accessores

#### TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220

# EIMAC Tubes Provide Superior Reliability at radio station KWAV – over 112,000 hours of service!



Ken Warren, Chief Engineer at KWAV- reports that their 10 kW FM transmitter went on the air in November, 1972, equipped with EIMAC power tubes. The original tubes are still in operation after over 13 years of continuous duty!

Ken says, "In spite of terrible power line regulation, we've had no problems with EIMAC tubes. In fact, in the last two years, our standby transmitter has operated less than two hours!"

Transmitter downtime means less revenue. EIMAC tube reliability gives you *more* of what you need and *less* of what you don't want. More operating time and less downtime!

EIMAC backs their proven tube

reliability with the longest and best warranty program in the business. Up to 10,000 hours for selected types.



Quality is a top priority at EIMAC, where our 50-year charter is to produce long-life products.

Send for our free Extended Warranty Brochure which covers this program in detail. Write to:

> Varian EIMAC 301 Industrial Way San Carlos, CA 94070 Telephone: (415) 592-1221




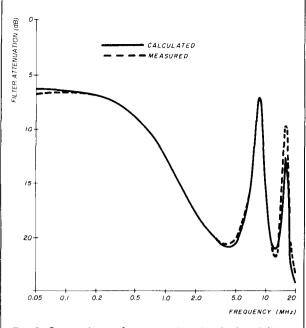


fig. 4. Comparison of measured and calculated filter response.

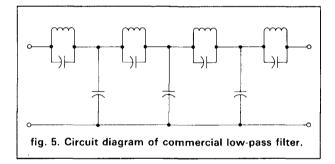

was designed to calculate the filter response at 50 frequencies, evenly separated logarithmically, between any desired lower and upper frequency limits. Both the number of filter legs and the number of points in the frequency response can be altered in the source code and the program may be recompiled with those values instead of the ones used.

As a test for the program, a four-leg filter was constructed and its frequency response was measured on the workbench. The circuit diagram of the filter is shown in **fig. 3**. This "filter" is not a valid design, but was constructed from components on hand to see how closely the calculated filter response was to the measured one. The measured data were compared to the response calculated by the program.

Each inductor was an Ohmite Z-50 rf choke. At 7.9 MHz, the measured inductance was 6.4  $\mu$ H with a *Q* of 100. These values were measured with a Boonton *Q* Meter. The parallel self-resonant frequency, measured with a grid dip meter, was 84 MHz. This corresponds to a parallel stray capacitance of 0.56 pF.

The capacitors were all 20-pF, 5 percent silver-mica capacitors, each with lead lengths of about 1/4 inch in total. Using the rule of thumb that No. 20 straight wire has an inductance of 20 nH per inch, the lead inductance was estimated to be 5 nH for each capacitor.

The filter termination was a coaxial 50-ohm load and the voltage across it was measured with an HP 411A rf millivoltmeter. The program was run with lower and upper frequency limits of 0.05 and 20 MHz, respectively, and the filter response was measured at the same frequencies used in the program. For frequencies below 1 MHz, the signal generator used was a AN/URM 25D with its output passed through a 20dB 50-ohm pad to make the output impedance 50 ohms resistive. Above 1 MHz, a Wavetek Model 3000 signal generator was used. The source and load elements were single 50-ohm resistors with zero lead inductance. As is evident in fig. 4, there is excellent agreement between the measured and calculated frequency responses. The disagreement between measured and calculated responses is greatest at frequencies where the filter attenuation is high and is probably attributable to measurement errors.

It's worth noting that the filter responses given by this program are all about 6 dB below what might be expected from a cursory glance at the setup. That is because, normally, filter response is given as the ratio of output to input voltage to the filter, whereas in this program the response is given as the ratio of filter output voltage to the internal "generator" source voltage. I did this because I wanted to be able to specify a source impedance which was not just purely resistive. For purely resistive sources and load *which are equal*, just add 6 dB to the program's values to get the numbers that are usually used.

As compiled, the program will handle ladder filters with up to nine legs. Although this may seem excessive, it will allow the calculation of the frequency response for many networks that may have far fewer legs. Consider the filter circuit shown in **fig. 5**. In some commercially-built versions of networks like this that I've seen, the parallel resonant circuit consisted of a small inductor and capacitor in the middle of a rather large shielded compartment with rather long leads going to the feedthrough capacitors which were in the partitions between compartments. In reality, these long leads have an inductive reactance which may be appreciable at higher frequencies. The actual circuit would be that shown in **fig. 6**.

This filter may be made into a ladder filter of the type used by the program by assuming that there are very large resistances to ground between the parallel sections and the series resistances, as shown in **fig. 7**. If values of, say, 100 megohms are assigned to these resistors, the calculated response of the filter won't be affected by them and will closely approximate the

# **ONE RADIO DOES IT ALL! BUSINESS/AMATEUR/C.A.P.**





# **TAD'S HOT** *M*8

- True 40 Watt Power
- Freg. Range 136-174 MHz
- 99 Channels
- Wide-Band (24 MHz)
- Programmable CTCSS, T.O.T.
- Multi Mode Scan
- Large LCD Display
- Cloneable
- FCC & DOC type-accepted
- Low Cost \$749.0

1 - 800 - 551 - 9922d usa 

2614 Western Avenue / Seattle, WA 98121

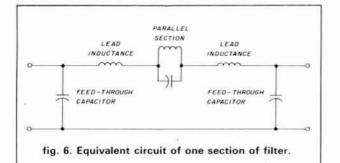

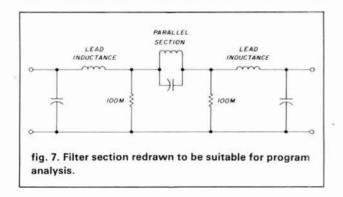



actual frequency response of the filter, as constructed.

A program like this allows you to predict, accurately, what the response for a real filter will likely be. I recently built a high-power (600-Watt) 6-meter amplifier. Using a spectrum analyzer, I noticed that there was a significant fourth harmonic output at 200 MHz. The problem turned out to be caused by excessive harmonic generation in the 25-Watt driver — a run-of-the-mill semiconductor, broadband amplifier. The simplest remedy seemed to be to put a low-pass filter between the driver and the final amplifier. I chose a precalculated standard-value capacitor (svc) design with a 3-dB corner frequency of 75.16 MHz.<sup>2</sup> This filter is a 7-element Chebyshev design; the schematic diagram is shown in **fig. 8**.

The program was first run for this filter with the assumption that the source and load were 50 ohm resistive, that inductors would have a Q of 100 throughout the desired range, and that the capacitors would have a lead inductance of 5 nH. The calculated filter response, very similar to the theoretical response for perfect components, is shown in fig. 9 as a solid line. However, the load provided to the filter by the amplifier isn't purely resistive because there's a tuned circuit in the transformer-coupled grid portion of the amplifier circuit. Indeed, the input to the amplifier is more like a 50-ohm resistance in parallel with a parallel tuned circuit. Assuming that this tuned circuit would be something like a 0.1 µH inductor in parallel with 100 pF, the calculated filter response with this load is shown as the dashed line in fig. 9 and deviates considerably from the theoretical response of the filter. Just out of curiosity, I also calculated the re-



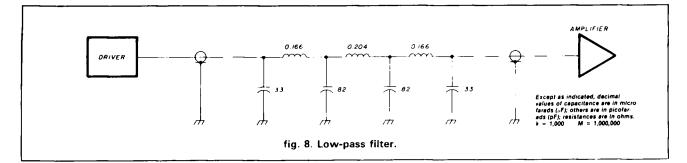

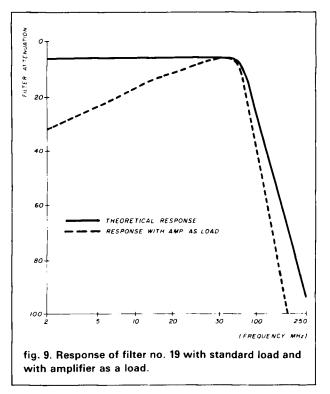

sponse of the filter into the same load (the amplifier), but with a filter in which the last 33 pF capacitor was replaced with a series trap at 200 MHz (a 0.1  $\mu$ H inductor in series with 6 pF). The response at 200 MHz, however, wasn't significantly affected by this "modification" to the filter, probably because the response was already down some 100 dB. Note that because of stray coupling and leakage, the practical ultimate stop-band attenuation will be less than 100 dB.

The point of all this is that the response of a filter in a real application may differ considerably from the theoretical response. This program allows one to "measure" a real filter response in a real situation.

It's also useful in examining various "what if" scenarios, in that it allows you to see what effect component tolerances have on filter response. You can observe the effects of "cut and try" solutions where you might, for example, replace a series section with a trap to remove a particularly troublesome unwanted signal. You can see what effect various load impedances have on the frequency response.

## getting the program

Photocopies of the program listing (Turbo PASCAL), which is too long to reproduce here, are available from the author for an SASE and one IRC or a 68-cent Canadian stamp. Diskettes including the program source code and executable files are available directly from the author for \$15 (U.S.) or \$20 (Canadian), on either CP/M 8-inch SSSD diskettes, Apple II CP/M diskettes, or in an IBM PC version on IBM PC-DOS diskettes. (Both an 8087 version and a non-8087 version of the executable program are included on the IBM PC diskette. The 8087 version runs considerably faster than the non-8087 version.)

The source code was originally written in a version of PASCAL called PASCAL MT +, marketed by Digital Research; source code for this version of PASCAL is included on the diskettes. The source code alone, modified to be compatible with DEC PASCAL on a VAX, is also available as VAX files on 8-inch RX01 diskette format for the same price.

The compiled and linked version of the program on the diskettes handles filters with up to nine legs and gives 50 points in the frequency response. Both these numbers may be changed and the program recompiled if necessary. The attenuation vs. frequency response is given in dB and the phase angles are in degrees.

#### references

1. Filter No. 19, Table 11, page 2-42, *1986 ARRL Handbook*, American Ra dio Relay League, Newington, Connecticut, 1985.

2. W. H. Hayward, W6ZOI, *Introduction to Radio Frequency Design*, Prentice Hall, 1982.

ham radio



# How to beat the high cost of cheap meters.



You get what you pay for. So get the Fluke 70 Series.

You'll get more meter for your money, whether you choose the affordable 73, the feature-packed 75 or the deluxe 77.

All of them will give you years of performance, long after cheaper meters have pegged their fishhook needles for the last time.

That's because they're built to last, inside and out. So they're tough to break. They don't blow fuses all the time. You don't even have to replace batteries as often.

And they're backed by a 3-year warranty. Not the usual 1-year.

Of course, you may only care that the world-champion 70 Series combines digital and analog displays with more automatic features, greater accuracy and easier operation than any other meters in their class.

You may not care that they have a lower overall cost of ownership than all the other "bargain" meters out there.

But just in case, now you know. For a free brochure or your nearest distributor, call toll-free 1-800-227-3800, ext. 229.

# FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.



FLUKE 73

\$79·



FLUKE 75



\$79*	\$99*
Analog/digital display	Analog/digital dis
Volts, ohms, 10A, diode. test	Volts, ohms, 10A, diode test
Autorange	Audible continuity
0.7% basic dc accuracy	Autorange/range
2000 + hour battery life	0.5% basic dc acc
3-year warranty	2000 + hour batte
	3-year warranty

FLUKE 77 Analog/digital display splay. Volts, ohms, 10A, mA mA; diode test Audible continuity Touch Hold" function curacy

Autorange/range hold 0.3% basic dc accuracy 2000 + hour battery life -year warranty Multipurpose holster

Suggested U.S. list price, effective November 1, 1985
 Patent pending.

#### J 131

IN THE U.S. AND NON-EUROPEAN COUNTRIES. John Fluke Mig. Co. Inc. P.D. Box C9090, M/S 250C. Eventl, WA 98206, Sales (206) 356-5400, Diner (206) 347-6100 EUROPEAN HEADDUARTERS. Fluke (Holland) B.V., P.D. Box 2269, 5600 CG Endbover, The Netherlands, (040) 458045, TLX: 51846 (© Copyright 1985 John Fluke Mig. Co. Inc. All rights reserved. Ad Net 4714-70

# The second service of the service of

# Antennas

HF, VHF, SWL, scanner, marine, & commercial for Mobile or Base. Cushcraft Mini-Products • Larsen B&W • Van Gorden Butternut • KLM Mosley • Hustler Telex Hy-Gain

# Towers

Unarco-Rohn, Hy-Gain, Tri-Ex Ask for special quotes on package deals including cable, guys, connectors, turnbuckles, etc.

# Accessories

Phillystran Kenpro • Alliance B&W • Telex Hy-Gain Daiwa • MFJ Bencher • Amphenol Astron • Welz B+K Precision

# Amplifiers

Diawa<sup>®</sup> • Ameritron Amp Supply • Vocom TE Systems Tokyo Hy-Power

# **Computer Stuff**

Packet Radio Hardware and Software for RTTY/Morse Hal • Kantronics Microlog • MFJ Ham Data Amateur Software.

# Shortwave

Panasonic Yaesu Kenwood Icom

Scanners Uniden/Bearcat Regency

More Radios Encomm/Santec KDK Ten-Tec NEW FT-23/73 Mini handheld for 2m or 440 MHz. 2.5 W output. 10 memories. LCD display.



FT-767GX All-mode transceiver. Cat system.

FT-757GX HF XCVR/Gen. Coverage Receiver.

FT-727G Dual-band handheld for 2m/440 MHz

SOFTWARE GX Turbo and Catpack for the FT-757GX and Catpack for the FRG-9600 Receiver



TS-440 HF XCVR with built-in Antenna Tuner.

TS-940 HF XCVR/Gen. Coverage Receiver.

TM-2530A / 50A / 70A 25/45/70-watt mobile 2m rigs.

> TM-201B 2m Mobile, 45-watts

Handheids TR-2600A, TR3600, TH21AT, 31AT, 41AT. Call for quotes



IC-735 Compact HF Transceiver

IC-751A HF XCVR/General Coverage Receiver.

VHF/UHF 2m- 27A, 27H, 271A, 271H 220 MHz- 37A 440 MHz- 471A, 471H, 47A

IC-02AT, 04AT Small, light HTs for 2m or 440 MHz. 10 memories and scan functions.

> IC-A2 in stock Aircraft handheld

IC-2AT, 3AT, 4AT, 12AT Handhelds for 2m, 220 MHz, 440 MHz, 1.2 GHz

Package Quotes on Radios/Accessories & Antennas/Towers

#### 13646 Jefferson Davis Highway Woodbridge, Virginia 22191 Store Hours: M-Th: 12 noon—6 pm F: 12 noon—8 pm

Free: 800-336-4799

(In New England: 800-237-0047)

EGE VIRGINIA

(In Virginia: 800-572-4201)

Information & Service: (703) 643-1063

Service Department: (703) 494-8750

Sat: 10 am—4 pm Order Hours: M-F 9 am-7 pm Sat 10 am-4 pm

## EGE NEW ENGLAND

8 Stiles Road Salem, New Hampshire 03079 New Hampshire Orders,\* Information & Service: (603) 898-3750 New England Orders: 800-237-0047 Store Hours: MTWSat: 10 am—4 pm ThF: 12 noon—8 pm Sun: Closed

\*Order and we'll credit you with \$1 for the call



Our Associate Store: Lacombe Distributors Davis & Jackson Road, P.O. Box 293 Lacombe, Louisiana 70445 Information & Service: (504) 882-5355

Terms: No personal checks accepted. Prices do not include shipping UPS COD fee: 52.35 per package. Prices subject to change without notice or obligation. Products are not sold for evaluation. Authorized returns are subject to a 15% restocking and handling fee and credit will be issued for use on your next purchase. EGE supports the manufacturers' warranties. To get a copy of a warranty prior to purchase, call customer service at 703:643-1063 and it will be furnished at no cost.

Much More in stock! Send \$1 for our New Fall Buyer's Guide-Catalog.

# **More Helpers**

- Marine radios by Icom
- Commercial Land Mobile by Yaesu
- Telephones by AT&T, Cobra, Southwestern Bell, & Panasonic
- CBs by Uniden, Midland, Cobra
- Radar Detectors by Uniden, Cobra and Whistler





# CIRCUIT ANALYSIS COMMODORE 64 LNCAP64

RF and Microwave Circuit Analysis can easily be performed using LNCAP64. Design and analyze RF circuits containing S,Z,Y and ABCD-parameters; R,L,C's, transmission lines, coupled lines, stubs and many other element blocks. Includes parallel and series branching and network combining; sensitivity and tuning mode. Also calculates stability factor for active networks. Print results to screen, disk or printer. Includes file editor with instructions and examples.

> NOW ONLY \$24.95 plus \$2.50 for S&H

BMA software 1234 Rousseau Drive Sunnyvale, CA 94087 (408) 732-9475 M.O. or Check Accepted. 1134

# MR. NICAD

# REPLACEMENT BATTERIES FOR COMMUNICATIONS

Yaesu, Kenwood, Santer, Azden, Tempo, Standard, Condless Finne etc.

> MR. NICAD E.H. YOST & CO.

EVERETT H. YOST RR = 1 BOX = 37 KB9XI SAUK CITY, WI 53583 (608) 643-3194

(608) 643-3194

✓ 133

# YAESU FT-757GX OWNERS

# Computer control your HF operation with GX Turbo.

Your computer belongs in your ham shack, especially now with powerful GX Turbo software.

GX Turbo runs with any Apple or Commodore 64/128, and really supercharges your FT-757GX operation.

Via computer control, you'll enter frequencies directly to VFOs and memories. Tune up and down, manually or automatically. Edit, save and load memory files. Exchange and copy frequencies between VFOs and memories. Even time a QSO and more.

So get the DX advantage with GX Turbo. For all the details, make a pit stop by your Yaesu dealer today.


Apple is a registered trademark of Apple Computer, Inc. Commodore 64 and Commodore 128 are registered trademarks of Commodore-Amiga, Inc.



Prices and specifications subject to change without notice.



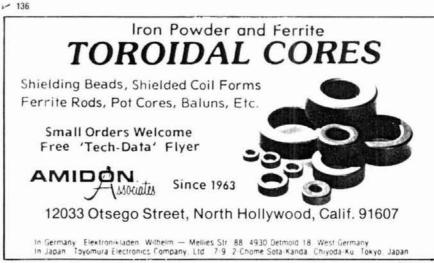Yaesu USA 17210 Edwards Road, Cerritos, CA 90701 (213) 404-2700 Yaesu Cincinnati Service Center 9070 Gold Park Drive, Hamilton, OH 45011 (513) 874-3100



# PERFORMANCE AND VALUE without compromise

# KRP-5000 REPEATER

# Word is spreading fast-"Nothing matches the KRP-5000 for total performance and value. Not GE, not even Motorola."


RF performance really counts in tough repeater environments, so the KRP-5000 receiver gives you 7 helical resonators, 12-poles of IF filtering, and a precise Schmitt trigger squelch with automatic threshold switching. The transmitter gives you clean TMOS FET power.

Enjoy high performance operation with: remote programmability, sequential tone paging, autopatch, reverse autopatch, 200-number autodial, remote squelch setting, status inputs, control outputs, and fieldprogrammable Morse messages.
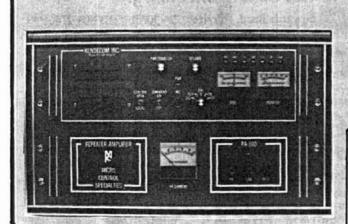
# Call or write for the full performance story ... and the super value price!

Micro Control Specialties 23 Elm Park, Groveland, MA 01834 (617) 372-3442

The first choice in Transmitters - Receivers Repeaters Repeater Controllers Power Amplifiers Voice Mail Systems



KRP-5000 Repeater shown with PA-100 Amplifier

# ham radio TECHNIQUES BUL WE SHI

# "white noise": technology bites back

When I received my ham license in 1934 I quickly got on the air with a three-tube receiver and a one-tube transmitter. The only problem was finding the band. It took me a week to make reasonably sure I was in the 20-meter band. After much confusion, I finally had two pencil marks on the dials of my receiver and transmitter. If my signal seemed to be near the marks, there was a good chance I was inside the band.

Today my transceiver reads out to 10 Hz in its flashing digits. Quite a change from the dear, dead days of 1934! But there's a price to pay for progress, and this price is becoming apparent — especially to Amateurs living in metropolitan areas where there are many stations per square mile. The price is white noise interference (phase noise).

What is white noise interference? I can tell you this: if you have it, you know it!

Just as white light is made up of light of many different wavelengths, "white noise" is made up of an infinite number of frequencies. Theoretically, white noise goes "from dc to daylight" with infinite amplitude. If you listen to it on a receiver, it covers an extremely wide band and sounds like a sizzling, frying background noise.\* When it's relatively weak, it sounds like a steady hiss. For the record, the *1986 ARRL Handbook* defines "phase noise" (which is a form of white noise) as "residual random variation of the phase difference between the synthesizer output and a perfect sine wave of the same frequency."

A representation of white noise is shown in fig. 1. In this hypothetical situation, the operating frequency of a signal is measured along the x-axis (frequency) and signal amplitude is measured along the y-axis. This drawing is of the white noise of a representative transmitter-exciter having a PLL (phase-lock-loop) frequency control system.1 The desired output signal is the tall "spike" at the center frequency. Below the signal, and on both sides of it, are sidebands (the noise "pedestal"), which gradually decrease in amplitude with distance from the desired signal. At some remote frequency, the noise sidebands disappear into the noise floor of the receiving system.

Spectral impurity, or phase noise, can be measured with reference to the noise floor or to the amplitude of the desired signal. It is commonly specified in terms of strength in a given bandwidth, measured a certain frequency from the main carrier. While spectral impurity is not specified for Amateur equipment, it is often given for commercial or miltary gear; the AN/PRC-117 transmitter, for example, has a noise limit of -162 dB/Hz, referenced to the carrier (dBc) at frequencies greater than  $\pm 10$  percent from the carrier.

A popular microwave signal generator has a specification or phase noise of greater than - 185 dBc (referenced to carrier) at 10-kHz spacing from the carrier

These specifications imply a certain

difficulty in measurement, since the measuring equipment is working with a signal ratio of much greater than 100 dB! Measurements of this type aren't done in the ham shack, or even in a reasonably well-equipped lab! They're not something a ham can easily check out and quantify on a late Saturday morning when the band is dead.

Nevertheless, white noise interference is becoming quite bothersome in areas of intense ham activity, particularly during contests. Unfortunately white noise generated in a PLL-type exciter is passed through a linear am plifier and boosted along with the desired signal.

## on-the-air effects

An easily-recognized symptom of white noise is a rushing sound adjacent to a strong carrier. Let me give you an example. Test's were run between my station and a local Amateur, about 3 miles away. We aimed our beams at each other one morning when the band was "flat." My friend's signal was 30 dB over S9 on my receiver. As he sent slow dashes, I tuned back and forth on each side of his signal. I instantly noticed a hissing sound that coincided with the transmitted dashes. Five kHz off the test frequency the hissing dashes were S5; 10 kHz away, the dashes were S2; 15 kHz away, the dashes were just above the noise level. We didn't try adding the linear amplifier to the tests because we wanted to examine only the exciter.

We now reversed the tests. My friend listened to my transceiver as I keyed it slowly. Sure enough, the same white noise was heard, even though the transmitters were of differ

<sup>\*</sup>On the lower HF bands it can be easily masked by at mospheric noise when an antenna is connected to a receiver. Ed.

# PAC-COMM DIGIPEATERS **DR-100 DR-200** SINGLE-PORT SOFTWARE OPTIONS

The Pac-Comm DR-100 and DR-200 are packet radio digipeater controllers which have been especially designed for dedicated repeater service. The DR-100 provides single-port controller capability at low cost. It is well-suited to any application where a singlefrequency digipeater is required.

The DR-200 is a dual-port controller. capable of digipeating on two separate frequencies and able to switch packets between ports. It is a basic network building block.

# **TECH LINE** (813) 874-2980

- DR-100 Single-Port Software -AX.25 Level 3 Switch -AX.25 Level 2 Digipeater
- DR-200 Dual-Port Software -AX.25 Level 3 Switch -KE3Z Dual-Port Digipeater -Southern California Dual-Port -Internet Protocol (TCP/IP)

# Amateur Net Price Schedule

	Kit	Assembled
DR-100	\$ 84.95	\$ 99.95
DR-200	\$139.95	\$159.95

# **DUAL-PORT**

Both digipeaters use a Z-80 processor which has up to 32k bytes of EPROM and two JEDEC sockets for 2/8/16/32k bytes of battery-backed RAM. Packet HDLC operations are handled in hardware by a Zilog 8530 SCC. Both use the AMD 7910 LSI modem chip. Each modem channel has a standard disconnect header and time-out timer. The CPU itself has a hardware watchdog timer and external hard reset line. The circuit board is RFI shielded by our extruded alumimum case. All connections are soldered to feedthroughs.

Write For Free Packet Catalog.

# ORDER DIRECT 800-223-3511 **FREE UPS BROWN** VISA Pac-Comm Packet Radio Systems, 3652 West Cypress St., Tampa, FL 33607 139



SERVICE CENTER for

# ICOM, KENWOOD

# and YAESU

Fully equipped repair shop Amateur, Marine and Land Mobile repairs.

> FCC NABER Lic Mon-Fri 10:00-4:00 pm

> > (206) 776-8993




Bob KG7D JA 140 23332 58th Ave. West Mountlake Terrace, Wa 98043

VISA soluced & C.O.D.S. Welcome

	"INSTANT" MORSE CODE
	WORSE CODE
	Beginners: Deliciously Easy
	Experts: Automatically Fast
	CURLYCODE™ MANUAL
	ONLY \$6.50
	Guaranteed
ľ	Minds eye Publications, Dept. H 21 Suite 115-199 1350 Beverly Rd. / 141 McLean, VA 22101
-	

7 M W

_	<u>\</u>			
MICROWAVE MODULES TRANSVERTERS				
MMT 1296/1440	1296 1298MH	z. 144if. 2w GA/	ASEE1 \$369	
MM1 432/28-S		28if. 10w		
MM1 220/28-S	220-225MHz	28if 10w	\$249	
MMT 144/28-R	144-146MHz 3	28if, 25w, DBM,	ψε το	
191911 19972011	GAASFET		\$339	
MM1-50/28-B	50-54MHz, 28i		<b>4</b> 007	
WIWLT JU/2011	high performa		\$349	
			3,04.0	
		RS & PREAMPS		
LT02S		Ow GAASFET DB		
L1335	902/144 Xvrtr		\$499	
L1235		10W GAASFET	\$549	
MICRO 13		0.5W GAASEET	\$399	
MICRO X		r 0.2W GAASEET		
DX144	144 Preamp 0	.4db nf 25db gai	n \$129	
DX432S	432 Preamp 0	.5db nf 20db gai	n \$179	
DX902S		5db nf 23db gai		
DX129S	1296 Preamn	0.5db nf 23db ga	in \$189	
DX2320S	2304 Preamn	0.8db nf 16db ga	un \$189	
MV144S-01	144 Swchd Pri	earno () 5db at	<b>Q</b> (0)	
1010 1440 01	25db gain	bump o odo m	\$199	
MV432S-01	422 Swebd Dr	eamp 0.5db nf	φ100	
WIV4323-01	25db gain		\$199	
MV902 S		eamp 1.0db nf	.0100	
MAA05 2	16db gain	camp roub m	\$219	
MV1296-S		reamn 1 0db 1 0		
MA (580-2		reamp roug ro	\$219	
0000054	16db gain	Mr		
DCW15A	Sequencer for	MV series Prear	nps \$69.	
HF 400		lay, 144 2KW 43	2.1KW\$119	
1220/28	220 MHz trans			
	- 28 or 50 IF, 1		\$220	
PA23200		er coolded PA.		
	2 tube, 200W	+.	\$275	
EME ELECTRON	10			
HF 400	Hinh power re	lay, 144 2kw, 43	2 1kw\$119	
PA23150	1296MHz 2 tu	be PA, 150 + V	/ \$369	
PA 1325	2304MHz 1 tu	be PA, 25 + W	\$349	
WATIMETER	432, 1296, 23		\$279	
PA23200		be PA, 200 + W		
PAZ3200	water coolers	bera, zou + w	\$275	
14/14/0		for 2C39, 7289.	\$C1.1	
WJ10		101 2659, 7769.	\$10	
	3CX100, etc.		•	
ALSO AVAILABI	e microwave i	MODULES, EME E	LECTRONIC	
TRANSVERTER		HANS PETER	S AVESCRUD	
BOX 6286 STAT		(416) 759-556		
10R0N10. 0N1		EVENINGS		
CANADA M5W		EALMDA/09	142	
CHINNON MON	11.0			

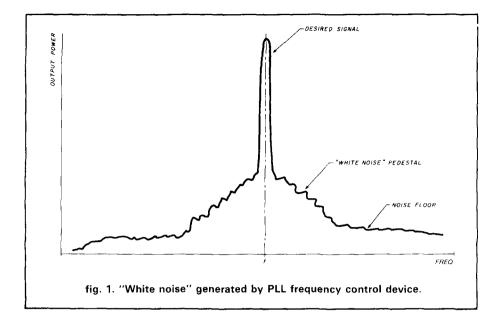

ent manufacture. I next cut out my external VFO (a PLL device) and cut in the internal VFO, which did not use PLL. I could thus test one frequency generation scheme against another at the push of a button. Using the internal VFO, the white noise disappeared immediately! My carrier was squeakyclean right up to my S9 plus 30-dB signal with no apparent sideband noise.

As an afterthought, my friend switched on his linear amplifier and keyed the transmitter. Alas, the hissing noise came up over an S-unit and was now apparent over nearly 100 kHz on each side of the main carrier.

What was the culprit? Most communications specialists believe the problem lies in the synthesizer technique, but instances have occurred in which white noise was generated in the solid-state final amplifiers of some equipment. It could also be mixing noise in some of the transmitter stages.

Amateurs in the western states well remember when a Voice of America transmitter operating on 21460 kHz switched over from crystal control to a frequency synthesizer. The whole top end of the 21-MHz band was obliterated by white noise, which was reported by Amateurs in South America as being over S9! The problem was finally resolved when the synthesizer was removed from service.

Talking to close friends who have some expertise in the subject indicates that transmitted white noise varies not only from make to make, but model to model, and from unit to unit of PLLcontrolled transmitters. Thus no specific make or model transmitter can be cited as being the main cause of the difficulty. The problem is much more complex than that.

## the solution?


The solution lies in the design of the synthesizer, as well as the lead dress and filtering. What is required is the establishment of ground rules that define the amount of white noise acceptable for a given transmitted power level just as in military gear. The problem of receiver overload seemed formidable a decade ago, but over the past few years it has been solved by the efforts of the equipment manufacturers. As to white noise, let's hope the same path will be followed. The first order of business is to recognize the problem; the next is to ascertain its magnitude. Does it affect only a few Amateurs? Or is it a more widespread problem, the cause of which has simply not yet been revealed to the general body of operators? I'll appreciate any comments that Amateurs may have regarding this subtle problem.

# 160-meter DX season – back again!

Hooray! The blasting summer static has dropped off in the Northern Hemisphere and Happy Days Are Here Again on 160 meters. Shown in fig. 2 is a top-loaded vertical antenna used by some operators who are trying to be loud even though they live on small lots. In most cases, it's made of wire and slung between two trees. The 40-foot vertical wire is attached to the midpoint of an 80-foot wire which serves as the top loading structure. The antenna is worked against ground, and resonated to the operating frequency by means of the seriesconnected rotary inductor. The feedpoint resistance depends upon the ground resistance, as is the case with any Marconi-type antenna. With a ground system consisting of a ground rod, or connection to the cold water pipe system of the dwelling, plus two or three guarter-wave radials, the feedpoint resistance will run about 20 ohms. A simple L-network may be reguired between the coax feed line and transmitter to drop the SWR to a low enough value to permit an easy match to today's modern solid-state equipment.

With regard to the ground system for a 160-meter Marconi-type antenna, Mitch, KB6FPW, has some interesting experiences to relate. He erected an inverted-L antenna (imagine the antenna of **fig. 2** with half the top wire removed). The wire was cut to a total length of 3/8 wavelength at 1.9 MHz. Most of the wire was in the horizontal plane.

His first rf measurements, using water pipe grounds, showed a feedpoint resistance of 100 ohms. Addition of a 4-foot ground rod and a quarterwave radial wire, wrapped around the perimeter of a fence and terminated in another 4-foot ground rod, brought the feedpoint resistance down to about 50 ohms. Mitch next added several extra radials of various lengths and a third ground rod. The feedpoint resistance dropped to 40 ohms. A second guarter-wave radial wrapped

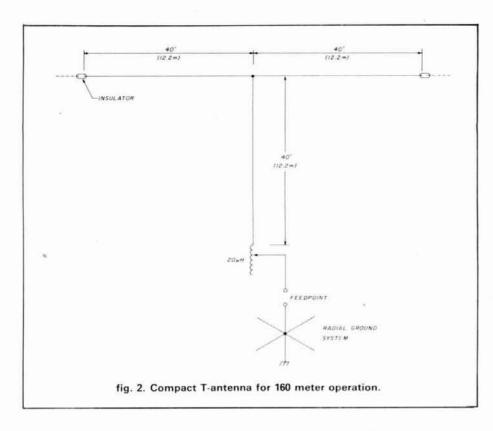

around the house didn't seem to make an appreciable difference. Mitch figured he had reached the point of diminishing returns, and there the experiment ended.

Mitch says, "There is a common misconception about ground radials. It's often said that a quarter-wave radial looks like a low impedance at the input end. If a short circuit (to ground) was applied to the far end of the radial, a high impedance would be reflected back to the input end. In free space this may be true, but when the radial is brought in close proximity to the ground, significant coupling exists enough to change the character of the radial. Terminating a quarter-wave radial, laid close to the earth, with a ground rod at the outer end does not reflect a high impedance back to the input end. Instead, it improves the efficiency of the radial and actually lowers its impedance.

"Electrically short radials depend upon proximity with the earth. I have performed experiments on 1750 meters with a 100-foot radial. When the wire was held clear of the ground (at about 4 or 5 feet elevation), the radial current was unmeasureable with a 100-mA rf ammeter. As the radial was lowered to the earth, the radial current climbed to a maximum figure of 8.5 mA."

Mitch, by the way, is conducting experimental VLF transmissions using the identifier MEL on 170.626 kHz.

## feedback from the field?

Great interest is expressed by newcomers to the 160-meter band: "What antenna should I use?" "What do the outstanding signals on the band use for antennas?" I'd like to hear from readers who have 160-meter antennas that work, and that may not be the common variety shown in all the handbooks. If you have an interesting antenna, write to me at: EIMAC, 301 Industrial Way, San Carlos, California 94070. Many thanks!

#### references

 Doug DeMaw, W1FB, and Wes Hayward, W7ZOI, "Modern Receivers and Transceivers: What Ails Them?," QST, January, 1983, page 12.

ham radio

Lodging - available at this time

Alexander Motel Fairborn Belton Inn Best Western Springfield Coach N Four Motel Command Motel Fairborn Cross Country Inn Crossroads of America Days Inn Dayton Mall Days Inn North Days Inn North Days Inn South Dayton Airport Inn Daytonian Hilton Econolodge Fairborn Motel Hampton Inn (Englewood) Holiday Inn Wright State Holiday Inn Dayton Mall Holiday Inn Fairborn Holiday Inn North Holiday Inn South Holiday Inn Troy Knights Inn Franklin Knights Inn Dayton North Knights Inn Dayton South Knights Inn Vandalia L & K Motel (Brandt Pike) LaQuinta Inn South Marriott Hotel Motel Capri Penny Pincher (L&K Troy) Ramada Inn Downtown Ramada Inn South Red Horse Inn Red Roof Inn South Rodeway Inn (Dayton) Rodeway Inn (Xenia) South Dayton Motel Traveler's Motel North Traveler's Motel South TraveLodge (North Dixie) York Motor Lodge Fairborn



# **Early Reservation Information**

# • Giant 3 day flea market • Exhibits

- · License exams · Free bus service
- CW proficiency test Door prizes

Flea market tickets and grand banquet tickets are limited. Place your reservations early, please.

# Flea Market Tickets

A maximum of 3 spaces per person (non-transferable). Tickets (for all 3 days) will be sold IN ADVANCE ONLY. No spaces sold at gate. Vendors MUST order registration ticket when ordering flea market spaces.

# **Special Awards**

Nominations are requested for 'Radio Amateur of the Year', 'Special Achievement' and 'Technical Achievement' awards. Contact; Awards chairman, Box 44, Dayton, OH 45401.

# License Exams

Novice thru Extra exams scheduled Saturday and Sunday by appointment only. Send current FCC form 610, copy of present license and check for \$4.25 (payable to ARRL/VEC) to: Mark Tessneer, 2859 Homeway Dr., Beavercreek, OH 45385

# Slide Show

35 mm slide/tape presentation about the HAMVENTION is available for loan. Contact Dick Miller, 2853 La Cresta, Beavercreek, OH 45324

# 1987 Deadlines

Award Nominations: April 4 Lodging: April 4 License Exams: April 4 Advance Registration and banquet: USA - April 11 Canada - April 4 Flea Market Space: Orders will not be accepted **before** January 1


# Information

General Information: (513) 433-7720 or DARA, Box 44, Dayton, OH 45401 Flea Market Information: (513) 223-0923 Lodging Information: (513) 223-2612 (*No Reservations By Phone*)

HAMVENTION is sponsored by the Dayton Amateur Radio Association Inc.
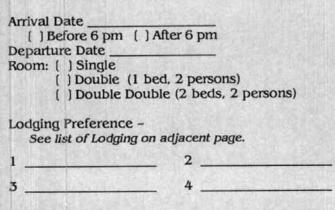
# Lodging Reservation Form

Dayton Hamvention - April 24, 25, 26 1987 Reservation Deadline - April 4, 1987 MAIL TO - Housing, Dayton Hamvention, 1980 Kettering Tower, Dayton, OH 45423-4880



Deposit required – Room deposit must be paid directly to the hotel or motel by date shown on the confirmation form sent to you. Use canceled check for confirmation.

# **Advance Registration Form**

# How Many

Admission (valid all 3 days)	@ \$8.00*	\$
Grand Banquet	@ \$15.00**	\$
Women's Luncheon (Saturday)	@ \$7.25	\$
(Sunday)	@ \$7.25	\$
Flea Market	@ \$23.00	\$
(Max. 3 spaces) Admission ticket must be ordered with flea market tickets	Total	\$

Make checks payable to - Dayton HAMVENTION. Mail to - Dayton Hamvention, Box 2205, Dayton, OH 45401

\* \$10.00 at door

\*\* \$17.00 at door, if available







Small enough to fit into a shirt pocket, our new 1.2 GHz and 1.3 GHz, 8 digit frequency counters are not toys! They can actually out perform units many times their size and price! Included are rechargeable Ni-Cad batteries installed inside the unit for hours of portable, cordless operation. The batteries are easily recharged using the AC adapter/charger supplied with the unit.

The excellent sensitivity of the 1200H makes it ideal for use with the telescoping RF pick-up antenna; accurately and easily measure transmit frequencies from handheld, fixed, or mobile radios such as: Police, firefighters, Ham, taxi, car telephone, aircraft, marine, etc. May be used for counter surveillance, locating hidden "bug" transmitters. Use with grid dip oscillator when designing and tuning antennas. May be used with a probe for measuring clock frequencies in computers, various digital circuitry or oscillators. Can be built into transmitters, signal generators and other devices to accurately monitor frequency.

The size, price and performance of these new instruments make them indispensible for technicians, engineers, schools, Hams, CBers, electronic hobbyists, short wave listeners, law enforcement personnel and many others.

#### STOCK NO:

#1200HKC	Model 1200H in kit form, 1-1200 MHz counter complete including all parts, cabinet, Ni-Cad batteries, AC adapter-battery charger and instructions \$ 99.95
#1200HC	Model 1200H factory assembled 1-1200 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger \$137.50
#1300HC	Model 1300H factory assembled 1-1300 MHz counter, tested and calibrated, complete including Ni-Cad batteries and AC adapter/battery charger \$150.00
ACCESSOR	NEC.

ACCESSORIES:

#TA-1005	Telescoping RF pick-up antenna with BNC connector
#P-100	Probe, direct connection 50 ohm, BNC connector
#CC-70	Carrying case, black vinyl with zipper opening. Will hold a counter and accessories \$10.00
144	accessories

ORDER FACTORY DIRECT



FLA (305) 771-2050

# **OPTOelectronics** inc

1-800-327-5912

5821 N.E. 14th Avenue Ft. Lauderdale, Florida 33334

Orders to US and Canada add 5% of total (\$2 min., \$10 max) Florida residents add 5% sales tax. COD fee \$2.

MasterCard

VISA

1.3 GHZ

1300 7548

AVAILABLE NOW!

# VHF/UHF WORLD for Reisert

# microwave and millimeter-wave update

Time really flies. Would you believe this month's column marks the beginning of the fourth year for "VHF/UHF World?" I'd like to thank those of you who have sent in such nice comments and ideas for future columns.

When I first started this column, I had about 15 possible topics outlined. Even though three years have gone by, that list is as long as ever. I'm always looking for constructive suggestions. Any ideas about subjects that need to be addressed or amplified? Just drop me a note. Your letters are always appreciated — even if I don't have time to answer them all.

About half of last year's columns were primarily oriented towards microwave and millimeter-wave subjects. This year I expect to continue in that vein. I hope I can keep the column well enough in balance so that all readers will be satisfied!

## microwave and millimeterwave update

North Americans were pioneers on the microwave and millimeter-wave bands, first with pulse and then "polaplexers."<sup>1</sup> However, in recent years we fell behind, especially in respect to our European colleagues. Most of the activity and DX records on these frequencies are presently held by Europeans. Even the "Gunnplexers" manufactured in the United States are being used in Europe to set new worldwide DX records!

We reviewed the general topic of microwaves in the January, 1986, column,<sup>1</sup> looking at available frequencies, DX records, microwave receivers, transmitters, antennas, feedlines, and

schemes for getting on the frequencies above 70 cm (450 MHz). Little did I know that 1986 would be such an explosive year for microwave and millimeter-wave growth in North America. Although none of the worldwide DX records held outside North America were reclaimed in 1986, many of the North American DX records were broken.

For starters, the 33-cm (903 MHz) DX record was extended — but this was to be expected because this band had been available to Amateurs for less than a year. K3YTL and W1JR held the record for just under one day (June 15, 1986); then K1WHS and K3YTL snatched the record! I expect that there will be several 33-cm DX extensions per year for the next several years as gear improves and activity increases.

The North American 23-cm (1296 MHz) tropo DX record was broken this past summer when KH6HME and WB6NMT spanned the Pacific. This record still stands worldwide and will be very difficult to extend much further!

Soon after the DX records were published in the January, 1986 column, the 13-cm (2304 MHz) North American tropo DX record was broken when W4ODW and WB5LUA caught one of those great openings that occur in the Gulf area early each year. They extended this DX record by about 40 miles.

The North Texas Microwave Society, after a real onslaught on the 13-cm band in 1985, decided to push higher in 1986 and challenge the 16-year DX record on the 9-cm (3456 MHz) band. It didn't take them very long; less than three months after they activated this band, one of the longest-standing North American DX records fell when WA5TNY/5 (portable) worked W7CNK/5, a fixed station in Oklahoma City, Oklahoma, for a new North American DX record of 221 miles. The QSO first took place on cw and then on two-way SSB.

The 6-cm (5650 MHz) North American DX record is now under fire by a hotbed of activity centered in northeastern Oklahoma. It looks as if this 9-year old DX record will soon be broken. Some one-way contacts have already exceeded the present 267-mile DX record on this band.

Finally, in the Pacific northwest, one of the first regions of the world to develop microwave activity and set DX records, the 12-mm (24 GHz) North American DX record has recently been extended by over 50 percent to 115 miles by WA3RMX/7 and WB7UNU/7. This record is rather unusual in that it was accomplished not only with very low power (20 milliwatts maximum), but with narrowband modulation. First the record was set on cw and then continued using two-way SSB perhaps the highest frequency where two-way SSB communications has ever been used by Amateurs, and perhaps even commercial interests as well.

Yes, 1986 was an exciting year for microwave and millimeter-wave activity, especially in North America. At long last it looks as if North Americans are again going to be in the forefront of activity and development on one of our highest frequency allocations.

To show the latest North American and worldwide VHF and above DX records, I've revised the tables published in references 1 and 2. **Table 1**  1. This table shows the latest claimed North American DX records on the frequencies above 6 meters. Note that the records are shown alphabetically by propagation modes. (Updated October 12, 1986.)

Frequency	Record	Date	Prop. Mode		DX
50 MHz	Note 2			miles	(km)
144 MHz	KA1ZE-WB0DRL	86-02-08	Aurora	1347	(2167)
	KH6GRU-WA6JRA	73-07-29	Ducting	2591	(4169)
	VE1UT-VK5MC	84-04-07	EME	10,985	(17676)
	W4EQR-W7HAH	81-07-09	Es	1881	(3027)
	W5HUQ/4-W5UN	83-07-25	FAI	1229	(1977)
	K5UR-KP4EKG	85-12-13	MS	1960	(3153)
	KP4EOR-LU5DJZ	78-02-12	ΤE	3933	(6328)
	K1RJH-K5WXZ	68-10-08	Tropo	1465	(2358)
220 MHz	W3IY/4-WB5LUA	82-07-14	Aurora	1145	(1842)
	KH6UK-W6NLZ	59-06-22	Ducting	2550	(4087)
	K1WHS-KH6BFZ	83-11-17	EME	5058	(8139)
	K1WHS-KOALL	85-08-12	MS	1274	(2049)
	KP4EOR-LU7DJZ	83-03-09	TE	3670	(5906)
	VE3EMS-WB5LUA	82-09-28	Tropo	1181	(1901)
432 MHz	W3IP-WB5LUA	86-02-08	Aurora	1182	(1901)
	KD6R-KH6IAA/P	80-07-28	Ducting	2550	(4103)
	K2UYH-VK6ZT	83-01-29	EME	11,567	(18612)
	W2AZL-W0LER	72-08-12	MS	1020	(1641)
	WA2LTM-WB5LUA	79-09-10	Тгоро	1310	(2108)
903 MHz	K1WHS-K3YTL	86-06-16	Tropo	310	(498)
1296 MHz	KH6HME-WB6NMT	86-08-13	Ducting	2528	(4068)
	K2UYH-VK5MC	81-12-06	EME	10,562	(16995)
	W4WSR-WA5TKU	85-06-03	Tropo	1112	(1790)
2304 MHz	PA0SSB-W6YFK	81-04-05	EME	5491	(8836)
	W40DW-WB5LUA	86-02-20	Tropo	628	(1003)
3456 MHz	WA5TNY/5-W7CNK/5	86-08-03	Tropo	222	(357)
5760 MHz	K5FUD-K5PJR	77-09-20	Tropo	267	(430)
10.368 GHz	WA4GHK/4-WD4NGG	84-08-07	Ducting	297	(478)
	W7JIP/7-W7LHL/7	60-07-31	LOS	265	(426)
24.192 GHz	WA3RMX/7-WB7UNU/7	86-08-23	LOS	115.5	(186)
48 GHz	W2SZ/1-WA2AAU/1	84-09-08	LOS	0.3	(0.5)
76-149 GHz	None reported				
474 THz	K6MEP-WA6EJO	79-06-09	LOS	15	(24)

Note 1. The records are listed alphabetically by mode. Ducting is suspected where the path is mostly over water. No efforts are made to separate out ducting on overland paths so they're grouped under tropo.

Note 2. Six-meter records were left off since the primary mode is often hard to distinguish. Also long-path QSOs have been reported during solar cycles 19 and 21 which exceed 12433 miles (20004 km).

shows the latest North American DX records on the bands above 50 MHz. **Table 2** shows the equivalent updated worldwide DX records. **Table 3** shows the worldwide EME DX records. Will the data in **Table 1** become ob-

solete before the end of 1987? I'll bet on it!

# why the increased activity?

1986 was a banner year for the microwave and millimeter-wave bands

primarily because North American microwave enthusiasts gathered together, organizing societies and conferences and pooling their interests and resources. New DX records were also on their minds. Until recently, the modulation for most North American microwave and millimeter-wave operation was fm or cw using a keyed multiplier chain. Fm requires a good signal-to-noise ratio and moderate to wide bandwidth. Keyed multipliers aren't always that stable, especially if operated in remote locations such as mountaintops.

For reliable communications, and especially DX, you need good frequency stability in the transmitter as well as in the receiver. Narrow bandwidth modulations such as cw and SSB are preferred. Also important are low noise figure receivers, reasonable transmitted output power, moderate- to highgain low-noise antennas, and low insertion loss feedlines. All these factors had to be addressed if real progress was to be forthcoming.

The same Amateurs who recently activated the microwave bands were also spurred on by the desire to use some of the new state-of-the-art technology that has recently become so affordable. After designing and building this new equipment, they organized mobile stations to travel to DX locations and to aid in activating new ''grids'' for the ARRL VUCC (VHF/UHF Century Club) award.

# equipment considerations

If you want to take advantage of cw and SSB with its improved higher signal-to-noise ratio, you must pay close attention to frequency stability. Receiver/transmitter frequency stability objectives can best be met on the microwave/millimeter-wave bands by using solid-state up/down converters or transverters.

Many homebrew as well as commercial designs are now on the market. Modern solid-state transceivers are now available through 1300 MHz and are often used as the transmit/receive i-f for these same converters/transverters. The combination of

2. This table shows the latest claimed worldwide terrestrial DX records for the Ama-	
teur bands above 6 meters.	

Frequency	Record Holder	Date/QSO	Prop.Mode		DX
50 MHz	Note 1.			miles	(km)
70 MHz	GW4ASR/P-5B4CY	81-06-07	Es	2153	(3465)
144 MHz	I4EAT-ZS3B	79-03-30	TE	4884	(7860)
220 MHz	KP4EOR-LU7DJZ	83-03-09	TE	3670	(5906)
432 MHz	KD6R-KH6IAA/P	80-07-28	Tropo duct	2550	(4103)
903 MHz	K1WHS-K3YTL	86-06-16	Tropo	310	(498)
1296 MHz	KH6HME-WB6NMT	86-08-13	Tropo duct	2528	(4068)
2304 MHz	VK5QR-VK6WG/P	78-02-17	Tropo duct	1170	(1883)
3456 MHz	VK5QR-VK6WG	86-01-25	ducting	1171	(1885)
5760 MHz	G3ZEZ-SM6HYG	83-07-12	ducting	610	(981)
10 GHz	IOSNY/EA9-IOYLI/IE9	83-07-08	ducting	1032	(1660)
24 GHz	I3SOY/3, IW3EHQ/3- I4BER/6, I4CHY/6	84-04-25	LOS	180	(289)
47 GHz	HB9AMH/P-HB9MIN/P	85-01-13	LOS	31.7	(51)
75 GHz	HB9AGE/P-HB9MIN/P	85-12-30	LOS	0.3	(0.5)
474 THz	K6MEP-WA6EJO	79-06-09	LOS	15	(24)

Note:

1. Six meters has been left blank on this listing because long-path QSOs (those exceeding 12440 miles or 20016 km) have been reported during solar cycles 19 and 21.

Band	Record Holder	Date/QSO	Prop.Mode		DX
				miles	(km)
50 MHz	K6MYC-K8MMM	84-07-24	EME	2127	(3422)
144 MHz	K6MYC/KH6-ZS6ALE	83-02-18	EME	12088	(19450)
220 MHz	K1WHS-KH6BFZ	83-11-17	EME	5058	(8139)
432 MHz	F9FT-ZL3AAD	80-04-18	EME	11679	(18793)
903 MHz	none reported				
1296 MHz	PA0SSB-ZL3AAD	83-06-13	EME	11595	(18657)
2304 MHz	PA0SSB-W6YFK	81-04-05	EME	5491	(8836)

a stable solid-state converter/transverter and i-f will produce stable operation on CW and SSB. It also permits moderate to narrow i-f bandwidth and its commensurately better signal-tonoise ratio is especially desirable for receiving weak signals. Finally, this combination will usually be more reliable and small to moderate in size, making it a good choice for portable operations, especially from high elevations free of local obstructions.

## conversion schemes

Before you start to design and build microwave and millimeter-wave gear — especially if you want to advance the state of the art — you should first develop an overall plan of attack. Foremost in that plan is choosing the frequency conversion scheme, which is very important because it affects cost, complexity, performance, and future flexibility.

The first step is to identify the generally accepted weak-signal microwave operating frequencies. Those for 13-cm and above were set up many years ago as multiples of 1152 MHz, as discussed in reference 1. These frequencies, as well as the generally accepted frequencies on the lower microwave bands, are shown in **table 4**.

Note that since the microwave frequency plans were originally established, some slight modifications have been made to accommodate EME. EME operation is now centered around this frequency with a guard band of at least  $\pm$  50 kHz. In North America it is now standard operating practice to use the frequency 100 kHz above the old operating or EME frequency for the terrestrial cw/SSB calling as shown on

# 1987 CALLBOOKS



# The "Flying Horse" sets the standards

Continuing a 66 year tradition, there are three new Callbooks for 1987.

The North American Callbook lists the calls, names, and address information for licensed amateurs in all countries from Canada to Panama including Greenland, Bermuda, and the Caribbean islands plus Hawaii and the U.S. possessions.

The International Callbook lists the amateurs in countries outside North America. Coverage includes South America, Europe, Africa, Asia, and the Pacific area.

The 1987 Callbook Supplement is a new idea in Callbook updates; it lists the activity in both the North American and International Callbooks. Published June 1, 1987, this Supplement will include all the new licenses, address changes, and call sign changes for the preceding 6 months.

Publication date for the 1987 Callbooks is December 1, 1986. See your dealer or order now directly from the publisher.

	ican Callbook	
	g within USA	\$28.00
incl. shippin	g to foreign countries	30.60
Internationa	al Callbook	
	g within USA	\$28.00
incl. shippin	g to foreign countries	30.60
Callbook Su	pplement, published J	une 1st
incl. shippin	g within USA	\$13.00
incl. shippin	g to foreign countries	14.00
SPECIAL OF	FER	
Both N.A. 8	International Callboo	
incl. shippin	g within USA	\$53.00
incl. shippin	g to foreign countries	63.00
•		
	sidents please add 61/2%	
All paym	ents must be in U.S. fu	nds.
RADIO AMA	TEUR	
C	allbook M	C.
10	Dept. F	
	925 Sherwood Dr., B	ox 247
Contraction.	Lake Bluff, IL 60044	
	Lake Blain, in ood44	, 054
	12) 234 6600	marker
Tel: (3	12) 234-6600	X
_		_
	1	CE
- 145	January 1987	60

# MAKE CIRCUIT BOARDS THE NEW, EASY WAY



WITH TEC-200 FILM

- JUST 3 EASY STEPS:
- Copy circuit on TEC-200 film using any plain paper copier
- · Iron film on to copper clad board
- · Peel off film and etch
  - SATISFACTION GUARANTEED convenient  $8\frac{1}{2} \times 11$  size
  - 5-Sheets for \$3.95 10 sheets only \$5.95 add \$1.00 postage – NY res add sales tax

The MEADOWLAKE Corp.

Dept. S. P.O. Box 497 - 146 Northport, New York 11768



 Covers 100 MHz to 199.999 MHz in 1 kHz steps with thumbwheel dial . Accuracy +/- 1 part per 10 million at all frequencies . Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate • External FM input accepts tones or voice . Spurs and noise at least 60 dB below carrier . Output adjustable from 5-500 mV at 50 Ohms Operates on 12 Vdc @ 1/2 Amp Available for immediate delivery • \$429.95 delivered • Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator · Call or write for details · Phone in your order for fast COD shipment. - 147

# VANGUARD LABS

196-23 Jamaica Ave., Hollis, NY 11423 Phone: (718) 468-2720 Mon. thru Thu.



4. Typical North American weak-signal microwave operating and calling frequencies for EME and terrestrial operation.

Band (cm)	EME center frequency (MHz)	Weak-signal callin frequency (MHz)	
33	903.0	903.1	
23	1296.0	1296.1	
13	2304.0	2304.1	
9	3456.0	3456.1	
6	5760.0	5760.1	
3	10368.0	10368.1	

**table 4**. Calling frequencies are great for finding activity, especially in areas where activity is low.

Next, if possible, choose a conversion scheme that will allow at least 15-20 dB of image rejection with simple filtering. If a low-frequency i-f is chosen (for example, 28 or 50 MHz), the rf filtering ahead of the first mixer will be more stringent, since the image frequency will be close to the rf frequency. This usually requires a narrow bandwidth filter, possibly with more than one pole. This type of bandpass filter is often more difficult to tune and may have higher insertion loss than a simple one-pole type.

Different i-f and LO (local oscillator) schemes are in use on the microwave bands, as discussed in reference 1. Nowadays a 2-meter i-f is most popular for the 23- and 13-cm bands. Therefore, an 1152- and 2160-MHz LO would be required for 1296- and 2304-MHz transverter operation, respectively, as shown in figs. 1A and 1B.

Interestingly enough, if you use these schemes, you can get on 3456 MHz almost for free. Simply mix the output of your 1296-MHz transmitter with the 2160-MHz LO and voila! you have 3456 MHz, as shown in **fig. 1C**. This is the scheme used by many of the operators now on 9 cm.<sup>3</sup>

If you use this scheme and a TVROtype (3.7-4.2 GHz) preamplifier, you get sufficient image and LO rejection for free. This is true because the image frequency is 864 MHz and the LO is 2160 MHz, well below the cutoff frequency of the waveguide typically used on TVRO-type preamplifiers.

Paul Shuch, N6TX, recently extended this technique to the 6- and 3-cm (10,368 MHz) bands.<sup>4</sup> His approach is more or less an offshoot of the 1152-MHz multiplier scheme described in reference 1.

Basically it goes like this. If you multiply the 1152-MHz LO three times and mix it with 2304 MHz, you get 5760 MHz (**fig. 1D**). Now if you also multiply the same 1152-MHz LO seven times and mix it with 2304 MHz, you get 10,368 MHz (**fig. 1E**).

Furthermore, if you don't care about the lower microwave bands, just multiply the 1152-MHz LO seven times and mix it with 2304 MHz. You'll get both 5760 and 10,368 MHz from a typical mixer. If an image rejection mixer is used, you'll have instant separation of the two desired outputs (**fig. 1F**).<sup>5</sup>

These conversion techniques all have their advantages and disadvantages, depending on the bands you want to work and the gear you have. If the frequencies specified in **table 4** are maintained, fewer LOs will be required to get on the microwave bands. This is significant because frequency instability is one of the biggest impediments to reliable microwave and millimeter-wave communications.

For over a decade 3-cm ("X" band) GunnPlexers have been in use. Various i-fs (such as 30, 50, and 88-108 MHz) have been used. The majority of stations in North America now seem to favor 30 MHz. The two most popular frequencies chosen for this scheme are 10,250 and 10,280 MHz, well away from the weak-signal calling frequency.


# mixer design

Anyone familiar with my designs is well aware of how much I favor the
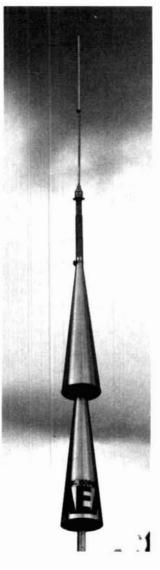
# Put More Punch in Your Packet

Outstanding mechanical design makes the IsoPole the only logical choice for a VHF base station, especially for Packet operation. All Isopole antennas yield the maximum gain attainable for their respective lengths and a maximum signal on the horizon. Exceptional decoupling from the feed line results in simple tuning and a significant reduction in TVI potential. The IsoPole antennas are all impedance matched in the factory so that no field tuning is required. The IsoPoles have the broadest frequency coverage of any comparable VHF base station antenna. This means no loss of power output from one end of the band to the other, when used with protected solid state SWR tranceivers. Typical SWR is 1.4 to 1 or better across the entire band.

A standard 50 Ohm SO-239 connector is recessed within the base sleeve (fully weather protected). With the IsoPole you will not experience aggravating deviation in SWR with changes in weather. The impedance matching network is weather sealed and designed for maximum legal power. The aerodynamic cones are the only appreciable wind load and are attached directly to the support (a standard TV mast which is not supplied).



## High Performance Hand-Held Antenna — The Hot Rod

The Hot Rod antenna can be expected to make the same improvement to hand-held communications that the IsoPole antennas have made to base station operation. Achieve 1 or 2 db gain over ANY 5/8 wave two meter telescopic antenna. The factory tuned HR-1 is 20% shorter, lighter and places far less stress on your handheld connector and case. It will easily handle over 25 watts of power, making it an excellent emergency base or mobile antenna. In the collapsed position, the Hot Rod antenna will perform like a helical quarter wave. Three Hot Rods are available; HR-1 1/2 wave 2M Ant., HR-2 for 220 Mhz, and HR-4 for 440 Mhz. Amateur Net Price on all Hot Rods is \$19.95.

For either base station or hand-held operation AEA has the perfect VHF/UHF antenna. Put more punch in your Packet station with an AEA IsoPole or Hot Rod antenna. To order your new antenna contact your favorite Amateur Radio Distributor. For more information contact Advanced Electronic Applications, P.O. Box C-2160, Lynnwood, WA 98036, or call 206-775-7373.

**IsoPole Specifications** 

Model Freq. Coverage (Mhz) 2.1 VSWR bandwidth Power Rating Gain\*\* Radiating Element Length Arnateur Net Price

144	220	440		
135-160	210-230	415-465		
)12Mhz @ 146Mhz	)15Mhz @ 220Mhz	)22Mhz @ 435Mhz		
1 kw	1 kw	1 kw		
3 dbd	3 dbd	3 dbd		
125.5" (3.2m)	79.25" (2m)	46" (1.2m)		
\$49.95	\$49.95	\$69.95		

\*\*dbd — db gain over a dipole in free space

r 149

Prices and Specifications subject to change without notice or obligation.



use of DBMs (double-balanced mixers) for up/down converters.<sup>6</sup> I feel even more strongly that, if available, they should be used in the microwave region. DBMs have fewer spurious outputs and usually are matched to 50 ohms at all ports, so they're easy to use with standard 50-ohm filters and amplifiers.

Many suppliers manufacture DBMs for the VHF/UHF bands, but the choices narrow as you go above 1 GHz, especially if price is any consideration — as it always is for us Amateurs! Once again, we're helped by the TVRO business, which has generated some reasonably priced DBMs that cover both the 9- and 13-cm bands.

Table 5 shows typical specificationsof some reasonably priced (less than\$100) DBMs that are usable through4.2 GHz. Be careful in your selection,because the upper limit of the i-f is notalways high enough for some of thehigher i-f conversion schemes just discussed.

Until moderately priced DBMs are available above 4.2 GHz, Amateurs will probably have to use single-balanced or single-ended mixers for the upper microwave and millimeter-wave bands. At 3 cm and above, waveguide mixers are readily available on the surplus market. Even some of the police radar detection mixers may be adaptable to Amateur operation.

Finally, don't overlook GaAsFETs as mixers. They may be more difficult to use than DBMs and may require additional filtering or tuning, but they can be much less expensive than DBMs. Single-gate GaAsFETs are usable, but the dual-gate types are a natural for mixers because the LO can be injected directly into the second gate. Furthermore, GaAsFET mixers often have conversion gain and hence require less follow on gain, an especially important consideration in transmitter applications.

## local oscillators

Local oscillators are a subject unto themselves. Many circuits have been published; the most successful ones used on the microwave bands have

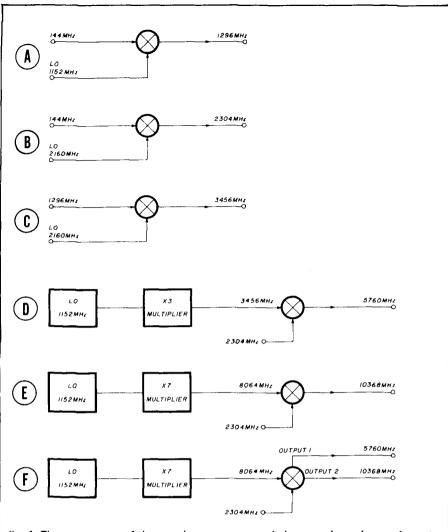


fig. 1. These are some of the popular or recommended conversion schemes for getting on the Amateur microwave bands. In all cases, the frequencies shown will place you near the most common operating frequencies listed in table 4. (See text for explanation of figs. 1A through 1F.)

been those that started with a fifth or seventh overtone crystal oscillator operating in the 90-125 MHz region followed by a transistor multiplier.<sup>5,6</sup>

Often a 96-MHz oscillator is multiplied 12 times to 1152 MHz as just discussed. Transistor or diode multipliers can be used if a high frequency (for example, 2160 MHz) is desired.<sup>7,8</sup> For the most critical applications, especially for the upper microwave and millimeter-wave bands, oven-stabilized oscillators may be preferred.

Recently several packaged oscillator/multipliers appeared on the surplus market; often they can be retuned to the Amateur bands. Some even use internal phase-locked oscillators. Several commercial sources are now available to the Amateur (more on this later), so I won't dwell on this subject at this time.

# low-noise preamplifiers

Only a decade ago receivers using crystal mixers in the front end were in common use. They still are used today in GunnPlexers. Receivers with a mixer as the first active stage frequently have noise figures of 8-10 dB or even higher!

If you want to take advantage of cw and SSB communications, you should design your receiver accordingly. Low noise figure preamplifiers and designs are now quite plentiful, especially since






TERMS ALL PRICES IN U.S. DOLLARS (...) SHIPPING & INSURANCE. CWO. VISA OR MC WELCOME INTRODUCTORY PACKAGE VALID FOR ORDERS PLACED BEFORE 31. JAN. 1987



35 Stroughton Crescent, → 150 Munster Hamlet, Ontario, Canada, K0A 3P0 (613) 838-5254


Dealer Inquiries Welcome



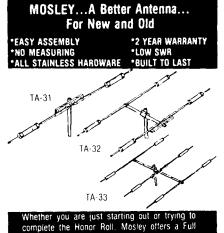

Line of Tr-Banders which will mechanically and electronically outperform the competition. For the new ham with limited space and pocket book, start with our TA-31 Jr. rotatable dipole. You can make our TA-31 Jr. into a 2 or 3 element as your needs increase

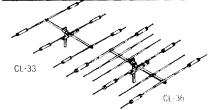If you start with the need to run higher power, then the TA-31 is for you. This also can be made into a 2 or 3 element beam as you expand your citation



For the ham that wants a little more performance out of a Tri-Bander but is limited in room, then our CL-33 on a 18 foot boom is the way to go. For those that want MONO BAND performance out of a Tri-Bander, want to hear better, and be louder, the CL-36-is for you.



For the ham that wants to start right at the top, the PRO-57 is the antenna that will give you king of the hill performance. It is the broadest banded, highest power, best performing Multi-Bander in our tine. PRO-57: (10, 12, 15, 18, 20) also available; PRO-67 (10, 12, 15, 18, 20 & 40)

Compare ours before buying any other antenna. All stainless standard, all heavy telescoping aluminum elements which means better quality and no measurement. Ease of assembly gives you a quality antenna with consistent performance. Our elements are pre-drilled so you will get the same performance as we do. All of our Tri-Banders come with a 2 year warranty.

If you are a new ham and are not familiar with MOSLEY, ask an older ham about us or call the PRESIDENT of MOSLEY. He will be glad to explain why MOSLEY is A BETTER ANTENNA.

These and other MOSLEY products are available through your favorite DEALER. Or write or call MOSLEY for the DEALER nearest you



 1344 BAUR BLVO
 ST. LOUIS.
 MISSOURI 63132

 1-314-994-7872
 1-800-325-4016

Table 5: Some recommended "standard level" (5 milliwatts LO) DBMs that will work on the microwave frequencies and cost less than \$100.00.

Part No.	Supplier	rf/LO freq GHz	i-f freq GHz	Conv.loss typ.dB	Price ea.	Notes
DBM-500	Vari-L Company	1.7-4.2	DC-1.5	7.5	95.00	w/SMA connectors
DBM-1120	Vari-L Company	1-2	DC-0.8	5	85.00	w/SMA connectors
PAM-42	Mini- Circuits	2-4.2	DC-1.3	7-8	26.95	module
SRA-5	Mini- Circuits	.05-1.5	DC-0.6	78	21.95	relay can
ZAM-42	Mini- Circuits	1.5-4.2	DC-0.5	78	39.95	w/SMA connectors
ZFM-4212	Mini Circuits	2-4.2	DC 1.3	7-8	39.95	w/SMA connectors

low-cost GaAsFETs became available.<sup>9</sup> Low-cost GaAsFETs can now yield noise figures under 2 dB through 25 GHz, which is more than sufficient for terrestrial communications!

TVRO preamplifiers without modifications seem to work quite well on the 9-cm Arnateur band and deliver 40-55 dB of gain with a typical noise figure of 1.5 dB. All they require is a waveguide-to-coax transition on the input and dc power applied directly to the unit or through the feedline if so configured. They're often available at flea markets for less than \$30!

# transmitter amplifiers

CW or SSB with narrow bandwidth i-fs and good frequency stability make microwave and millimeter-wave DX very feasible using low power (less than 1 watt), as discussed previously. The use of a low-level upconverter with a DBM is becoming very popular even in the microwave region.<sup>10</sup> The rf output power available from a "standard" level DBM is typically in the 10-100  $\mu$ watt region. Therefore, this approach normally requires 25-50 dB of gain to reach a reasonable transmitter output power level.

Inexpensive gain (at \$2-4 per device) is now readily attainable by the use of MMICs (monolithic microwave integrated circuits). Many devices are available up through at least 6 GHz, with output powers approaching 100 milliwatts.<sup>7,11</sup> The MMIC will probably be the workhorse for power levels below 100 milliwatts.

GaAsFETs are particularly attractive for transmitter applications since they're low in cost and have high gain. Even the small-signal types can usually deliver 10-100 milliwatts of output power.

Microwave class C power bipolar transistors and GaAsFETs — especially the "internally" matched types — are also usable, especially if only cw operation is contemplated. They are less costly than linear types with higher power levels (5 to 10 watts or more).

Linear types of bipolar and GaAs-FETs that can deliver 2 to 5 watts are also available. These devices are expensive (\$100 to \$300), but offer considerable performance and size advantages when compared to conventional power generation techniques. Prices of these devices are constantly dropping.

One of the real sleeper bargains is the TWT (Traveling Wave Tube). Expensive only if it's purchased new, it provides very high gain (typically 25-40 dB), usually over an octave of bandwidth into 50 ohms -- without external tuning! Two-to 4-GHz TWTs are quite common and cover two Amateur microwave bands for the price of one!

Available through 25 GHz and usually moderate in size (typically only 6 to 12 inches long), TWTs are generally linear amplifiers. Transmitter-type TWTs that deliver up to 100 watts of output power at 10 GHz are also available! TWTs do require several different voltages, often up to or above 1000 volts, with a positive ground. They can be used for portable operation if 115 VAC is available either locally or from a small gasoline generator or a dc-toac inverter.

Don't overlook receiver-type TWTs, which also have high gain and typically deliver 1-10 milliwatts of maximum output power, more than adequate for low-power operation. However, they're not recommended for front ends on receivers because they usually have 5-10 dB noise figures.

TWTs have been used in satellites and point-to-point microwave links for many years. However, the trend is to use solid-state amplifiers because they require only a few low voltages and are very compact. Furthermore, some of the TWTs used by telephone companies are being replaced by solid-stateamplifiers. As a result, TWTs are finding their way into the Amateur surplus market, especially for the 6- and 9-cm Amateur bands.

Below 3.5 GHz, the ubiquitous 2C39/7289 vacuum tube family is still usable. Twenty-five to 50 watts output per tube has been reported on 13 cm. Power klystrons that deliver hundreds of watts are also available for the microwave frequencies if you're fortunate enough to locate them, but that's another ball game.

## antennas and transmission lines

Antenna designs have also come a long way in recent years. The principal workhorse of the microwave bands is the parabolic dish, although the loop Yagi has been used as high as 10 GHz.<sup>12,13,14</sup>

The real bargains are the used or surplus UHF TV and TVRO dishes. Channel Master makes a 7-foot UHF TV dish which, when covered with proper screening, works well up through 13 cm.<sup>13,15</sup>

Feeding dishes isn't too complicated for terrestrial work. Two 3-pound coffee cans soldered together using a quarter-wave probe works well at 23 cm.<sup>15</sup> A similar arrangement using a one-pound coffee can will cover 13-cm<sup>15</sup> while a Campbell's soup can makes a good feed on 9 cm.<sup>7</sup>

Recently scalar feeds such as the TVRO "Chaparral"<sup>™</sup> type are being used. They seem to work well on the lower F/D (0.35-0.4) dishes.<sup>12,13</sup> When this feed is used on the larger diameter (6 foot minimum) dishes on the 9-cm Amateur band, the overall gain seems to be very near the expected value.

Feedlines are always a problem on the microwave bands. Low dielectric foam or air dielectric Heliax<sup>™</sup> used in the shortest possible length are recommended.<sup>16</sup> The popular trend on the microwave bands is to use antennamounted preamplifiers and to locate the transmitter as close to the antenna feed as possible. This is increasingly more feasible when solid-state devices are used in the transmitter. Low-loss waveguide feedline is recommended on 10 GHz and above.

#### commercial gear

As previously mentioned, there are now commercial converters, transverters, and LOs available for all the Amateur bands through 13 cm. SSB Electronics uses a very interesting packaging concept. Each of their subsystems is a separate module. For instance, for a transverter you buy a separate LO with dual outputs, receive downconverter, and transmit upconverter. The LO for a 13-cm setup is a compact unit that puts out a stable 3-5 milliwatts of power at 2160 MHz for about \$100. This unit can be adapted to the 9-cm scheme mentioned earlier.

Recently SSB Electronics announced a 3-cm (10,368 MHz) transverter that sports a 2.5-dB maximum receiver noise figure and over 150 milliwatts of output on CW or SSB. A 144-MHz i-f is used. The filtering required is obtained by the use of several dielectric resonators that have very high Q and low insertion loss. At less than \$500 for the basic transverter, this should be a natural for weak-signal "X" band enthusiasts.

\*Transverters Unlimited, Hans Peters, VE3CRU, Box 6286 Station A, Toronto, Ontario, Canada M5W 1P3.

#### propagation

This subject was discussed in detail earlier.<sup>2.17</sup> It's quite obvious from the details already discussed on new North American DX records that the microwave and millimeter-wave Amateur enthusiasts are taking advantage of many of the radio propagation opportunities available to them. Once again this proves that these are very worthwhile frequencies, quite capable of supporting radio propagation well beyond the line of sight!

#### summary

This month's column was primarily aimed at updating all the recent happenings on the microwave and millimeter-wave bands and in particular the recent record breaking DX contacts. It's great to see such activity and advancement of the state of the art.

Some of the latest techniques and devices that are presently being used were also discussed. It's good to see that Amateurs are really taking advantage of the new low- to moderatelypriced solid-state devices, and nice to see Amateurs benefit from the UHF and TVRO businesses. It's no longer very difficult to build or operate gear on our highest Amateur bands.

#### Important VHF/UHF Events:

•	
January 3:	Predicted peak of the Quad- rantids Meteor Shower at
	1830 UTC.
January 10-12:	ARRL VHF Sweepstakes
	Contest
January 28:	EME perigee
February 25:	EME perigee

#### references

1. Joe Reisert, W1JR, "VHF/UHF World: Amateur Microwave Bands," *ham radio*, January, 1986, page 44.


2. Joe Reisert, W1JR, "VHF/UHF World: Microwave and Millimeter-Wave Propagation: Part 1", *ham radio*, July, 1986, page 82.

3. Rick Fogle, WA5TNY, "3456 MHz Operation," Proceedings of the 1986 Central States VHF Conference, St. Louis, Missouri, July, 1986.

4. Paul Shuch, N6TX, "A Five-Band Microwave Transverter," *Proceedings of the Microwave Update 86 Conference*, Estes Park, Colorado, August, 1986.

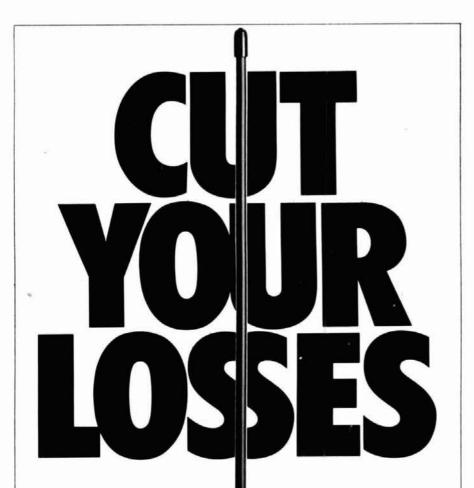5. Joe Reisert, W1JR, "Getting Started on 13 and 23 cm", *Proceedings of the 1985 1296/2304 MHz Conference, Estes Park, Colorado, September, 1985.* 6. Joe Reisert, W1JR, "VHF/UHF World: VHF/UHF

 Joe Reisert, WIJR, "VHF/UHF World: VHF/UHF Receivers," harn radio, March, 1984, page 42.
 Al Ward, WB5LUA, "MMIC Update/Cascading



Portable radios can be a trade-off. In return for mobility you get loss of performance.

Well now you can cut your losses significantly. All you need is the new Larsen UHF KūLDUCKIE<sup>®</sup> KD14-HW half-wave antenna\* It's a mouthful but it'll do your ears a lot of good.

Because it's half-wave, the KD14-HW is fully resonant despite the poor ground plane portables are faced with. Under ideal ground plane conditions, it delivers performance equal to a full quarter-wave. And that's a powerful improvement over most portable antennas! And because it is inherently resonant, the KD14-HW can also be easily remoted with a length of coax.

The KD14's flexible, easyto-get-along-with radiating element measures a scant 12 inches. At the base is a 3<sup>1</sup>/<sub>4</sub> inch impedance transformer that gives added strength.

The KD14 half-wave series is also available in a collapsable 2-meter version.

Cut your losses and improve your gain when you operate with the new Larsen UHF KūLDUCKIE<sup>®</sup> KD14-HW, with no-nonsense warranty. You can see it at your favorite amateur dealer.

\*For units with BNC output.



See your favorite amateur dealer or write for a free amateur catalog. IN USA: Larsen Electronics, Inc. /11611 N.E. 50th Ave. /P.O. Box 1799 / Vancouver, WA 98668/206-573-2722 IN CANADA: Canadian Larsen Electronics, Ltd. /149 West 6th Ave. / Vancouver, B.C. VSY 1K3/604-872-8517

LARSEN\* KúLROD\* AND KÚLDUCKIE\* ARE REGISTERED TRADEMARKS OF LARSEN ELECTRONICS. INC

MMIC's," Proceedings of the Microwave Update 86 Conference, Estes Park, Colorado, August, 1986.

 Richard L. Campbell, KK7B, "A Clean Microwave Local Oscillator," *Proceedings of the 1985 1296/2304 MHz Conference*, Estes Park, Colorado, August, 1985.
 Joe Reisert, W1JR, "VHF/UHF World: Low-Noise GaAsFET Technology," *ham radio*, December, 1984, page 99.

10. Joe Reisert, W1JR, "VHF/UHF World: VHF/UHF Exciters," ham radio, April, 1984, page 84.

11. Joe Reisert, W1JR, "VHF/UHF World: Broadband Amplifiers in Receiver Design," *ham radio*, November, 1986, page 91.

 Joe Reisert, W1JR, "VHF/UHF World: Reflector Antennas — Part 1," ham radio, February, 1986, page 51.

 Joe Reisert, W1JR, "VHF/UHF World: Reflector Antennas — Part 2," *ham radio*, March, 1986, page 68.
 Joe Reisert, W1JR, "VHF/UHF World: Designing and Building Loop Yagis," *ham radio*, September, 1986, page 56.

 Gerald Handley, WA5DBY, "The Care and Feeding of a 7-Foot Dish," *Proceedings of the 1985 1296/2304 MHz Conference*, Estes Park, Colorado.
 Joe Reisert, W1JR, "VHF/UHF World: Transmission Lines," *ham radio*, October, 1986, page 83.

 Joe Reisert, W1JR, "VHF/UHF World: Microwave and Millimeter-Wave Propagation — Part 2, ham radio, August, 1986, page 69.

ham radio

#### NE5205 wideband amplifier

There is an error in Mike Gruchalla's article, "NE5205 Wideband Amplifier" (September, 1986, page 30). In the last few sentences of the section on performance (page 38), the 20-dB return loss is stated as being related to an impedance within 0.5 ohm of 50 ohms. This is incorrect. The port-one impedance  $Z_1$  is given in terms of the S-parameter  $S_{11}$  by:

$$Z_{I} = Z_{0} \frac{(l+S_{II})}{(l-S_{II})}$$

The display of S11 in dB indicates the magnitude of the ratio of the reflected power from and the incident power to port 1. That ratio is equal to the magnitude of S11 squared. A 20-dB return loss is a power ratio of 1/100, which implies that the magnitude of S11 is 0.1. The two value extremes that will result in real (i.e., non-complex) values for load impedance are +0.1 and – 0.1. Using the equation above and a 50-ohm characteristic impedance, the impedance corresponding to a return loss of 20 dB could be as high as 1.22 Z<sub>0</sub>, or 61 ohms, and as low as 0.82 Z<sub>0</sub>, or 41 ohms. So, the 20-dB return loss represents a port impedance within about 10 ohms of 50 ohms, and not 0.5 ohms as stated in the article. (TNX W3NQN - Ed.)



- 160

## a deluxe logic probe

## Accurate logic probe detects high frequencies and pulses

Plenty of good logic probe circuits have already been described in print. Unfortunately, a review of their schematics shows that each lacks something either speed, accuracy, flexibility, or protective devices. Increasing use of microprocessors, PLL synthesizers and digital signal processing circuitry makes the need for an improved probe obvious.

The logic probe shown in **fig. 1** represents an attempt to overcome problems with existing circuits and produce a device which is simple in design and easy to construct, yet powerful and inexpensive.

#### circuit description

To protect the probe from an accidental reverse voltage connection, a diode is included in series with the power supply (**fig. 2**). The 1N270, a germanium diode, has a lower forward voltage drop than a silicon diode and has a peak reverse breakdown voltage of

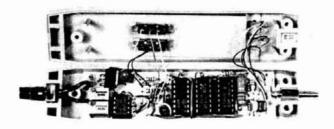



fig. 1. Deluxe logic probe.

about 100 volts. The LM330T-5.0 is a low-voltage dropout voltage regulator which provides a regulated 5.0 volts output with an input as low as 5.6 volts.1 In addition, this regulator has an approximately linear voltage output drop as the input supply voltage falls below 5.6 volts. For instance, with this device connected to a 5-volt TTL supply, its output would still be approximately 4.3 volts. The combined effects of the diode and voltage regulator are such that when the probe is connected to any supply above 6.0 volts (CMOS) the regulated output voltage V<sub>REG</sub> will be 5.0 volts. When the probe is connected to any TTL supply, the voltage at V<sub>REG</sub> will be about 4 volts, which is acceptable. In fact, I've found that the probe still works with an input supply voltage down around 4 volts. The 60-µF capacitor is necessary for proper requlation and should be a tantalum.

To protect the input from accidental negative or high voltage, I've used a technique similar to that used to protect CMOS gate inputs. The 2.2 k (3 watt) resistor provides current limiting when either the lower 1N914 diode conducts (negative input) or when the top 1N914 diode conducts (positive input greater than supply). The 0.068- $\mu$ F ceramic capacitor provides an ac bypass for pulses.

To allow high-speed pulse detection, I've separated the pulse and level detection functions. This was necessary because most comparators have a response time far below that of most modern logic operating frequencies and therefore would reduce or miss high frequency pulses.<sup>2</sup> At the input, a 100-pF ceramic capacitor couples pulse signals into an MC74HC04 CMOS inverter.<sup>3</sup> The MC74HC04 is a HEX high-speed CMOS inverter which has an operating speed similar to that of LSTTL. In addition to low power consumption typical of CMOS, this device can be powered from

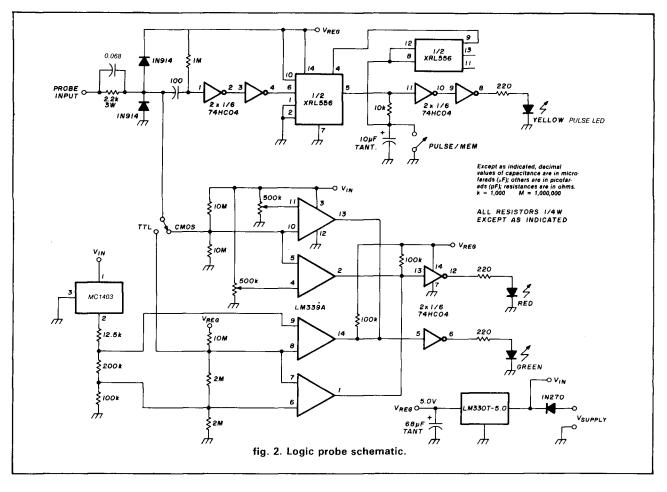M. Wilde, 7708-181 Street, Edmonton, Alberta, Canada T5T-127



a wide range of supply voltages — 2 to 6 volts. This is useful because of the approximately 1-volt drop across the probe power supply. The 1-megohm resistor connected from the input to  $V_{REG}$  is a pullup resistor used to prevent the CMOS input from floating and erroneously triggering. The incoming pulses are put through two inverters which buffer the original pulse and square up the waveshape.

The pulse trigger and display use an XRL556 dual timer.<sup>4</sup> The first timer is a negative edge-triggered Set/Reset flip-flop, and the second a comparator/flipflop. When a negative edge first appears at the input of timer 1 (pin 6), a flip-flop is set and its output goes high. This causes the pulse LED to turn on and the  $10-\mu F$  capacitor to begin charging toward the supply voltage. When the voltage on this capacitor reaches 0.66 V<sub>REG</sub>, the second timer turns on, resetting the flip-flop in timer 1. Now the pulse LED is turned off, and the  $10-\mu F$  capacitor begins to discharge toward ground. The flip-flop in timer 1 remains reset until the decreasing voltage on the capacitor reaches 0.33 V<sub>REG</sub>. At this point, timer 2's output goes low and timer 1 is ready for retriggering. Two timers provide a fixed on and off time, which will cause the pulse LED to flash on and off (at about 1 Hz) when repetitively triggered, thereby providing a pulsing display for a


pulsing input. By shorting out the  $10-\mu$ F capacitor, timer 2 is never allowed to reset timer 1, which provides memory.

#### logic level detection


Logic level detection is accomplished by two separate window detectors with their outputs ORed together. A National Semiconductor LM339 quad, single-supply comparator, which has open collector outputs is used.<sup>5</sup>

Two 500-k, 10-turn trim pots set to 70 percent and 30 percent of the supply voltage are used to set the CMOS thresholds. Using a 10-turn pot allows an accurate and stable setting, with the possibility of resetting these ranges to, say, 80 percent and 20 percent if it's ever necessary to detect a narrower range. Two 10-megohm resistors in series from the supply to ground hold the CMOS window comparator input to 0.5 volts  $V_{IN}$ . This keeps the logic level output LEDs 'off when there's no input signal. Large value resistances were chosen to reduce power consumption and provide a high input impedance.

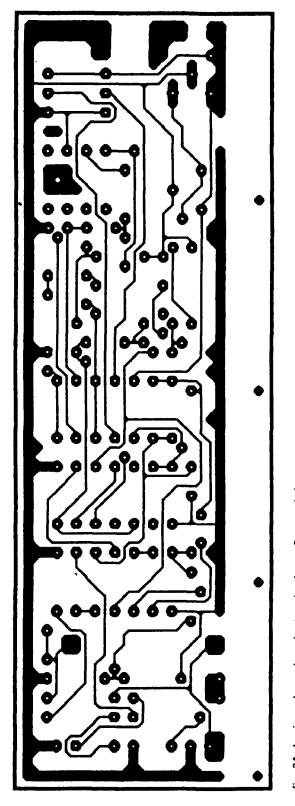
For the TTL window detector, I used the combination of a 10-megohm resistor and two 2-megohm resistors to keep this window input at a nominal 1.1 volts (remember the approximate 1-volt drop across the





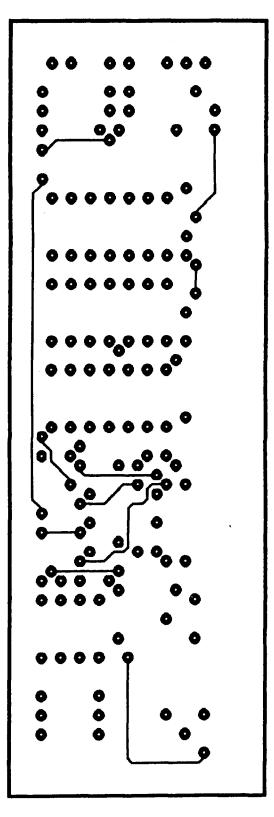



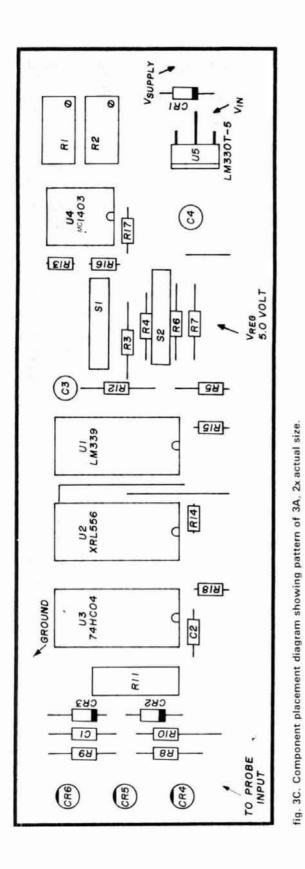

C1	0.068 µF ceramic chip		
C2	100 pF ceramic		
C3	10 µF tantalum, 10 volts		
C4	68 µF tantalum, 16 volts		
CR1	IN270		
CR2,3	IN914		
CR4	LED Miniature Green		
CR5	LED Miniature Yellow		
CR6	LED Miniature Red		
R1, R2	500 k, 10-turn (poten-		
	tiometer)		
R3, R4, R5	10-Megohm, 1/4-watt		
R6, R7	2-Megohm, 1/4-watt		
R8, R9, R10	220-ohm, 1/4-watt		
R11	2.2 k, 3-watt		
R12	10-k, 1/4-watt		
R13, R14, R15	100-k, 1%, 1/4-watt		
R16	200-k, 1%		
R17	12.4-k, 1%		
R18	1-Megohm		
S1, S2	Miniature slide switch		
U1	LM339N		
U2	XRL556CP		
U3	SN74HC04N		
U4	LM 1403		
U5	LM 330T-5.0		

supply). The logic thresholds themselves are set by a voltage divider network connected to an MC1403 precision voltage reference IC.<sup>6</sup> The MC1403 provides a stable temperature-compensated 2.5 volts output and operates at a supply voltage range of 4.5 to 40 volts. Because of this lower voltage limit, this device must be connected to V<sub>IN</sub> and not V<sub>REG</sub>, because the additional 0.6 volt drop would be too much. The resistor combination shown in **fig. 2** provides 0.8- and 2.4-volt references for the TTL window detector.

#### calibration and assembly


The only calibration required for this probe is to set the CMOS logic levels on the multi-turn pots. This is easily done by connecting the probe to a 10-volt supply and adjusting the pots until they provide 7 volts and 3 volts at pins 11 and 4, respectively, of the LM339.

I've tried to measure the maximum frequency and minimum pulse width this probe is capable of detecting, but the probe is capable of detecting higher speed pulses than my test equipment will provide. With my test equipment I've found that the probe will at least work up to 20 MHz (square wave input) and detect pulses as narrow as 20 nanoseconds. This is sufficient for most work currently being done, but still isn't the limit of the probe.

The slow response time of the comparators (LM339) results in the green and red LEDs turning on and a

## ALL NE DUAL BAND ANTENNAS FOR ULTIMATE PERFORMANCE!!

Model	Description		Sug. List
2X4Z	Base/Repeater 200	) Watt	\$168.95
Gain 14	6 MHz 8.2dB, 446 MHz 11	.5dB	
2X4SR	Mobile with Mag. M	t. 150 Watt	71.90
Gain 14	6 MHx 3.8dB, 446 MHz 6.	2dB	
2X4SDY	Mobile with Mag. M	t. 100 Watt	65.95
Gain 14	6 MHz 2.15 dB, 446 MHz	3.8dB	
HT 702	146/446 MHz Hand	d Held BNC 50 Watt	29.95
C7-71	Base/Repeater 920	0 MHz	\$115.95
	50 Watt 7.14 dB Ga	ain ,	
C202N	Mobile 920 MHz wi	th Mag. Mt.	72.95
	5 dB Gain 50 Watt		
1234E	Base/Repeater 200	0 Watt	\$178.95
Gain 44	6 MHz 8.5dB, 1.2 GHz 10.	1dB	
124X	Mobile with Mag. M	t. 100 Watt	104.95
Gain 44	6 MHz 2.5dB, 1.2 GHz 3.5	dB	
1221S	1.2 GHz Base/Repe	eater 100 Watt	\$158.95
Gain 15	5dB, 21 Step colinear		
1210M	1.2 GHz Mobile with	h Mag. Mt. 50 Watt	76.95
Gain 8.8	8dB		
415M	High power duplexe	er 146 MHz 400 Watt	59.95
	446 MHz 250 Watt		
412N	UHF/GHz Duplexer	446/1400MHz	68.95
	Max. 70 Watt		
NG.4 00	1275 NORTH GROVE ST.		- 161
	ANAHEIM, CALIF. 92806		ces may be
NCG	(714) 630-4541 CABLE: NATCOLGLZ	diritire	nt than list.
$\langle - \rangle$	FAX (714) 630-7024	Prices and specifications change without notice or	

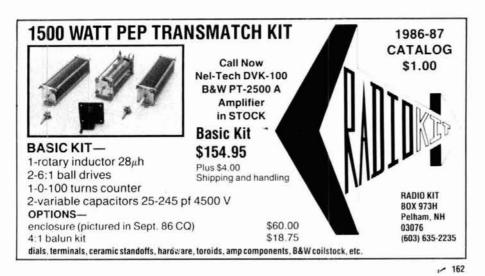



			-9913	
			EN CABL	
Belden #	Mil.#	500° Roll		99° & down
9913	RG-8	\$185		. 319
8267	RG-213	195	49	.40)
8214	RC+8	149	3.4	35
8237	RG-8	145	_\$2	_3-4
0.258	RC, 8X	80	17	.17
Ampheno	l connect	OFS:		
UG-21D		e cable en	d	3.00
UG-21D	'Fitted I	or Belden	9913	4,50
UG-29A		rel connec		4.75
UG-58A		ale chassi		3,50
UG-146		to UHF ja		7.50
UG-83		to UHF p		8.50
PL-259		ale cable e		2.00
PL-258 UG-260B		ug for Mini		3.60
UG-625B		nel recept		1.35
			wire 28¢/	ít.
COMP Seth Reg. price	Vibro MFJ an LETE ST Thomas	plex Key tenna Tu OCK, SA 13" 24-1	Now on	c. HIPPING n Clock



flashing pulse LED for square wave inputs under about 2 MHz. For square waves over about 5 MHz, however, the green and red LEDs will be off (because of the slow comparators), but the pulse LED will still flash. Although I initially thought this was a shortcoming, others have suggested that this is actually useful because it provides a rough indication of speed. The probe will indicate a true pulse and logic level condition for all narrow pulses because one logic level is present for most of the time.

The pc board, which measures approximately 1 x 4 inches, fits nicely into a logic probe case available from Global Specialties.\* The case comes with a probe tip and power cord, but the holes for the switches have to be drilled and a label made (if desired). The proto-type used sockets for all ICs; this causes some height problems, however, and I recommend leaving them out.

The pc board artwork is reproduced in fig. 3A. Figure 3B illustrates the reverse side (component side) hole diagram as well as a computer-generated jumper placement. Point-to-point wiring is recommended for this side. Figure 3C details component placement using the same pattern shown in fig. 3A.

#### references

- 1 LM33OT 5.0 data sheet, National Semiconductors.
- 2. J. Rozenthal, "Improved Logic Probe," ham radio, April, 1983, page 91
- 3 SN74HC04N data sheet, Motorola
- 4. XRL556CP data sheet, EXAR
- 5. LM339N data sheet, National Semiconductors
- 6. LM1403 data sheet, Motorola.

\*Global Specialities, Inc., 70 Fulton Terrace, P.O. Box 1942, New Haven, Connecticut 06509.

ham radio





A monthly of 100-plus pages—has everything you need to know about where to find equipment, how to install it, system performance, legal viewpoints, and industry insights! With your subscription to STV\* you will receive a FREE LCD Calendar/Clock.

Only \$19.95 per year (12 monthly issues)
\$1.00 for sample copy



The best in satellite programming! Featuring: ★All Scheduled Channels ★Weekly Updated Listings ★Magazine Format ★Complete Movie Listing ★All Sports Specials ★Prime Time Highlights ★Specials Listing and ★Programming Updates!

- Only \$45.00 per year (52 weekly issues)
- 2 Years \$79.00 (104 weekly issues)
- \$1.00 for sample copy

Visa<sup>®</sup> and MasterCard<sup>®</sup> accepted (subscription orders only). All prices in US funds. Write for foreign rates.

Send this ad along with your order to:

#### STV®/OnSat®

P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384 SUBSCRIPTION CALLS ONLY TOLL FREE 1-800-438-2020

## CORPORATION


9 Autry Irvine, CA 92718 (714) 458-7277 Canadian Distributor Eastcom Industries, Ltd. 430 Signet Drive Weston, Ont. Can 49L 2T6 (416) 743-7801

	ASTRON POWER SUPPLIES • HEAVY DUTY • HIGH QUALITY • RUGGED • RELIABLE •				
INSIDE VIEW – RS-12A	<ul> <li>FOLD-BACK CUR from excessive ci</li> <li>CROWBAR OVER except RS-4A.</li> <li>MAINTAIN REGU input Voltage.</li> <li>HEAVY DUTY HE</li> <li>THREE CONDUCT</li> </ul>	RES ECTRONICALLY REGULATE RENT LIMITING Protects P urrent & continuous shorted VOLTAGE PROTECTION on LATION & LOW RIPPLE at AT SINK • CHASSIS MOU	ower Supply d output. all Models low line	PERFORMANCE SPECIFIC • INPUT VOLTAGE: 105 - 12 • OUTPUT VOLTAGE: 13.8 V (Internally Adjustable: 11- • RIPPLE: Less than 5mv per & low line)	25 VAC VDC ± 0.05 volts 15 VDC)
Autrest data		EL RS-50M		MODEL VS-5	
	Constant of the second s	MOUNT POWER SUPPLIES		MUDEL V3-3	
RM-A Series	Model RM-35A RM-50A	Continuous Duty (AMPS) 25 37 It and Amp Meters 25	ICS* (AMPS) 35 50 35	Size (IN) HXWXD 51/4 × 19 × 121/2 51/4 × 19 × 121/2 51/4 × 19 × 121/2	Shipping Wt. (lbs.) 38 50 38
MODEL RM-35A	RM-50M	37	50	$5\%$ $\times$ 19 $\times$ 12½	50
RS-A SERIES		Continuous	ICS*	Size (IN)	Shipping
IIS-A SEIIES	MODEL	Duty (Amps)	(Amps)	HxWXD	Wt (lbs)
MODEL RS-7A	RS-4A RS-7A RS-7B RS-10A RS-12A RS-20A RS-35A RS-50A	3 5 7.5 9 16 25 37	4 7 10 12 20 35 50	$\begin{array}{c} 3\frac{3}{4} \times 6\frac{1}{2} \times 9 \\ 3\frac{3}{4} \times 6\frac{1}{2} \times 9 \\ 4 \times 7\frac{1}{2} \times 10\frac{3}{4} \\ 4 \times 7\frac{1}{2} \times 10\frac{3}{4} \\ 4\frac{1}{2} \times 8 \times 9 \\ 5 \times 9 \times 10\frac{1}{2} \\ 5 \times 11 \times 11 \\ 6 \times 13\frac{3}{4} \times 11 \end{array}$	5 9 10 11 13 18 27 46
RS-M SERIES					
MODEL RS-35M	Switchable volt a     MODEL     RS-12M     RS-20M     RS-35M     RS-50M	nd Amp meter Continuous Duty (Amps) 9 16 25 37	ICS* (Amps) 12 20 35 50	Size (IN) H x W x D 4 <sup>1</sup> / <sub>2</sub> x 8 x 9 5 x 9 x 10 <sup>1</sup> / <sub>2</sub> 5 x 11 x 11 6 x 13 <sup>3</sup> / <sub>4</sub> x 11	Shipping Wt (lbs) 13 18 27 46
VS-M SERIES		nd Amp Meters adjustable from 2-15 voli ustable from 1.5 amps t Continuous Duty (Amps) @13.8v0C@10V0C@5V0C 16 9 4 25 15 7 37 22 10		Size (IN) H x W x D 5 x 9 x 10 ½ 5 x 11 x 11 6 x 13 ¼ x 11	Shipping Wt (lbs) 20 29 46
RS-S SERIES	Built in speaker				
MODEL RS-12S	MODEL RS-7S RS-10S RS-10L(For RS-12S RS-20S	Continous Duty (Amps) 5 7.5 LTR) 7.5 9 16	ICS* Amps 7 10 10 12 20	Size (IN) H x W x D 4 x 7% x 10% 4 x 7% x 10% 4 x 7% x 10% 4 - 9 - 13 4% x 8 x 9 5 x 9 x 10%	Shipping Wt (Ibs) 10 12 13 13 13 18
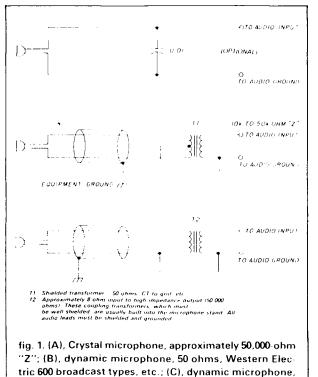
## modifying microphones

Adapt yesterday's microphones for use with modern rigs

Although modern transceivers are designed to accommodate low-Z, hand-held microphones, some of us prefer desk-type units to handhelds. We'd like to use a prized older microphone but know it just won't match the new transceiver. Older microphones *can* be modified, however; this article describes some simple modifications and a special preamplifier that may be added if necessary.



8-500 ohms, into 10,000 to 50,000 ohm "Z."

Most modern rigs use low-Z impedance microphones, usually around 500 ohms. Because you can run a lower-Z unit into a higher Z-input and lose only gain, it isn't necessary to "match" the impedance, provided you have adequate microphone gain. No changes are necessary unless you want to use, for ex ample, a Western Electric 50-ohm broadcast micro phone with a 430S. In this sort of arrangement, it would be necessary to use a matching step-up trans former as shown in **fig. 1**.

Other low-Z microphones may also be used in this manner. Some manufacturers enclose the transformer and the 50- kilohm microphone in the same unit. Un der these circumstances, the transformer must be magnetically shielded and preferably located in the base of the microphone stand. I found this system satisfactory for rigs that have adequate microphone gain; others may require an additional outboard preamplifier. Some manufacturers provide such units. As a rule, though, lower-output microphones are a better choice.

Crystal microphones can be used only into a high impedance input of 50 kilohms or more. An Astatic D104, for example, may be shunted at the microphone terminals with a  $0.01\mu$ F capacitor to equalize the audio output.


Condenser Electret microphones (CEM), widely used by ICOM and other manufacturers, usually employ a transistor preamplifier built into the microphone capsule. This requires that preamplifier power be supplied. Generally a small battery is incorporated into the base of the stand, or, as in the Radio Shack 33-1058 tie clip that I use, a built in mercury cell is incorporated within the microphone case. No on/off switch is required because the life of the battery is equal to its shelf life. The IC-HM12, for example, obtains its preamp voltage from the transmitter (eg., IC 735, 745, 751), via the same terminal (No. 1) that carries the audio from the preamp. (See **figs 2 and 3**.)

The output impedance of these units is 600 ohms, at a level above that of an unamplified dynamic micro

**By A.G. Sheffield**, **VE7CB**/**W6**, Tri-Palms Es tates, 32-291 Merion Drive, Thousand Palms, California 92276



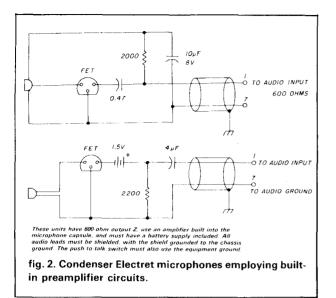
phone. It should be noted that equipment designed for CEM microphone inputs will not have sufficient gain unless a preamplifier is added. Using the RS




33-1058 capsule, the circuit shown in **fig. 3** is more than adequate.
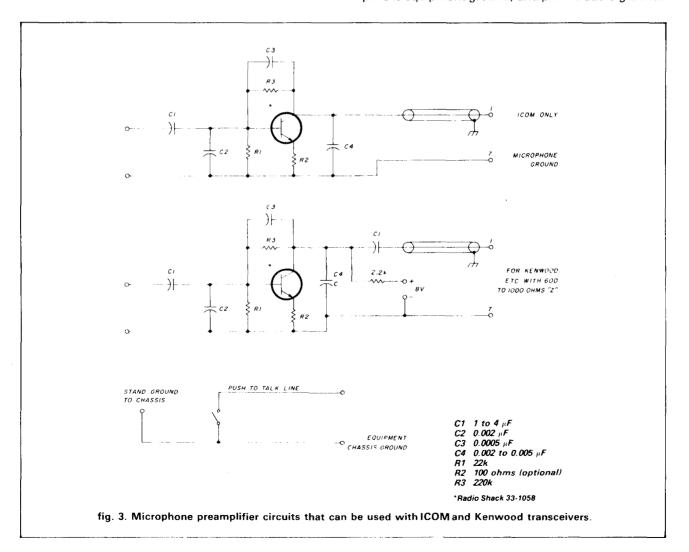
#### providing more gain

The preamplifier was constructed on a 1 X 2-inch piece of insulating board, with holes punched through for each component lead. It was wired directly into the microphone output and transceiver input via the microphone cord, directly from the base of the desk unit. (Note that the preamp termination must match vour rig's input Z. Also, if a common audio and voltage line isn't used — as in the ICOM series — a battery for the preamp will be necessary.) Matching to 600 ohms is enhanced by using a larger transistor than normal and operating it at a lower level. I have used a 2N3053, 2N1304, 2N2430 satisfactorily in this application, with no hiss or distortion noticeable at full gain. It's very important that the audio line to the microphone plug be an insulated shielded wire and that the microphone and preamp ground be kept insulated and separate from the chassis ground. Pin 1 is audio, pin 8 is equipment ground, and pin 7 is audio ground.


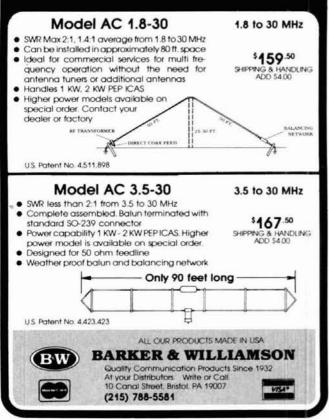
#### CONTINUOUS COVERAGE ANTENNAS FOR COMMERCIAL & AMATEUR SERVICE



This grounding method is essential in order to prevent hum and RF feedback. I wrap the microphone capsule with clear plastic tape to insulate it from the stand clamp. There should be no continuity path between the capsule and microphone stand; if there is, severe RF feedback will be evident.

For operation on SSB, it's especially important that the frequency response from 300 to 3000 Hz be flat and free of spurious peaks. Speech limiters and processing will level off these peaks somewhat, but it's at this point that the distortion inherent in such designs becomes apparent. Clipping produces square waves and harmonics within the audio range and is therefore not desirable. Response can be tailored to suit by reducing C1 for less bass and increasing the value of C2 for less highs. If full gain is required, remove emitter resistor R3. In my case, with the 745, the microphone gain is equal to the HM12's with the resistor left in. It is higher, but still within usable limits with the resitor out.

This low-cost, conventional design is the result of many hours testing different microphones and preamplifiers. Through its use, increased operating comfort — plus good voice quality and clean audio, with no spurs or splatter — can be achieved.

ham radio



been updated with plenty of exciting new projects, new theory and information chapters and the latest in state-of-the-art technology. Check out these new features: Passive LC filter design including standard value capacitor tables, overview of 23cm FM fast scan tv weather satellites basics, a complete

revision of the radio frequencies and transmission section (chapter 22) and satellite communications section (chapter 23). Some of the exciting new projects are: a new hf legal limit, all band amplifier using the 8877 tube, a dedicated CRT for Wefax image display and a new marker generator project for general use to name just a select few. Over 200 pages have been revised and updated. Great reference book that should be in every Ham's shack. Order your's today! Over 1100 pages. © 1986

AR-HB87 AR-BB87



Softbound \$17.95 Hardbound \$26.95

Please enclose \$3.50 to cover shipping and handling BOOKSTORE Greenville, NH 03048

## ham **radio** Reader Service

For literature or more information, locate the Reader Service number at the bottom of the ad, circle the appropriate number on this card, affix postage and send to us. We'll hustle your name and address to the companies you're interested in.

 101
 113
 125
 137
 149
 161
 173
 185
 197
 209
 221
 233
 245
 257
 269
 281
 293
 305
 317
 329
 341

 102
 114
 126
 138
 150
 162
 174
 186
 198
 210
 222
 234
 246
 258
 270
 282
 294
 306
 318
 330
 342

 103
 115
 127
 139
 151
 163
 175
 187
 199
 211
 223
 235
 247
 259
 271
 283
 295
 307
 319
 331
 343

 104
 116
 128
 140
 152
 164
 176
 188
 200
 212
 224
 236
 248
 260
 272
 284
 296
 308
 320
 332
 344

 105
 117
 129
 141
 153
 165
 177
 189
 201
 213
 225
 237
 249
 261
 273
 285
 297
 309
 3

Limit of 15 inquiries per request.

NAME	CALL		
ADDRESS			
CITY	STATE	ZIP	
Please use before April 30, 1987		March 1987	7

AFFIX POSTAGE
OR
POST OFFICE
WILL NOT
DELIVER

## ham **radio**


magazine

READER SERVICE CENTER P.O. BOX 2558 WOBURN, MA 01888

ATTN: Reader Service Dept.

# Expanding Our Horizons

## Introducing Mirage/KLM 1.2-44 LBX

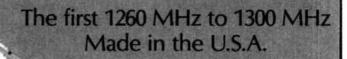

Factory Tested

- Completely Assembled
- Completely Weatherized Balun
- Also Available Soon . . .
  - **Power Dividers**

#### **SPECIFICATIONS**

#### Electrical

- Band Width ..... 1260–1300 MHz
- Gain ...... 18.2
- VSWR ..... Better than 1.5 to 1
- Feed Imp...... 50 Ohms
- Balun ...... 4:1 Rigid Coax

#### Mechanical

#### Mirage Communications Equipment, Inc. P.O. Box 1000 Morgan Hill, CA 95037 (408) 779-7363

#### THE MOST AFFORDABLE REPEATER ALSO HAS THE MOST IMPRESSIVE PERFORMANCE FEATURES (AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

WIRED BAND KIT \$630 \$880 6M, 2M, 220 \$730 \$980 440

(Also available for commer-



#### **FEATURES:**

cial bands)

- SENSITIVITY SECOND TO NONE; 0.15 uV (VHF), 0.2 uV (UHF) TYP.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE XTAL FILTER & CERAMIC FILTER FOR > 100 dBAT ± 12KHZ. HELICAL RESON-ATOR FRONT ENDS TO FIGHT DESENSE & INTERMOD.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMIT-TERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).

#### **RECEIVING CONVERTERS**

Models to cover every practical rf & if range to listen to SSB, FM.ATV.etc. NF = 2dBorless.

		Antenna Input Range	Receiver Output
	198	28-32	144-148
A PRICE AND A RECEIVING O	ONVERTER	50-52	28-30
	***	50-54	144-148
. <b>.</b> .	S	144-146	28-30
		145-147	28-30
		144-144.4	27-27.4
-		146-148	28-30
VHF MODELS		220-222	28-30
VIIF MODELS		220-224	144-148
Kit with Case	\$49	222-226	144-148
	\$39	220-224	50-54
Less Case	•	222-224	28-30
Wired	\$69		
UHF MODELS			
		432-434	28-30 28-30
Kit with Case	\$59	435-437	
Less Case	\$49	432-436	144-148
Wined	\$75	432-436	50-54
	<i><b></b></i>	439.25 902-928	61.25 422-448

SCANNER CONVERTERS Copy 806 MHz band on any scanner. Wired/tested ONLY \$88.

#### TRANSMIT CONVERTERS

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.


For VHF.	Exciter Input Range	Antenna Output
,	28-30	144-146
Model XV2	28-29	145-146
Kit \$79	28-30	50-52
	27-27.4	144-144.4
Wired \$149	28-30	220-222
(Specify band)	50-54	220-224
(Specity band)	144-146	50-52
	144-146	28-30
For UHF.	28-30	432-434
Model XV4	28-30	435-437
	61.25	439.25
Kit \$79	144-148	432-436*
Wired \$139	*Add\$	20 for 2M input

VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models. kits from \$78.

- Send \$1 for Complete Catalog (Send \$2.00 or 4 IRC's for overseas mailing)
- Order by phone or mail Add \$3 S & H per order (Electronic answering service evenings & weekends)
- Use VISA, MASTERCARD, Check, or UPS COD.
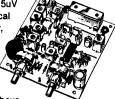
#### HIGH QUALITY XMTR & RCVR MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.

• R144/R220 FM RCVRS for 2M or 220 MHz. 0.15uV sens.;8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity, >100dBat ± 12kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138.



- R451 FM RCVR Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$138.
- R76 FM RCVR for 10M, 6M, 2M, or 220. As above, but w/o AFC or hel. res. Kits only \$118. Also avail w/4 pole filter, only \$98/kit.
- R110 VHF AM RECEIVER kit for VHF aircraft or ham bands or Space Shuttle. Only \$98.
- TA51 VHF FM EXCITER for 10M, 6M. 2M. or 220 MHz. 2 Watts continuous. up to 3W intermittent. Kit only \$68
- TA451 UHF FM EXCITER 2W cont., up to 3W intermittent. Kits only \$68. Xtal oven avail.
- VHF & UHF LINEAR AMPLIFIERS. For either FM or or SSB. Power levels from 10 to 45 Watts to go with exciters & xmtg converters. Several models. Kits from \$ 78.

NOW-FCC TYPE ACCEPTED TRANSMITTERS, RECEIVERS, AND REPEATERS AVAILABLE FOR HIGH-BAND AND UNF. CALL FOR DETAILS

#### Hamtronics Breaks the Price Barrier! ¥ No Need to Pay \$80 to \$125 for a GaAs FET Preamp.

LOW-NOISE PREAMPS

#### FEATURES

- Very Low Nose: 0.7dB VHF, 0.8dB UHF
- High Gain: 13 to 20dB, Depending on Freq.
- Wide Dynamic Range for Overload Resistance
- Latest Dual-gate GaAsFET, Very Stable

MODEL	TUNES RANGE	PRICE
LNG-28	26-30 MHz	\$49
LNG-50	46-56 MHz	\$49
LNG-144	137-150 MHz	\$49
LNG-160	150-172 MHz	\$49
LNG-220	210-230 MHz	\$49
LNG-432	400-470 MHz	<b>\$49</b>
LNG-800	800-960 MHz	\$49

#### HELICAL RESONATOR PREAMPS

Low-noise preamps with helical resonators reduce intermod and cross-band interference in critical applications. 12 dB gain.



MODEL	TUNING RANGE	PRICE
HRA-144	143–150 MHz	\$49
HRA-(*)	150–174 MHz	\$49
HRA-220	213–233 MHz	\$49
HRA-432	420–450 MHz	\$64
HRA-(*)	450–470 MHz	\$64
• •	ter frequency desired	

GaAsFET Preamps with fea-

**MINIATURE PREAMPS** 


NEW

tures similar to LNG, except designed for LOW COST and SMALL SIZE: only 5/8 W × 1-5/8L × 3/4H. Easily mounts inside many radios.

Model LNW-( \* ) ..... Only \$19/kit, \$34wired

Models available to tune the following bands: 25-35, 35-55, 55-90, 90-120, 120-150, 150-200, 200-270, and 400-500 MHz. \*Specify band

#### **IN-LINE PREAMPS**

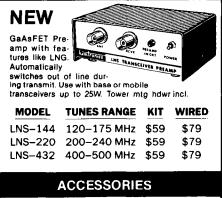

- MO-202 FSK DATA MODULATOR. Run up to 1200 baud digital or packet radio signals through any FM transmitter.
- DE-202 FSK DATA DEMODULATOR COR-2 KIT With audio mixer, local speaker
- amplifier, tail & time-out timers.
- COR-3 KIT with "courtesy" beep'
- DTMF DECODER/CONTROLLER KITS AUTOPATCH KITS. Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control.
- · CWID KITS SIMPLEX AUTOPATCH

hamlronics, in 65-E MOUL ROAD • HILTON NY 14468 Phone: 716-392-9430

Hamtronics<sup>x</sup> is a registered trademark





## PRACTICALLY SPEAKING ... ) E Can

## "function generator" circuits: part 2

Last month we discussed using textbook integrator circuits as low-pass filters, for generating quadrature sine wave signals, and for generating triangle waves out of square waves. This month, we'll look at some practical circuits, keeping in mind that there's a serious difference between textbook circuits and real, on-the-workbench ones.

#### a practical integrator


Almost all textbooks on linear integrated circuits or operational amplifiers include the circuit shown in **fig. 1**. This circuit produces an output voltage that is related to the integral of the input signal and the gain (-1/R1C1).

The nature of the integrator is that it produces an output voltage that is the time-average of the input voltage. There's only one problem with the traditional circuit: with real operational amplifiers, it often doesn't work! But unfortunately, some articles and books don't tell you what the problem is and how to deal with it. When I first started building integrators several years ago I discovered the problem the hard way.

The main problem in practical integrators is that the dc offset voltage normally present at the output of real operational amplifiers charges capacitor C1, and thereby soon saturates the op-amp. The output voltage starts rising immediately after power is applied and soon is off scale.

One method used to cancel the effects of offset is to use an operational amplifier that has a very low offset potential and no input bias current (or very little). For low-cost applications, the CA-3140 BiMOS op-amp (which uses MOSFET input transistors) is a good choice. Devices of the 741 family are almost useless for integrator service except for periodic signals with no dc offset.

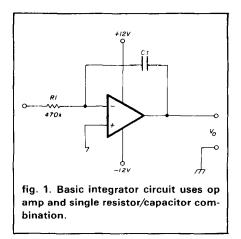Another procedure is to connect a resistor across the integrator capacitor in order to keep the dc from building up (**fig. 2**). This is especially useful for integrators that see periodic input signals. The rule of thumb is to make the shunt resistor (R2) very much larger than R1. In the test case, I used a 470-k input resistor and a 10-Megohm shunt resistor, which worked quite nicely.



Finally, we may also have to use an offset null potentiometer in some circuits. In my test case, with 400-Hz sine, square, and triangle wave input signals, the potentiometer was not needed. Other cases, however, may require a counter offset provided by R3. Although the values of the resistors in this network are dependent upon the application, most of the time a 5-k value for R3, and 10 to 27-k for R4 and R5 will suffice. Make R6 equal

to R1 for starters; it can be increased or decreased as needed after the circuit is tested.

To adjust the potentiometer, short the input of the integrator (making  $V_{in} = 0$ ). Adjust R3 for a potential of zero volts at point "A." Momentarily close S1 to force the output voltage to zero. If the output voltage rises to either positive or negative values after S1 is opened, adjust R3 to cause the rate of increase to slow down to zero. Again close S1 and see if the output voltage changes. Repeat the procedure until the output voltage remains at zero following every closing of S1.

In normal operation, switch S1 is used to reset the integrator after it performs an operation. It is used in some instruments where a value is calculated, but is only occasionally needed in cases where an integrator sees a periodic signal with no dc offset component. For slow circuits, the switch can be a relay, while in faster circuits it can be a CMOS electronic switch with an "on" channel resistance very much lower than R1. Keep in mind that this switch dumps the charge in capacitor C1, so the CMOS switch selected must be able to withstand the charge in the capacitor without burning up.

#### sawtooth generator circuit

Not long ago, when I was building Science Workshop's "Poor Man's Spectrum Analyzer," decribed by W4UCH in a recent *ham radio* article,<sup>1</sup> I needed a sawtooth generator circuit from an oscilloscope. But W4UCH had used a 30-year old Heathkit, and modern oscilloscopes don't have a sawtooth output. (Mine is a modern triggered sweep model with "X-Y" capability.) Although I eventually



Chas Browning, W4PKA

VISA

v 171

Subscription rates: 1 year USA \$18, Canada CDN\$24, Overseas US\$21; 2 years \$33, \$44, \$39 respectively. Single issue \$2.

TRY US! SUBSCRIBE OR SEND \$1 FOR YOUR SAMPLE COPY.

RADIOSPORTING Magazine

PO Box 282, Pine Brook, NJ 07058, USA

### /~ RADIO HANDBOOK **23rd Edition**

by Bill Orr W6SAI

Here are some of the highlights of this exciting new edition: New easy-to-use charts for Chebyshev and elliptic filter configuration, new data on power MOS-FETS, how to use state-of-the-art OP-AMPS, and home computer RTTY to name just a few examples. New projects include: GaAsFET preamps for 902 and 1296 MHz, easy-to-build audio CW filter, Economy two 3-500Z, 160 meter amplifier, multiband amp using two 3CX800A7's, and a deluxe amplifier with the 3CX1200A7 tube. New antenna projects include: efficient Marconi design for 160 and 80 meters, computer generated dimensions for HF-Yagis, and a 2 meter slot beam. Also all the other information you count on Bill Orr for! You deserve the latest Radio Handbook. 23rd edition ©1986

 $\Box$ 22424


Hardbound \$26.95
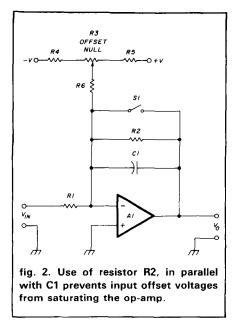
#### Reg. 29.95 SAVE \$3

Please enclose \$3.50 to cover shipping and handling








bought the Science Workshop sweep board described in W4UCH's article, I decided to look into sawtooth generator circuits. Because they're based on the integrator circuit, I decided to include them here.


**Figure 3** shows one attempt at designing a sawtooth circuit. It consists of an integrator (A1) followed by a voltage comparator; the output of the comparator drives the control input on an electronic switch (which is active-LOW). At turn-on, the charge in capacitor C is zero, so voltage  $V_A$  is zero. Because voltage V1 is positive, the output of the comparator (V2) is positive. Under this circumstance the control line of S1 is inactive, so S1 is open.

At turn-on, the stable reference voltage  $-V_{REF}$  causes the output of the integrator to increase. At the point where  $V_A = V1$ , the output of A2 drops LOW, forcing S1 to close. This discharges C, forcing the output voltage  $V_A$  down to zero.


Figure 4 was derived from a circuit given in one of Graeme's classic opamp books.<sup>2</sup> The ramp generator circuit is the integrator formed with A1, C1, and R3 (being driven by V – ). The output voltage rises until it reaches the threshold of comparator A2. That comparator uses positive feedback and a reference voltage V<sub>REF</sub> provided by

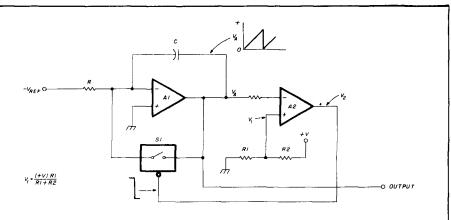



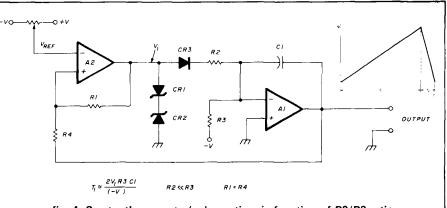




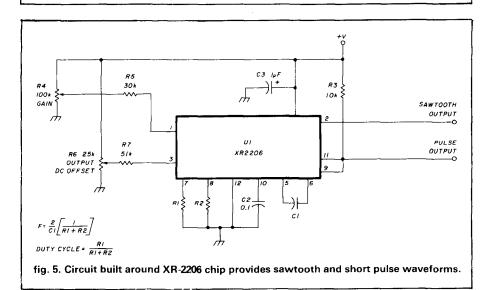

a potentiometer. The trip threshold is  $V_{REF}$  + V1 (which is set to 0.7 volts greater than the zener voltage of CR1/CR2, assuming that these diodes are identical). When the output voltage hits the threshold voltage, the

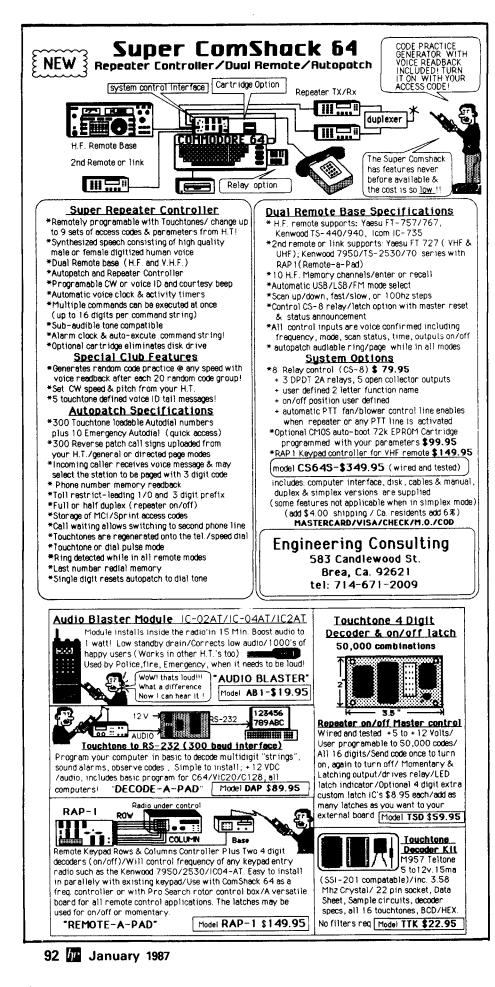comparator output snaps positive and forward biases diode CR3. If resistor R2 is very much less than R3, then C1 will discharge very rapidly, resulting in the classical sawtooth waveshape (see **fig. 4** inset). The reset time, T2, will



be very much shorter than the period, T1, if R2 < R3.

Another means of generating a sawtooth waveform is to use a special function generator chip such as the Exar XR-2206.\* The XR-2206 is capable of generating sine/square wave/ triangle waveforms; it is used to generate a sawtooth and a short duty cycle pulse in the circuit in fig. 5.

The frequency of this sawtooth generator circuit is set by resistors R1 and R2, plus capacitor C2:

$$F = \frac{2}{Cl(Rl + R2)}$$

where: F is in Hz, C1 is in Farads, and R1 and R2 are in ohms. The duty cycle is:

$$\frac{RI}{RI + R2}$$

Jameco\*\* makes a circuit board "function generator" kit for less than \$20 that creates the sine wave, square wave, and triangle wave signals. It can be easily modified for sawtooth applications.

#### references

1. Bob Richardson, W4UCH, "A Low-Cost Spectrum Analyzer with Kilobuck Features," ham radio, September, 1986, page 82.

2. Jerald G. Graeme, "Designing With Operational Amplifiers: Applications Alternatives," McGraw-Hill Book Company, New York, 1977, pages 159-162.

\*Dick Smith Electronics, P.O. Box 8012, Redwood City, CA 94063-8021. Order part No. Z6820 (\$3.95). \*\*Jameco Electronics, 1355 Shoreway Road, Belmont, CA 94002.

#### ham radio

#### MULTI-BAND SLOPERS ALSO: DIPOLES & LIMITED. SPACE performance of WPINN entennas is band BIG-SIGNAL reports! Automati-Coax feed - 3kw power - Compact-cilled center frequency each band

NN antennas is well known! Nowen-ports I Automatic bandswitching very wer - Compact - FUL y ASSEMBLED Compact - FUL y ASSEMBLED - Easy to install V Gery citana - Your personal check accepted for 1t - ... \$ 48 ppd 60 ft - ... \$ 48 ppd 60 ft - ... \$ 43 0, 40 A brt - ... \$ 57 160 fbru 100 - \$ 55 - 80 fbru 46 ft long \$ 55 - 80 fbru 100 - \$ 55 - 85 fbru 100 - \$ 55 fbru 100 -4611, long \$ 85 ppc out tuner) SEND SASE for complete de W9INN ANTENNAS 312-384-3414 И 172 вох зэзэн мт. PROSPECT, IL 60056

#### **Foreign Subscription Agents** for Ham Radio Magazine

Ham Radio Austria Karin Ueber Postfach 2454 D-7850 Loerrach West Germany Ham Radio Belgium

Brusselsesteenweg 416 B-9218 Gent əlgiur Ham Radio Holland Posibus 413 NL-7800 Ar Emmen Holland

Ham Radio Europe Box 2084 S-194 02 Upplands Vasby Sweden Ham Radio France

Ham Radio Switzerland Karin Ueber Postlach 2454 D-7850 Loerrach West Germany

Ham Radio Italy Via Maniago 15 1-20134 Milano

Galada Send orders to Ham Radio Magazine Greenville. NH 03048 USA Prices in Canadian funds 1 yr \$41.85, 2 yrs \$74.25 3 yrs \$99.90

Alma House Cranborne Road Potters Bar Herts EN6 3JW England

## Ham Radio England c/o R.S.G.B

Ham Radio Germany Karin Ueber Postfach 2454 Postfach 2454 D-7850 Loerrach West Germany

SM Electronic 20 bis, Ave des Clarions F-89000 Auxerre



## ACCESSORIES FOR RAMSEY COUNTERS



## open-wire line for 2 meters

## Low-loss, inexpensive VHF ''cable''

It's a well-known fact that transmission line losses increase with the frequency of operation. Coax and open-wire line manufacturers supply data to permit users to select the proper transmission line for a given frequency. The data is usually in the form of dB loss per 100 feet, specified at discrete frequencies or by means of a curve expressed in dB loss per 100 feet versus frequency. Typical transmission line attenuation losses are shown in **table 1**.

#### line loss and cost considerations

For any frequency, it's possible to find a line that provides the lowest losses to the antenna system. For frequencies below 30 MHz, losses are not a problem unless line lengths are great — for example, over 300 feet at 30 MHz. At that frequency, RG8/U may produce a 3-dB loss over the line length, which represents one-half the power being lost in the coax line.

There's also a relationship between transmission line loss and cost, which is nonlinear. For a given frequency, cost versus line loss is an inverse function; that is, the lower the loss, the higher the cost. At 145 MHz, we have the choice of several readily-available transmission lines (**table 1**). The table also shows the market cost of each type as determined from recent magazine advertisements. Some of the transmission line costs are high, especially for long runs.

I'm interested in both minimum line loss and minimum costs. Reference 1 describes such lines for operation below 30 MHz in lengths of approximately 500 feet. Those lines are open four-wire transmission lines of 200 ohms impedance, which can be converted to 50 ohms with 4:1 baluns at the high frequencies. Open two-wire lines of 200 ohms impedance become impractical because of the very close spacing (less than 0.1 inch) required.

#### running the line

When it came time to consider the location of a 2-meter beam to pick up the Carolina DX Association


repeater at a distance of approximately 50 miles, the closest tower was an 80-footer 120 feet from the operating position.

It has been my practice to bury coax cable from the house to the base of the antenna tower and run the coax up the tower. That practice was appropriate for low-frequency antennas in lengths of less than 200 feet. An alternative method would be to run a support line of steel cable between the house and the tower, securing the coax to the support line. Either way is acceptable; it's simply a matter of esthetics.
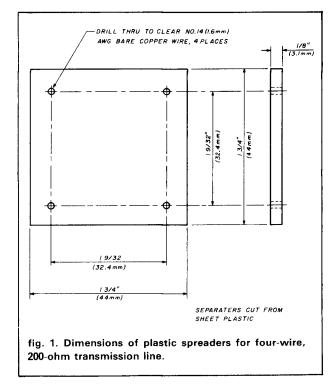
#### choosing the line

To run the coax underground and up the tower to the 50-foot level would require approximately 190 feet of transmission line. A suitable transmission line to produce an attenuation less than 2 dB for the total length would be one of the hard-line types.

Because of my successful experience with the four-



**By Henry G. Elwell, Jr., N4UH**, Rt. 2, Box 20G, Cleveland, North Carolina 27013


Table 1. Attenuation as a function of transmission line length.					
Cable Type	Impedance (ohms)	dB/100 ft (150 MHz)	Avg cost/100 ft (dollars)		
RG213/U	50	2.3	30.00		
RG8X	52	3.5	15.00		
RG58/U	52	6.0	12.00		
Aluminum (1/2 inch)	50	1.2	79.00		
Heliax, (1/2 inch)	50	0.9	179.00		
Heliax, (7/8-inch)	50	0.5	399.00		
Four-conductor, open-wire	200	0.6	46.00		
Notes: 1. Coax-type cables do not include connector cost. 2. The cost of the four-conductor open-wire line includes \$36.00 for 400 feet of No. 14 copper wire plus an additional \$10.00 for homemade spreaders and baluns. 3. The loss for the 200-ohm line is calculated from <b>eq 5</b> of refer- ence 1.					

wire, 200-ohm transmission line, I decided to use it for the straight-line, 120-foot run to the 2-meter antenna. Since I wanted as short a run as possible, the transmission line would be supported at the ends with no intervening support poles. That decision meant that the line would require good separation along its length as well as proper end supports.
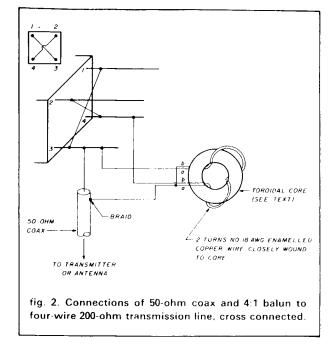
#### building the line

Four 120-foot lengths of No. 14 copper wire were measured, and about a dozen square plastic spreaders made by W2IRC (**fig. 1**) were slipped on one end. That end was tied to a tree. The remaining spreaders were slipped on the other end, and the line pulled tight and secured. The spreaders were finally separated by a distance of 3 feet, with each hole encapsulated with silicone rubber to retain each spreader at its selected location. The transmission line was left undisturbed; after a few days, I found they were properly secured.

I used a special four-wire, 200-ohm terminating block, available from W2ER,\* at each end. One was attached to the house and the other to the tower. Meanwhile, because commercial baluns for 145 MHz appeared to be unavailable, I made two 4:1 baluns. I decided small cores would be adequate for the amount of power to be used (25 watts maximum), so I wound Amidon iron-core type T94-12 cores as shown in **fig. 2** and soldered them to the cross-connected four-wire line at each end. Then I mounted a coax receptacle on the tower terminating block for ease of



assembly and wrapped the baluns in tape for minimal weather protection.

#### final assembly

I connected one end of the transmission line under the eaves, then ran the line to the transmitter using a 15-foot piece of RG8/U coax. I connected the other end to the 80-foot tower at the 50-foot level, then added a noninductive, 50-ohm resistor across the coax connector at the tower. The VSWR of the line measured 1:1.

This whole exercise came about because of the prodding of N4ZC, who wanted me to be able to access the Carolina DX Association repeater located near the North Carolina/South Carolina border. His final exhortation included an offer to install the 10-element beam for me. With that kind of an offer, who could refuse?

N4ZC installed the beam at the 50-foot level, connected the 6-foot length of coax, and inquired whether the Carolina DX repeater could be accessed from the height. I raced into the house, raised the repeater, then ran outdoors again to report success!

Before this system was installed, I couldn't hear any signals at all from the Carolina DX Association repeater; now, operation over the less-than-ideal 50-mile path is satisfactory. And although the VSWR on the antenna system becomes very high during heavy rain storms, operation into other North Carolina repeaters has improved tremendously.

#### references

ham radio

"Marshall Etter, W2ER, 16 Fairlane Drive, East Quoque, New York 11942.

<sup>1.</sup> Henry G. Elwell, Jr., N4UH, "Long Transmission Lines for Optimum Antenna Location," *ham radio*, October, 1980.


#### BLACK DACRON® POLYESTER ANTENNA ROPE UV-PROTECTED HJGH ABRASION RESISTANCE REQUIRES NO EXPENSIVE POTTING HEADS ·EASY TO THE & UNTIE ENOIS · EASY TO CUT WITH OUR HOT KNIFE SIZES: 3/32" 3/16" 5/16" SATISFIED CUSTOMERS DECLARE EXCELLENCE THROUGHOUT U.S.A. LET US INTRODUCE OUR DACRON ROPE TO YOU . SEND YOUR NAME AND ADDRESS AND WE'LL SEND YOU FREE SAMPLES OF EACH SIZE AND COMPLETE ORDERING INFORMATION 174 synthetic textiles,inc.

#### Save Time-Money with HAZER

- · Never climb your lower again with this elevator system
- · Antenna and rotator mount on HAZER complete
- system transitiower in verticle upright position
   Safety lock system on HAZER operates while
- raising-lowering & normal position. Never can fall Weight transferred directly to tower. Winch cable used only for raising & lowering. Easy to install and
- Will support most antenna arrays // 175
   High quality most antenna arrays
- · High quality materials & workmanship
- · Safety Safety - speed - convenience - smooth travel - inexpensive
- · Complete kit includes winch, 100 ft of cable, hardware and instructions. For Rohn 25 G Tower

Hazer 2-Heavy duty alum 12 sq ft load \$297 00 ppd Hazer 3, Standard alum, 8, sg. H. load 213,00 ppd Hazer 4-Heavy galv, steel, 16, sg. H. load 278,00 ppd Ball thrust bearing T8-25 for any of above 42,50 ppd

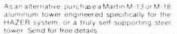Satisfaction guaranteed. Call today and charge to Visa or MasterCard



GLEN MARTIN ENGINEERING INC. P.O. Box H 253 Boonville, Mo. 65233 816-882-2734

## Subscribe Today

**Call Toll Free** (orders only) 1 (800) 341-1522 Have your credit card ready Ham Radio Magazine



A. Microwave Associates 10 GHz Gunnplexer. Two of these transceivers can form the heart of a 10 GHz communication system for volce, mcw, video or data transmission, not to mention mountaintop DXing! MA87141-1 (pair of 10 mW transceivers) \$251.95. Higher power units (up to 200 mW) available. B. Microwave Associates 24 GHz Gunnplexer. Similar characteristics to 10 GHz unit. MA87820-4 (pair of 20 mW transceivers) \$739.20. C. This support module is designed for use with the MA87141 and MA87820 and provides all of the circuitry for a full duplex audio transceive system. The board contains a low-noise, 30-MHz fm receiver, modulators for voice and mcw operation, Gunn diode regulator and varactor supply. Meter outputs are provided for monitoring received signal levels, discriminator output and varactor tuning voltage. RXMR30VD assembled and tested \$119.95. D. Complete, ready to use communication system for voice or mcw operation. Ideal for repeater linking. A power supply capable of delivering 13 volts dc at 250 mA (for a 10 mW version), microphone, and headphone and/or loudspeaker are the only additional items needed for operation. The Gunnplexer can be removed for remote mounting to a tower or 2 or 4 foot parabolic antenna. TR10GA (10 GHz, 10 mW) \$399.95. Higher power units available. TR24GA (24 GHz, 20 mW) \$639.95. Also available: horn, 2 and 4 foot para-

#### Advanced Receiver Research

Box 1242 • Burlington CT 06013 • 203 582-9409



- 176

#### HERE'S A NEAT GIFT IDEA

bolic antennas, Gunn, varactor and detector diodes, search and lock systems, oscillator modules, waveguide,

flanges, etc. Call or write for additional information. Let

ARR take you higher with quality 10 and 24 GHz equipment!

When we first saw the Casio PQ-40U Portable World Time Clock, we knew instantly that Ham Radio Bookstore customers would love this one.

This time piece is more than a simple clock. Besides all the standard features, alarm, snooze, lightweight portable design and digital readout, this clock gives you time at 21 different locations around the world at the twist of a dial. DX'ers will delight at being able to get rid of their cumbersome manual time calculators: determining band and path to use will be greatly simplified. Contesters can simultaneously display both local and UTC times for logging purposes. In fact, every Amateur will find at least a dozen uses for this nifty clock. You can take it with you when you go on vacation-business trips-set the alarm and get out of meetings early-anywhere you need a clock, the PQ-40U can go with you. Get a couple of them and give them as gifts, one for the house, car, office, just about anywhere you need a clock, the PQ-40U can go with you. Quantities are limited-order now and avoid disappointment.

PQ-40U

ham

radio

\$29.95

Please enclose \$3.50 shipping and handling

Greenville, NH 03048


BOOKSTORE


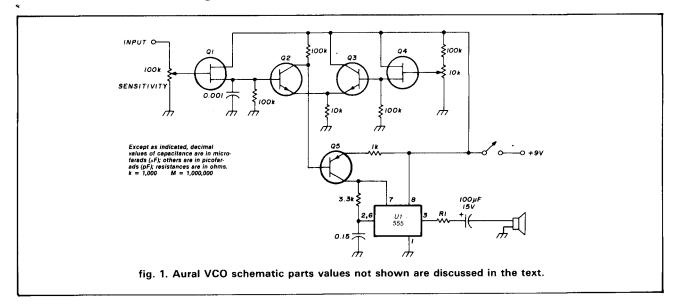
#### the weekender: aural VCO provides relative metering

frequencies, however, conventional varicap diodes aren't effective. Instead, transistor Q5 and the 1000ohm resistor form the variable element needed for controlling the frequency of our VCO by limiting the charging current flowing into the 0.15  $\mu$ F timing capacitor according to the forward bias being applied to Q5.

As the voltage on pins 2 and 6 of U1 reach 2/3 Vcc (about 6 volts with a 9-volt supply) the timer will fire and pin 3 will be pulled low. Pin 7, an open collector output, goes low and begins to discharge the timing capacitor — through the 3.3-kilohm resistor. The discharge time provided by this resistor assures a reasonable, although asymmetrical, waveform for the aural



**Being an avid 2-meter foxhunter**, I'm always willing to try out any new gadget that might serve that end. This article describes a circuit, shared with me by Don Lèwis, KF6GQ, for an RF sniffer which produces a tone that rises in frequency as the signal gets stronger. Ideas for a number of useful Amateur applications will be discussed.

#### how it works

**Figure 1** shows the schematic for the aural VCO. The heart of the circuit is a 555 timer used as an RC audio oscillator. The frequency is determined by the RC values; increasing the value of resistance or capacitance lowers the frequency, while decreasing either has the opposite effect. In an HF VCO design, a varicap diode would be used as the variable element controlling the frequency of oscillation; at audible

By Peter J. Bertini, K1ZJH, 20 Patsun Road, Somers, Connecticut 06071

signal generated by U1. At 1/3 Vcc the internal flipflop resets, the output on pin 3 goes high, the open collector output on pin 7 floats, and the timing cycle begins again.

Transistor Q5, a PNP device, is used in a common collector configuration. Forward bias occurs as the base is driven towards ground. Transistors Q1 and Q4 form a differential amplifier. The quiescent bias for Q5 is set by the 10-kilohm pot's setting the bias at one of the differential amp inputs. The input signal, applied to the remaining differential amp input, in turn controls the forward bias of Q5. As the input voltage rises, transistor Q5 is driven further into conduction, reducing the RC time constant and thus increasing the frequency of the tone.

#### adjusting and using the VCO

The tone level is set through the value of R1, the resistor in series with the pin 3 output of U1 and the speaker. Battery life will be greatly reduced if too small a resistor is used for R1. Depending on the audio level

## Join AMSAT...Today

Amateur Radio Satellite OSCAR 10 provides:

• A New Worldwide DX Ham Band open 10 hours a day.

• **Rag Chew With Rare DX Stations** in an uncrowded, gentlemanly fashion.

• **Popular Modes In Use:** SSB, CW, RTTY, SSTV, Packet

• Full Operating Privileges open to Technician Class licensee or higher.

Other AMSAT Membership Benefits:

Newsletter Subscription: Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

> **Satellite Tracking Software** Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

**AMSAT Membership** is \$24 a year, \$26 outside North America. VISA and MC accepted.

## AMSAT P.O. Box 27 Washington, DC 20044

301 589-6062


needed, 47 to 1000 ohms will serve here. The 555 can source or sink upwards of 200 mA and will easily drive speakers with 8 to 45 ohms impedance. With no input signal the zero-set pot is adjusted for the desired resting tone. A steady click-click-click (similar to the sound of a Geiger counter) marks the lowest frequency that should be set. At this point any signal applied to Q1 will proportionally increase the tone frequency.

#### construction

Because layout is not critical, perfboard with 0.1-inch centers may be used for component mounting; all of the parts are available "off-the-shelf" from your nearest electronics distributor or Radio Shack. A 2N2222, 2N3904, or similar small-signal NPN device may be used for Q2 and Q3. A 2N2907, 2N3906, or similar small-signal PNP transistor will serve for Q5. Q1 and Q4 are N-channel JFETs; an MPF102, 2N5485, 2N5486, or 2N5487 will work well, although the pinchoff voltage rating, if too low, may limit the range of the device. Feel free to use junkbox parts if they're available; the circuit is forgiving of part substitutions.

#### putting the VCO to work

**Figure 2** shows the VCO being used as a sensitive 2-meter field strength meter. Combined with a handheld DF antenna, the meter lets you leave your vehicle and find a hidden transmitter within easy walking distance.

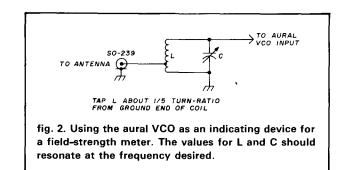


In a recent article I showed a simple external metering and attenuator for 2-meter FM transceivers.<sup>1</sup> Connecting this aural VCO to the signal-strength metering circuits allows you to orient your directional antenna without having to watch the S-meter — certainly a feature conducive to safe driving. Sightless or mobile HF operators might find that the aural VCO could replace the meter movement used for SWR bridges or relative output indication to facilitate antenna tuner or radio tuneup.

#### reference

1. Peter J. Bertini, K1ZJH, "The Foxbox: A Direction-Finding Tool," ham radio, October, 1985, page 25.

#### ham radio

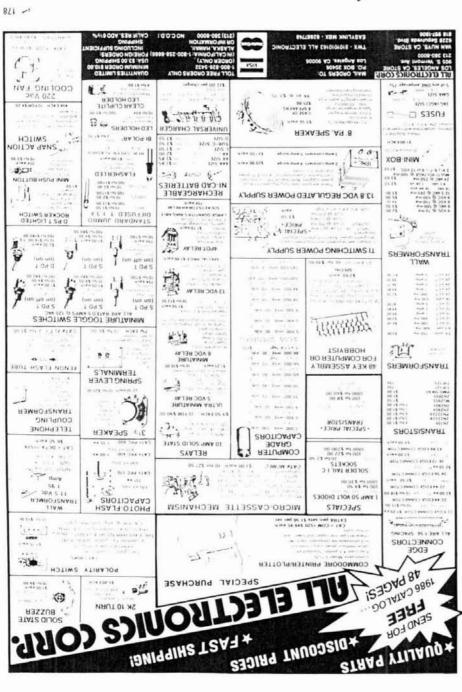



R.C. LUKASZEWICZ, WDBRCL 1948 COVENTRY COURT THOUSANDS ORKS, CA 91362 (805) 497-2397 WEST COAST DISTRIBUTOR

DIGITREX

States and

1853

1 B

6/1 1

Protessional and dependable perfor-

TRADE at a low cost

%100 of bafaidilso

9 volt battery

antenna

Uses 1 standard

Built-in telescoping

counters

nisp 8b 91 .

1

Xt.

入山

adA 1

A Carlot and a contraction of the contraction of th

dn-juer3

L I L I L I L

.mulA 11 08

indino/ni 9 02 .

SHAT mithin 1 kHz

Compact design-pocket sized

500 MHz Freq. Counter

044 26.6\$ YJN0 .

**NEW POCKET SIZED** 

· Increase sensitivity of receivers or

· Built, tested & ready-to-go

0.5 - 200 MHz bandwidth

• Over 8,000 sold since 1976 •

Wideband Preamp

80X 2806HR VERO BEACH, FLA. 32960-2806 80X 2806HR

ALUMA TOWER CO.

19w01 BmulA Van Mounted Crank-Up

Four Section 50 FL

adAr

alidom

1211811

10

Model T 140

do surro

48. ¥inu

IN

SPECIAL

vite tot details

REAL REPORT SUBJECT SU

EXCELLENT FOR

Crank-ups to 100 ft. Easy to install. Low Prices. LILT-OVER MODELS

TELESCOPING (CRANK-UP)

ALUMINUM

**YTIJAUO TZEHEIH** 

AMUJA Yd OWERS

Wodel 1 60 H . GUYED (STACK.UP)

1997

pue paufisap sieroads

- apeul slawoj jaajs pue

Over 36 types aluminum

apem

er ag hajugog

bns betzet-erg stinu IIA .

71152 bright, Virginia 23117 7572-894-5777

south liA

ES jopin and buildings

consultations must

185 -1

115

HF         Equipment         Regular SALE           IC-735         HF         transceiver/SW         999.00         849*           PS-55         External power supply         199.00         179*           AT-150         Automatic antenna tuner         445.00         359*           FL-32         500 Hz         W filter
IC-745         9-band xcvr w/.1-30 MHz rcvr 1049.00 899*5           PS-35         Internal power supply
IC-751         9-band         xcvr/.1-30         MHz         rcvr         1399.00         999%           IC-751A         9-band         xcvr/.1-30         MHz         rcvr         1649.00         1399           PS-35         Internal power supply
RC-10         External frequency controller         39.25           Other         Accessories:         Regular         SALE           IC-2KL         160-15m solid state amp w/ps 1999.00         1699         PS         169.00         154 <sup>33</sup> PS-30         Systems p/s w/cord, 6-pin plug         299.00         269 <sup>35</sup> 00         269 <sup>35</sup> OPC         Opt. cord, specify 2, 4 or 6-pin         10.00         MB         Mobile mount, 735/745/751A
SP-3         External speaker         61.00           SP-7         Small external speaker         49.00           CR-64         High stab. ref. xtal (745/751)         63.00           PP-1         Speaker/patch         159.25           SM-6         Desk microphone         44.95           SM-8         Desk microphone         78.50           SM-10         Compressor/graph EQ. 8 pin mic.         136.25           AT-100         100W 8-band auto antenna tuner         445.00           AT-500         500W 9-band auto.         559.00         489*3           OPC-118         Adapts AT-100/500 to 1C-735         16.00
AH-2 8-band tuner w/mount & whip 625.00 549% AH-2A Antenna tuner system, only 495.00 429%

	M
Check the Prices at	AES"!
Other Accessories - continued: GC-4 World Clock (Closeout) GC-5 World clock	99.95 <b>59*</b> 91.95
6-meter VHF Portable IC-505 3/10W 6m SSB/CW portable BP-15 AC charger	14.00
EX-248 FM unit LC-10 Leather case	39.50
VHF/UHF base multi-modes IC-551D 80W 6-meter SSB/CW EX-106 FM option	140.00 12695
BC-10A Memory back-up. IC-271A 25W 2m FM/SSB/CW AG-20 Internal preamplifier	64.00
IC-271H 100W 2m FM/SSB/CW AG-25 Mast mounted preamplifier IC-471A 25W 430-450 SSB/CW/FM xcvr	95.00 979.00 869*5
AG-1 Mast mounted preamplifier IC-471H 75W 430-450 SSB/CW/FM AG-35 Mast mounted preamplifier	1399.00 <b>1169</b> 95.00
Accessories common to 271A/H a PS-25 Internal power supply for (A) PS-35 Internal power supply for (H)	115.00 10495 199.00 17995
SM-6 Desk microphone EX-310 Voice synthesizer TS-32 CommSpec encode/decoder	46.00 59.95
UT-15 Encoder/decoder interface UT-15S UT-15S w/TS-32 installed	92.00
VHF/UHF mobile multi-modes IC-290H 25W 2m SSB/FM, TTP mic IC-490A 10W 430-440 SSB/FM/CW	Regular SALE 639.00 56935 699.00 59935
VHF/UHF/1.2 GHz FM IC-27A Compact 25W 2m FM w/TTP mic	
IC-27H Compact 45W 2m FM w/TTP mic IC-37A Compact 25W 220 FM, TTP mic	459.00 <b>399</b> <sup>95</sup> 499.00 <b>439</b> <sup>95</sup>
IC-47A Compact 25W 440 FM, TTP mic PS-45 Compact 8A power supply UT-16/EX-388 Voice synthesizer	139.00 <b>129</b> *5 34.99
SP-10 Slim-line external speaker IC-28A 25W 2m FM, UP/DN mic IC-28H 45W 2m FM, UP/DN mic	459.00 39955
IC-38A 25W 220 FM IC-48A 25W 440-450 FM	459.00 399** 459.00 399**
HM-14 TTP microphone UT-28 Digital code squelch UT-29 Tone squelch decoder	37.50
HM-16 Speaker/microphone IC-3200A 25W 2m/440 FM w/TTP	34.00 599.00 <b>499</b> <sup>95</sup>
UT-23 Voice synthesizer AH-32 2m/440 Dual Band antenna AHB-32 Trunk-lip mount	34.99 37.00 34.00
Larsen PO-K Roof mount Larsen PO-TLM Trunk-lip mount	20.00 20.18
Larsen PO-MM Magnetic mount RP-3010 440 MHz, 10W FM, xtal cont. IC-120 1W 1.2 GHz FM Mobile	1229.00 1099
ML-12 1.2 GHz 10W amplifier IC-1271A 10W 1.2 GHz SSB/CW Base	379.00 339*5 1229.00 1079
AG-1200 Mast mounted preamplifier PS-25 Internal power supply EX-310 Voice synthesizer	
TV-1200 ATV interface unit UT-15S CTCSS encoder/decoder RP-1210 1.2 GHz, 10W FM, 99 ch. synth	129.00 119 <sup>95</sup> 92.00

	MasterCard	VISA <sup>.</sup>
	Hand-helds IC-2A 2-meters IC-2AT with TTP	299.00 25935
	IC-3AT 220 MHz, IC-4AT 440 MHz, IC-02AT 2-meters, IC-03AT for 220 I	ITP 339.00 299*5 399.00 339*5
	IC-03AT for 220 F IC-04AT for 440 F IC-02A 2-meters IC-02AT with TTP.	MHz 449 00 389*3 299 00 269*3
	Accessories for u2 GHz FM HT/batt/cgr/	A/T Call TTP 459.00.399**
Accessories fo BP-7 425mah/	13.2V Nicad Pak -	Regular use BC-35 74.25
BC-35 Drop in BC-16U Wall of	8 4V Nicad Pak - use desk charger for al harger for BP7/BP8	I batteries 74.50 20.25
LC-14 Vinyl cas LC-02AT Leathe	se for DIx using BP-3 se for DIx using BP-7 er case for DIx models	/8
BP-3 Extra Std.	or IC and IC-O se 7.2V Nicad Pak - use 250 mah/8.4V Nica	ad Pak 37.50
BP-5 425mah/	attery case 10.8V Nicad Pak telescoping 2m ante flexible antenna	use BC35 58 50
CP-1 Cig lighte CP-10 Battery	telescoping 2m ante flexible antenna r plug/cord for BP3 separation cable w/o tion pak for standa	or Dix 13.00 clip 22.50
EX-390 Bottom MB-16D Mobile	slide cap mtg. bkt for all HTs case for standard n	5 50 
RB-1 Vinyl wate HH-SS Handhel HM-9 Speaker	erproof radio bag Id shoulder strap microphone	34 95 16 95 47 00
HS-10SB PT	icrophone/headset w unit for HS-10 & D I unit for HS-10 in/10w out amplifier	
SS-32M Comms Receivers	spec 32-tone encode	Regular SALE
RC-11 Infrar FL-32 500 H	-30 MHz, 117V AC. ed remote controller z CW filter z CW filter (1st IF). filter (2nd IF).	67.25 66.50
EX-257 FM u EX-310 Voice	init e synthesizer	178 00 <b>159</b> ** 42 50 46 00
SP-3 Externa CK-70 (EX-29	stability oscillator ) al speaker	61 00 12 25
R-7000 25 MH RC-12 Infrar	le mount 2-2 GHz scanning ed remote controller	rcvr 1099 00 <b>969</b> <sup>95</sup> 67 25
AH-7000 Ra	e synthesizer diating antenna	89 95 (12)
Milwaukee WA	Mon. thru Fri. 9-	-0411 answered
WATS lines	1 8:00 pm Monday are for Quotes & 0 line for other Info	Ordering only,
11110-1111-1-1-1-1-1-1-1-1-1-1-1-2-2-3	list are subject to cha side Milwaukee	



## an IF sweep generator

## Versatile unit tests and aligns LC, crystal and mechanical filters

How would you like to have a versatile piece of test gear that could be used to align LC, crystal, or mechanical filters as well as to provide fm discriminator alignment? The generator described in this article can be set to a center frequency of 455 kHz and frequency modulated at any desired deviation up to  $\pm$  40 kHz. The sweep rate of 25 Hz is suitable for checking filters such as the Murata CFS series and for fm discriminator alignment. A 2-Hz rate is used for checking narrow-bandwidth crystal and mechanical filters. Linearity of sweep is excellent. A crystal diode detector is built in. A dc-coupled scope and a frequency counter are needed for calibration and display.

#### circuit operation

Referring to the schematic (fig. 1), U1, Q1, Q2 and associated components make up the rate and ramp generator. U1 is connected in the conventional astable circuit, but with the addition of CR4 and CR5 silicon diodes.



Photo 1. BP1 is labeled IN. Connect to input filter under test. BP3 is labeled OUT. Connect to output of filter under test. Positive going pulses about 5 microseconds long occur at the output, pin 3, at 40-millisecond intervals (fast rate) and at about 480-millisecond intervals (slow rate).

Assume that at turn-on, C1 is at zero voltage. Q2 is turned off and C9 in the 555 timer circuit is also at zero voltage. C1 begins to charge through constant current generator Q1. A linear voltage ramp appears at Q2 collector. When U1 times out, a short positive pulse is coupled to Q2 base through R3. It turns Q2 on, which rapidly discharges C1, and the cycle is repeated at the rate selected by S1. Ramp voltage is applied to the gate of Q3. which is used as an inverting buffer and for dc-level shifting. Q3 drain is directly connected to modulation input pin 5 of U2, an LM566 function generator. It is a voltage-controlled oscillator, which outputs approximately square waves at pin 3 (not used here) and more or less triangular waves at pin 4. The changing voltage at pin 5 frequency modulates the output at pin 4, which is applied to the unit under test. Output from that unit is detected and filtered by CR3 and associated components, and a dc voltage proportional to this output is supplied to the scope vertical amplifier at J3.

The scope horizontal amplifier is connected to J1. The ramp voltage sweeps the trace left to right and the detected output voltage deflects the trace vertically. Thus the display can trace out the passband of a filter or the characteristic S-curve of an fm demodulator.


#### component selection

Capacitors C1 and C2 should be tantalum. C4 is polystyrene; an NPO ceramic would probably serve as well.

R1 in the constant-current generator limits charging current to C1, and its value may need to be changed to allow C1 to be charged to about 4 volts during the 40-millisecond period of the 25-Hz sweep rate. When in the 2-Hz mode, C1 will charge to about 8.5 volts. Neither value of voltage is critical.

O2 must be a fast-switching type, capable of handling the high peak current that flows when C1 is discharged. Its duty cycle is very low. The 2N2222A used here has

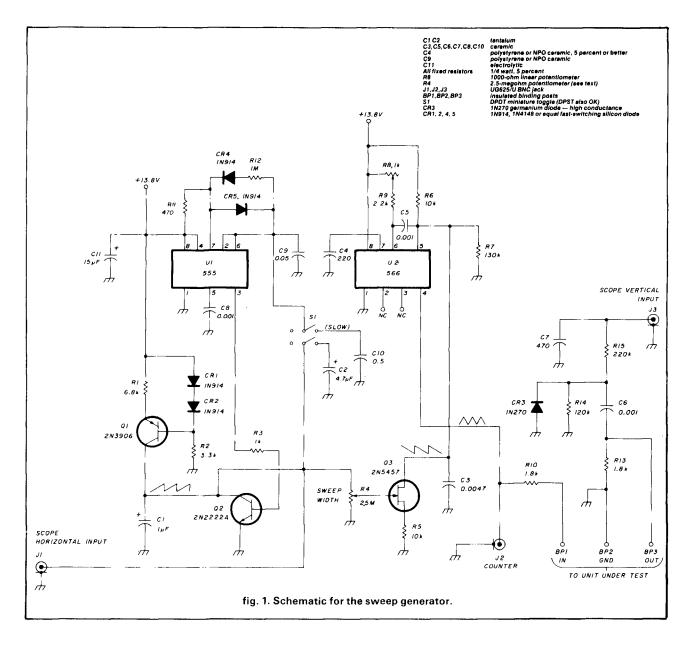By Bob Griffith, W2ZUC, 476 Keenan Avenue, Fort Myers, Florida 33907




survived many hours of operation. R3, the 1-kilohm resistor in series with Q2 base, is near the maximum value that allows the collector to be driven close to ground.

It's possible that U1 may fail to output the desired 5-microsecond pulse. If so, increase R11 to 1-kilohm, which will lengthen the pulse but won't upset operation.

Sweep width control R4 is a 2.5-megohm potentiometer. It may be replaced by a 1-megohm potentiometer in series with a 1-megohm fixed resistor to Q2 collector. The full ramp voltage isn't needed (or usable) at the gate of Q3.

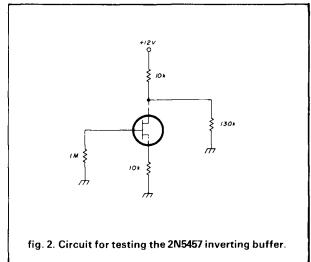Q3 is a readily available JFET. However, the spread in characteristics is broad, and it may be necessary to try more than one in this circuit. The selection can be made by setting up the test circuit of **fig. 2**. Pick a transistor that draws enough current to make the drain voltage approximately 12.0 volts and source voltage about 0.8



volts. The value of the 130-kilohm resistor can be varied  $\pm 20$  percent if necessary.

U2 center frequency is determined by R8, R9, and C4. R9 is near the recommended 2-kilohm lower limit for the 566. When the sweep is zero, the output frequency can be varied from 350 kHz to 486 kHz. The upper frequency limit of the chip is 1 MHz, but any lower range can be obtained by increasing the values of R and C in the timing circuit.

The inverted ramp voltage supplied to U2, pin 5 from Q3 drain causes the VCO frequency change. Sensitivity is high; from a resting voltage of 12.0 volts, a drop of 0.1 volts to 11.9 volts increases the frequency about 22 kHz. Thus the output frequency at pin 4 increases during the ramp cycle, and the display is from left to right for increasing frequency.

Resting voltage at U2 pin 5 should be close to 12.0 volts for a 13.8-volt supply to obtain best linearity of sweep frequency. Total current drawn is 48 mA. An on-card 12-volt regulator can be used. If so, adjust the value of R7 to bias pin 5 at 10.5 volts. Closely regulated voltage isn't necessary, but it must be well filtered. The ramp generator and U2 are sensitive to hum voltages. For that reason, an external power supply is used.

#### construction

All the components except width control R4, center frequency control R8, S1 with C2 and C10, and the binding posts and jacks are on a single-sided board measuring 1.5 by 5 inches. I don't have a layout for it; I make lines and pads using dental burrs in a a high-speed grinder. Perf board should be acceptable.

The controls, switch, three binding posts, and three UG-625/U BNC jacks are mounted on an aluminum panel measuring 3.5 by 6 inches. The board is held to the panel by two small angle brackets. A short two-conductor cable with a two-contact male connector passes through a hole in the phenolic box, which measures 3.8 by 6.3 by 2 inches. No high frequencies are involved, but there are some high-impedance points and good insulation is needed.

#### initial checkout

Connect a counter to J2 and connect the scope DC vertical input to J1. Turn sweep width control R4 fully counter-clockwise and set center frequency control R8 fully clockwise. Set S1 to fast and apply well-filtered 13.8 volts to the power connector. The frequency should be about 486 kHz. Turn the center frequency control fully counter-clockwise. The frequency should be about 350 kHz. If the upper frequency is below about 475 kHz, you can shunt R9 with a fixed resistor from 22 kilohms upward, or try a slightly smaller value of capacitor at C4. The upper limit isn't critical, but it must be high enough to allow setting of the frequency at the upper point of a filter under test, which will be explained later.

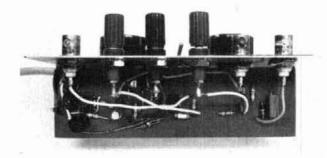


Photo 2. Bottom view of circuit board. The 555 timer is at left. Q2 and Q1 are next to the right. Q3 is near the front of the board between BP1 and BP2. The 566 is near the center of the board. Detector and associated components are at the right end.

Check the ramp voltage. It should be a very linear sawtooth having a period of approximately 40 milliseconds and a peak amplitude of about 4 volts. If no signal is here, check Q1 for short or open circuit and check Q2 base for a positive-going pulse. If it's missing, check the 555 timer. Set S1 to slow. The sawtooth amplitude should be about 8.5 volts and the period near 480 milliseconds.

This procedure assumes that you have a scope with a calibrated sweep. If not, the counter should work on the 25-Hz rate, and the 2-Hz rate can be estimated by visual check against a sweep second hand. Neither rate is really critical. If you don't intend to check very narrow filters, the slow rate and switch can be eliminated.

Disconnect the counter and connect the scope probe to J2. Turn the sweep width control to about 10 o'clock. Triangular waves about 3 volts peak-to-peak above a 5-volt DC level should appear. Successive waves should appear to move left and right at the repetition rate of the ramp voltage. If little or no movement can be seen, check for a signal at the gate of Q3 and at its drain. If there's a normal signal at the gate but no inverted signal at the drain, check the dc bias at the drain and at pin 5 of the 566.

Connect a jumper from BP1 to BP3 (binding posts). Connect the scope dc horizontal input to J1 and vertical input to J3. Turn the sweep width control to minimum. Vary the center frequency control through its range and observe the trace on the scope face. It should be a straight line at 400 to 500 millivolts above ground. Turn up the width control. Output at J3 should not change except near maximum sweep.

#### calibration and use

Connect the input of the filter to be tested to BP1, ground to BP2, and the output of the filter to BP3. Set the center frequency and width controls to obtain a display that looks like an inverted U. Check both sweep rates. If there's a noticeable difference in the trace shape, use the slower rate. Increase the sweep width and note

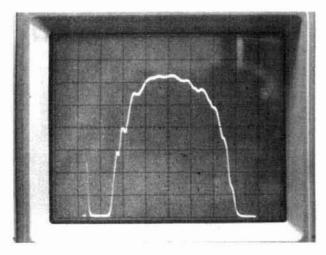


Photo 3. Scope display of passband of Murata CFS455E filter. Each horizontal division is 0.5 volts. Each vertical division is 50 mV. Sweep rate is 25 Hz. The 6dB points are at 446 and 466 kHz. The pip at left of trace is not a spurious response of the filter. It is display of retrace during the negative going portion of the ramp voltage, since there is no blanking during that interval.

that the trace moves to the left. This is normal. Restore to center by adjustment of the center frequency control.

Reconnect the counter to J2. Position the trace so that a point near the middle of the passband is at some easily noted height — for example, six divisions above the zero-volt baseline. Reduce the sweep to zero and adjust the center frequency control for six divisions in height of the now-straight horizontal line. Read the frequency from the counter. This is the frequency for approximately the center of the filter. Now readjust the center frequency control for three divisions in height at both low and high-frequency ends of the passband. Read the counter again. These frequencies are at the 6-dB points for that filter. Symmetry and ripple within the passband are easily seen on the display.


It's impossible to determine the 60-dB points accurately on a filter passband using the simple diode detector in this unit. An idea of the skirt selectivity and presence of nearby spurs can be obtained by reducing scope attenuation to a minimum. Alternatively, you might disconnect the detector circuit and measure the output voltage of the filter with a well-calibrated RF millivoltmeter.

For narrow passband ceramic or crystal filters, follow the manufacturers' recommendations for input and output terminations. The values may be quite different from the 1.8 kilohm series and shunt resistors I chose. (Mine were close to the 1.5-to-2 kilohm terminations specified for the Murata CFS series filters that are commonly used in 2-meter fm receivers and in VHF marine radios.) Mechanical filters usually require shunt C at both input and output to resonate the coupling coils within them. You may wish to remove R13 from the board and use it or other values externally between BP2 and BP3. For the home brewer of multipole crystal filters, this generator should make it much easier to trim to the desired center frequency and minimize ripple.


For discriminator alignment, input a signal through a capacitor of 1000 pF to a point in the receiver ahead of the discriminator but following any 455-kHz filter. Use a 1-kilohm potentiometer for level adjustment and check with a scope to see that sufficient signal is injected to cause limiting before the discriminator. Set the center frequency and sweep width as required to obtain a trace of the S-curve and adjust the primary and secondary for best linearity. The desired center frequency should be halfway between those at the ends. If a very narrow (for fm) filter such as the CFS-F is used in the receiver, you may wish to remove the filter and determine its actual passband and center the discriminator to match.

You can also determine the curve for the ceramic discriminator now used in many 2-meter transceivers. These are fixed and no adjustment is provided. They appear to be inferior to a good Foster-Seeley discriminator with respect to linearity, although they are undeniably smaller and probably less expensive.

ham radio

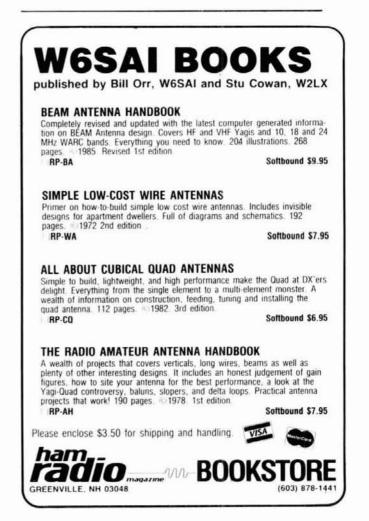



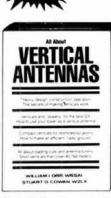

## ALL ABOUT VERTICAL ANTENNAS

by Bill Orr, W6SAI and Stu Cowan, W2LX

Smart DX'ers know that the vertical antenna can be the secret to low band DX success. Until now, most books gave at best a cursory overview and a couple of projects for the vertical. Ham Radio's well known columnist and book author Bill Orr, has now given the vertical the kind of attention it deserves in his own popular style. Theory, design, construction, operation-all the secrets of making the vertical work-are fully covered in clear concise easyto-read text. Orr is a master at making the complex simple and this book is no exception. Here's just a sample of what this exciting new book covers: Horizontal vrs vertical-which is best? Top loaded and helical antennas, 5 high efficiency Marconi antennas for 80 and 160, verticals and TVI-Is there a problem? The effects of ground on vertical antennas and a how to make an effective ground system, The Bobtail beam, construction data for 25 different antennas, matching circuits of all descriptions-which is best, plus P-L-E-N-T-Y more! For years Hams having been asking for this book. Get your's now. You won't regret it! 1986, 1st Edition. RP-VA

Softbound \$10.95

Please enclosed \$3.50 shipping and handling ham radio's bookstore

Greenville, NH 03048



While some mergers result in funny names, the recent merger of Monitoring Times and International Radio (formerly the Shortwave Guide) has resulted in an excellent new 60-page magazine covering fullspectrum utilities communications as well as worldwide shortwave broadcasting activities. To keep it simple, we've retained the name of one of the two partner companies-Monitoring Times. It's all new, bigger, more colorful and more informative. Clearly, it's the most comprehensive publication for the radio listener available today!



Send for a free "sample digest" or subscribe by contacting: MONITORING TIMES P.O. Box 98

Brasstown, N.C. 28902 704-837-9200 Rates: 1 Yr. \$14; 2 Yrs. \$25; 3 Yrs. \$36

## Your Number One Source of PACKET Information



For Computerists and Amateur Radio

		New Second			
U.S.A		\$18.0		Yr	
		\$33.0 \$48.0			
Mexic	<b>%</b> 0	ψτυιν		′ • •	
Cana		\$32.0	00 1	Yr	
All OI		<b>^</b> ^^			
Coun	tries	\$68.0		Yr	
		(Air) \$43.(			
and and a second se		(Sur			
	FUND	<u>S`ONI</u>			
	anent l				
Subs	criptior ole Cop	ר גי ג	15U.( ¢ 2	10   50	
Samp	ne cop	У	φυ.	50	
Cut out and	mail co	oupon	at r	ight t	:0:
Circu	latio	n N	<b>l</b> ar	lag	er
	04 Sa			-	
Birmin	igha	<b>m,</b> <i>A</i>	Ł	55	235

(205) 854-0271

185

## Why you Should Should Subscribe! Read what our subscribers say!

•Your magazine is the fines i innovation that I have seen in ham radio since 1953 - except... maybe the all-solid state transceiver. Carl Soltesz • Twelve more, please. Ed Shaughnessy • Love the articles on Timex-Sinclair computers. A. Nieuwenhoff, Sutton, MA • ...have most certainly received my moneys worth in software... Michael Regan, K8WRB • ... information contained in the articles has made me more "computer literate" than would have been possible reading only publications dedicated to my particular computer. Donald H. Halsccher, W8MHR, Martinsburg, WV • Here it is renewal time already -- time sure passes fast when you are having fun (reading CTM). Bob Sirekis, Holly Hill, FL • ....thank your for a great magazine. Frank Davis, Peru, IN • Another year goes by and another subscription dollar well spent. R. P. Campbell, LaPlace, LA • CTM and you have found the way to an advertisers heart. Quality of publication and reasonable advertising rates are basic criteria you have achieved better than your competition. But what really sets you apart from others is empathy, a tasteful quality in which you excell while others can't even pronounce the word. Bob Harris Sr., BCD Electro, Richardson, TX • ...,you have found a nice niche for CTM in packet... you have me getting interested... Charlie Curle, AD4F Chattanooga, TN • The packet/computer info convinced me to subscribe. John Skubick, K8JS • Enclosed is my check for renewal of my subscription. I enjoy the down to earth and homey style of your magazine and the many fine computer raticles... Andy Kosiorek, Lakewood, OH • I was both pleased that I have seen in any of the computer or amateur radio magazine. It would appear that CTM has just the right blend of packet/amateur radio aricles and computer articles. Barry Siegfried, K2MF • Thank you for an excellent magazine, and the only magazine i formative magazine. I coking forward to each issue. Carl & Nancy Jones, Kodiak, AK • ...received my moneys word work just other magazines I receive e ach comith cart so there thou

NAME		
CALL SIGN		
ADDRESS		
<u>CITY</u>	<u>ST</u>	
<u>ZIP</u>	PHONE	
<u>DATE</u>		
SIGNATURE		







" Crystal For most Ham Rigs from: **KENWOOD • YAESU • HEATHKIT** Also Drake R-4C/7 Line, COLLINS 75S3-B/C and ICOM FL44A, FL52A, FL53A clones. **Finest 8-pole Construction** ALL POPULAR TYPES IN STOCK CW • SSB • AM ASK ABOUT OUR MONTHLY UNADVERTISED SPECIALS Phone for Information or to Order. VISA/MC or COD accepted Why risk disappointment? Buy timetested Fox-Tango Filters to be sure! FQX-TANGO Corp. Box 15944, W. Palm Bch, FL 33416 Telephone: (305) 683-9587 European Agent: INGOIMTEX, Post Fach 2449, D8070 Ingolstadt, West Germany

187



Garth Stonehocker, KØRYW

## **DX** propagation

When you're working DX, you can usually expect that the conditions that optimize your transmitted signal will do the same for your receiving capability. There are exceptions to this rule, of course — during ionospheric tilt conditions, for example.\*

For the strongest signals, it's best to use the highest frequency band (i.e., near the maximum usable frequency, or MUF) the ionosphere will support for the path in the direction of interest (see chart). Doing so reduces the number of hops required through the signal-absorbing D-region to the distant station and results in a stronger, more readable signal with less distortion and variation.

To be able to use the maximum hop length (the lowest number of hops) the take-off angle (TOA) of the signal from the antenna must be about 10 degrees. The longest paths in the chart are to Australia (from Eastern USA), South Africa (from mid-USA), and Antarctica (western USA). All of these paths' hop lengths are between 1711 and 2456 miles, with TOAs within a range of from 3 to 9 degrees and 2 to 5 hops.

Because the MUFs and TOAs exhibit diurnal, seasonal, and solar variations (sunspot/solar flux numbers), a new chart is published each month. MUFs for specific locations can be found by using programs like MINIMUF 3.5<sup>1</sup> and modified versions that consider other path parameters such as bearings, distances and TOA, as discussed in previous columns.<sup>2,3</sup>

The italicized numbers in the chart refer to MUFs during the night and predawn hours, which may be problem times. At these times, particularly near sunrise, the ionosphere develops a tilt that causes rapid changes in frequency and height, affecting east-west paths every day. Bands come in or go out at these sunrise and sunset times on the path, and DX openings are often unusually good, if brief.

To be continued next month . . .

#### last-minute forecast

Because of the increased probability of solar activity, the middle of January is expected to be the best time for openings on 10 through 30 meters. Good transequatorial openings in the evenings can be expected to continue through the third week of the month, when an unstable geomagnetic field is anticipated. The lower frequency bands, open mainly during the night, should be at peak performance during the first week of the month. The last week will also be very good, except for a greater probability of lower-level signals being affected by winter anomolous absorption after the 15th.4 However, because January is the month in which atmospheric noise is lowest and the geomagnetic field is least disturbed, operation should be outstanding.

#### band-by-band summary

Ten, twelve, fifteen, and twenty meters will be open to most areas of the world from morning to early evening almost every day. Openings on the higher of these bands will be shorter and will occur closer to local noon. Transequatorial propagation on these bands will more likely occur toward evening during conditions of highest solar flux and disturbed geomagnetic field conditions.

Thirty and forty meters will be useful almost 24 hours a day. Daytime conditions will resemble those on 20 meters. Skip distances and signal strength may decrease during midday on days that coincide with the higher solar flux values. Nightime DX will be good except after days of high MUF conditions and during geomagnetic disturbances. Look for DX from unusual places on east, north, and west paths during this time. The usable distance is expected to be somewhat less than 20 in daytime and greater than on 80 at night.

Eighty and one-sixty meters will exhibit short-skip propagation during daylight hours and lengthen for DX at dusk. These bands follow the darkness regions, opening to the east just before local sunset, swinging more to the south near midnight, and ending up in the Pacific areas during the hour or so before dawn. The 160-meter band opens later and closer earlier than 80.

#### references

1. Robert B. Rose, K6GKU, "A Simplified MUF-Prediction Program For Microcomputers," QS7, December, 1982, page 36.

<sup>\*(</sup>We like to think of the D, E and F region as concentric layers, but this is not always the case-Ed.)

<sup>2.</sup> Garth Stonehocker, KORYW, "Antenna-tolonospheric Path Match," DX Forecaster, *ham radio*, October, 1986, page 92.

<sup>3.</sup> Garth Stonehocker, KORYW, "Ionosphere Matching," DX Forecaster, *ham radio*, January 1985, page 92.

<sup>4.</sup> Garth Stonehocker, K0RYW, "More On Winter Anomalous Absorption," DX Forecaster, *ham radio*, December, 1986, page 101.

		WESTERN USA					MIDUSA									1		EASTERN USA										
QMT	PST	N ¶	NE	E 	SE	s ↓	sw	₩	NW	MST	N ↑	NE	E —	SE	s ↓	sw	₩ ♣—	NW	ĊST	EST	N <b>↑</b>	NE	E —	SE	s↓	sw	w 	NW
0000	4:00	40	40	20	12	12	10	12	20	5:00	40	40	20	15	12	10	12	20	6:00	7:00	40	40	20	20	15	12	15	40
0100	5:00	30	40	20	15	12	10	10	20	6:00	30	40	30	20	15	12	12	30	7:00	8:00	40	40	30	20	20	20	20	40
200	6:00	30	40	20	20	12	12	12	20	7:00	30	40	30	20	15	15	12	30	8:00	9:00	40	40	30	20	20	20	20	40
100	7:00	40	40	30,	20	15	15	15	30	8:00	40	40	30	20	20	20	12	40	9:00	10:00	40	80*	30	20	20	20	20	40
0	8:00	40	40	30	20	20	20	20	30	9:00	40	40	30	20	20	20	15	40	10:00	11:00	40	80*	30	20	20	30_	30	40
00	9:00	40	40	30	20	20	20	20	40	10:00	40	40	30	20	30	20	20	40	11:00	12:00	40	80	30	30	20	30	30	40
20	10:00	40	40	30	30*	20	20	20	40	11:00	40	80	30	30	30	20	20	40	12:00	1.00	40	80	30	30	30*	30	30	40
x	11:00	40	40	30	30	20	20	30	40	12:00	40	80	30	30	30	30	20	40	1:00	2:00	40	80	30	30	30	30	30	40
00	12:00	40	40	30	30	20	30	30	40	1:00	40	80	30	30	30	30	30	40	2:00	3:00	40	80	30	30	30	30	30	40
<b>00</b>	1:00	40	40	30	30	30*	30	30	40	2:00	40	80	30	30	30	30	30	40	3:00	4:00	40	80	30	30	30	30	30	40
90	2:00	40	40	30	30	30	30	30	40	3:00	40	40	30	30	30	30	30	40	4:00	5:00	40	40	20	30	30	30	30	40
0	3:00	40	40	30	30	30	30	30	40	4:00	40	40	20	30	30	30	30	40	5:00	6:00	40	30	12	20	30	30	30	40
0	4:00	40	40	30	30	30	30	30	40	5:00	40	40	15	20	30	30	30	40	6:00	7:00	30	20	10	15	30	30	30	40
0	5:00	40	40	20	20	30	30	30	40	6:00	40	30	12	15	30	30	30	40	7:00	8:00	40	20	10	12	20	20	2.0*	40
ю	6:00	40	30	12	12	30	30	30	40	7:00	1 -	20	10	12	20	20	30	40	8:00	9:00	40	20	10	12	20	20	20	40
00	7:00	40	20	12	12	20	20	30	40	8:00	40	20	10	12	20	20	20	40	9:00	10:00	40	20	10	12*	15	20	20	40
00	8:00	40	20	10	10	15	30	20	40	9:00	40	20	10	10	15	20	20	40	10:00	11:00	40	20	10	10	15	20	20	40
0	9:00	40	20	10	10	115	20	20	40	10:00	40	20	10	10	15	20	20	40	11:00	12:00	40	20	10	10	12	20	30	40
00	10:00	40	30	10	10	15	15	20	40	11:00	40	20	10	10	12	15	20	40	12:00	1:00	40	20	10	10	12	15		40
00	11:00	40	40	10	10	12	15	20	40	12:00	40	30	10	10	12	15	20	40	1:00	2:00	40	30	10	10	12	12	20	40
00	12:00	40	40	12	10	12	12	20*	30	1:09	40	40	10	10	12	.12	15	40	2:00	3:00	40	40	12	10	12	12	15	40
00	1:00	40	40	12	10	12	12,	15	20	2:00	40	40	12	10	12	12	15	30	3:00	4:00	40	40	12	10	12	12	15	30
00	2:00	40	40	15	10	12	10	12	20	3:00	40	40	15	10	12	10	12	30	4:00	5:00	40	40	20	12	12	10	12	20
00	3:00	40	40	20	10	12	10	12	20	4:00	40	40	15	12	12	10	12	20	5:00	6:00	40	40	20	15	12	12	12	30
	JANUARY	ASIA FAR EAST	EUROPE	S. AFRICA	S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN		ASIA FAR EAST	EUROPE	S. AFRICA	S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN			ASIA FAR EAST	EUROPE	S. AFRICA	CARIBBEAN S. AMERICA	ANTARCTICA	NEW ZEALAND	OCEANIA AUSTRALIA	JAPAN

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides MUF during "normal" hours. "Look at next higher band for possible openings.



## Heath SA-2550 remote antenna matcher

Heathkit has always been known for being the "haven" for gadgeteers - I'm one of them, and I've always been intrigued by their various offerings.

Their latest Ham gadget is the new Remote Antenna Matcher, the SA-2550 (see **fig. 1**). Simple in design but elegant in use, this remotely tuned 40-500 pF variable capacitor can be continuously varied from the comfort of your hamshack.

The control unit is a power supply and dc rectifier with a switch that allows you to turn the capacitor either clockwise or counter-clockwise by reversing the polarity of the voltage it sends to the matching unit motor. The motor-driven capacitor moves slowly enough so that it's hard to miss the lowest point of SWR, but not so slowly that you have to wait forever for it to make its rounds. The control voltage can be sent to the remote unit either through the antenna feedline or through two control wires.

Heath designed the Remote Matcher to be compatible with their Remote Antenna Switch (see the product review on page 124 of the May, 1986 issue). If you want to use the two units together, you'll have to control the remote matcher through the two external wires because of a dc-blocking capacitor in the HA-1481; in most Amateur installations, this will be no more than a minor inconvenience. Owners of other brands of remote switches will have to check their schematics to see what configuration their units use. If you use external cable to control your remote switch, you'll be able to use the feedline to control the SA-2550. If the remote switch uses the feedline for control, you'll need to use two external wires.

#### construction

Heath should get an award for their construction manuals. My hat's off to their technical writers. While this isn't a particularly difficult kit to build, the clear, concise style of writing makes building *very* easy.

As per any kit, I highly recommend you read the manual at least twice before you even open one parts envelope. Then, I suggest you take a complete parts inventory to make sure that nothing is missing. Try stealing a muffin pan from the kitchen and use it to sort and organize all the parts. This is especially helpful with all the hardware: screws, nuts, bolts, and washers. A few extra minutes in organization will save plenty of time later on.

Construction is straightforward and really progresses quite quickly. You start with the control unit/power supply (about an hour's work) and then move on to the matcher unit chassis. Here's where it gets a bit interesting; building the capacitor proved to be a slight stumbling block for me. It wasn't the instructions or anything other than my own sloppiness. Putting all the plates of the stator and rotor together went fine, but I had my problems in getting the proper alignment between the plates. I spent a little time carefully adjusting the four alignment nuts and had the capacitor positioned exactly where it was supposed to be. (If the plates aren't properly spaced and aligned, the voltage rating will decrease and the capacitance won't be within specifications. The unit won't perform as it should and could arc over under full-power applications.)


After the capacitor was set aside, completion of the project took just about an hour more. My total time into the project was about three hours, with another ten minutes to run some resistance and voltage checks and to run the operational "smoke" test. When it was all hooked up, everything worked as expected.

Though I was impressed with the motor that Heath supplies to turn the capacitor, I was a little concerned that I hadn't left enough slack in the capacitor's rotor and that the motor would have trouble turning the capacitor. Not to worry: my guess is that the motor could probably be used to turn the Empire State Building! There's plenty of torque, with some to spare. The motor gear drive lube is specified for operation over -40 to +60 degrees.
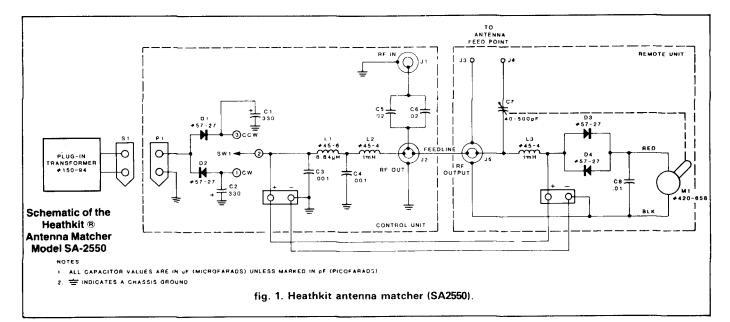
#### installation

The remote matcher is designed to be mounted at the antenna feedpoint. If you're designing a dipole, the remote matcher can be used in place of a center insulator. It's too heavy, however, to be used without support and should either be mounted on the side of a tower or suspended from a catenary wire.

Here's a typical installation you might use with the remote matcher. Cut an antenna to the middle of the 80-meter band. By formula, each leg of the dipole will be approximately 64.3 feet. (Heath recommends that you add an additional 15 percent — in this case, 9.6 feet — to the length of each leg.) Each leg of the dipole becomes 73.9 feet long. Installation proceeds as with any other dipole, except in that the remote matcher takes the place of the center insulator. When the antenna is installed, the capacitor is



used to tune out the reactive inductance of one leg of the antenna as you move away from the design frequency. This allows the transmitter to see close to a 50-ohm impedance over a wider portion of the band. This "magic" is accomplished by varying the capacitor over its tuning range and adjusting for minimum SWR.

Heath includes instructions on using the remote matcher with inverted Vs and bottom-fed verticals of both single and multi-band designs.

#### tuning and adjustment

Simply hook the remote unit up according to Heath's instructions and you're ready to go. If you have a linear amplifier, don't use it during tuning of *any* antenna; you could damage both the remote matcher and the amplifier.

Key the transmitter in CW on the bottom of the band you want to use and turn the remote capacitor until you have a minimum SWR reading. It's a good idea to tune up the whole band and make yourself an SWR chart to refer to so that you'll know approximately what SWR you're looking for as the antenna nears resonance.

Quoting from Heath's instruction manual: when the antenna is properly tuned at the low end of the band, with the Antenna Matcher adjusted for minimum SWR, the Variable capacitor should be between 2/3 and 3/4 meshed. You do not want a situation where the capacitor is either fully closed or fully open. If the capacitor is fully closed when tuned for the low end of the band, the antenna is too long. On the other hand, if the capacitor is fully open at the high end of the band, the antenna is too short.

#### other applications

With the addition of a tapped coil and relays, you can use the Remote Matcher as a multi-band tuner. Consider the application discussed by Jack Belrose, VE2CV, in a *ham radio* article ("The Half-Delta Loop") in May, 1982. In a follow-up article written with Doug DeMaw and published in *QST* (September, 1982), the idea was further pursued, with actual on-the-air testing. The antenna was fed with a remotely tuned LC network (with variable C and tapped L — see fig. 2). The problem in replicating this antenna was locating a suitable remotely tuned capacitor. The SA-2550 seems to be designed with this project in mind.

Using a tuning network with the same configuration, you can tune a variety of different antennas for full- and multi-band performance. Folded uni-poles, base-fed verticals, Bob-tail Curtains, and loops of all kinds are just a few of the examples of antennas that can be used with this remotely controlled capacitor.

While not inexpensive (\$149.95), the Heath SA-2550 represents a great value for anyone who's looking for a way of remotely tuning antennas. I had fun with this project and look forward to trying out all my antenna ideas before too much snow flies. See you on the bands!

Circle #301 on Reader Service Card.





Barry Electronics Commercial Radio Dept. offers the Best in two-way communications for Businesses, Municipalities, Civil Defense, Broadcasting Companies, Hospitals, etc. Sales and Service for all brands: Maxon, Yaesu, Icon, Tad, Octagon, Regency/Wilson, Midland, Standard, Uniden, Shinway, Fujitus, Seas, Spillsbury, Neutec, etc. Call or write for information. 212-925-7000.







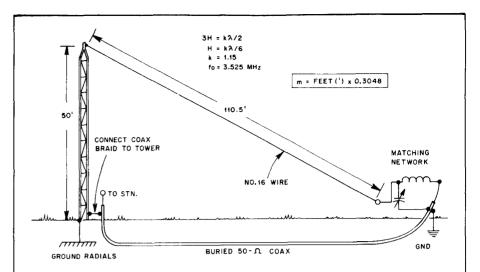

 

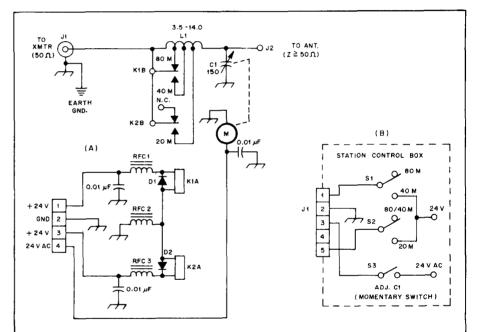


fig. 2B. Three-band L-network matches half-delta loop to 50-ohm cable. (Reprinted with permission from QST, September, 1982, page 31.)



#### packet repeater controllers

Pac-Comm has announced the release of its new DR-series of packet repeater controllers. The DR-200 dual-port controller provides an inexpensive, off-the-shelf packet switch to move traffic on inter-LAN networks. The DR-100 provides basic, single-port controller capability in a ruggedized package at low cost, and is well suited to applications in which a single-frequency repeater is appropriate.

Both units share the same digital design, which provides a Z80 CPU with up to 32k bytes of EPROM program storage and up to 32k bytes of RAM for buffering, configuration parameters, and other functions. Packet HDLC operations are handled by a Z8530 Serial Communications Controller.

The DR-200 has two independent 300/1200 baud modems using the AMD 7910 World Chip<sup>™</sup> modem. Each modem channel also has a standard disconnect header for accessory modems. Both channels have PTT line time-out-



timers and the CPU has a watchdog timer. Both models support two methods for communication with external terminals.

Several versions of dual-port software adapted to the DR-200 are available through Pac-Comm. The "Dual-Port Digipeater" program written by Jon Bloom, KE3Z, uses an easily-implemented routing algorithm based on default SSID's and an explicit routing table. The single- or dual port version of the "AX.25 Level 3 Packet Switch" program by Howie Goldstein, N2WX, is available for both the DR 100 and DR 200. The other single-port program is an adaptation of Pac-Comm's Version 1.1.3 that provides standard AX.25 Level 2, Version 2 digipeater support. All software has been enhanced to utilize the optional serial ports for setting site specific parameters. Any one of these programs may be selected with the purchase of a Pac-Comm dig ital controller and will be provided at no charge; additional copies are available for the cost of reproduction and documentation

At presstime, the DR-100 Single Port was priced at \$79.95 (kit) and \$99 (assembled). The DR-200 Dual-Port was priced at \$139.95 (kit) and \$159.95 (assembled); final prices may be subject to variation because of changes in the semiconductor market.

For complete details, contact Pac-Comm Packet Radio Systems, Inc., 3662 West Cypress Street, Tampa, Florida 33607.


Circle #302 on Reader Service Card.
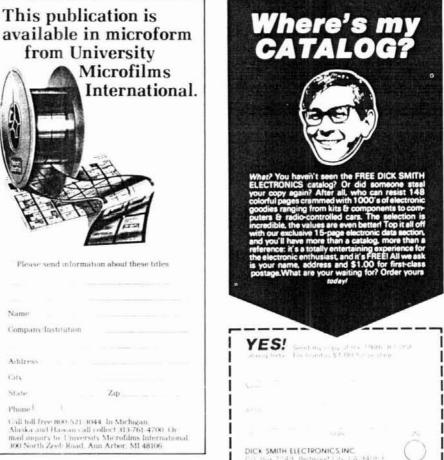
## ICOM IC-03AT 220-MHz handheld

ICOM has announced the release of the IC-03AT, a new 220 MHz counterpart to its IC-02AT and IC-04AT top of the line handhelds.










**1987** Ham Radio Photo Wall Calendar Your daily reminder of radio events... Great for home, office, shack,

or as a gift!

J Now, a calendar for radio hams! Operating events, times radio history dates, plus 10 pages of reference data. B/w photo for each month shows excitement of ham radio to all! Calendar is 11x17" (unfolded) and spiral bound to hang flat. Allow 2 weeks ARO Send \$9.95(U.S., VE, XE) \$14.00 for DX Write for discounts starting quantity of 5

KB1T Box 1015-H Amherst, NH 03031

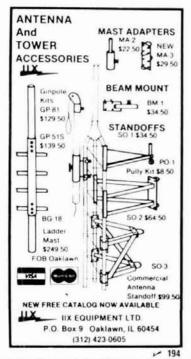

CADDELL COIL CORP. Constant of the second se

eration (See ARRL Handbook pages 6.20 for construction details.)	
100 Watt (4 1.6.1.9.1. or 1.1 Impedence - selectione)	\$10.50
Universal Transmatch LKW (4.1 impedence)	14.50
Universal Transmatch 2 KW (4-1 Impedence)	17.00
Universal Transmatch LKW (6-1-9-1, or 1-1 - selectione)	16.00
Universal Transmatch 2 KW (6-1.9-1. ur.1.1. selectione)	18.50
Please send large SASE for into	

the antenna. They are designed for 3.30 MHz on

flea t ..... market

PACKET PROGRAM FOR YOUR PC. A telecommunications

program especially written to interface your packet controller with your PC or compatible. Features Split Screens, ASCII, Binary, X. Modern file transfers. DOS shell. Macro Keys. 5 types time/date/oper. ID. Lots of goodies. Software support. Write for complete information. VISA/MC, Kalt and Associates, 2440 E. Tudor Rd, Suite #138, Anchorage, AK 99507 (907) 248.0133

REMEMBER TROLLEY CARS? Trolley Treasures. "The War time Years in New Jersey" (1939-1947), a 4 volume pho todocumentary history, includes 1600 unpublished, original photographs plus extensive historical notes. Volume 1, "The Compromise Roof Cars of Public Service Coordinated Trans port", ready now. For details, or to order, contact. Trolley Themes, A W. Mankoff, 2237.3 Woodside Lane, Sacramento, CA 95825, (912-95 plus \$1:50 StH1).

WANTED: Tube Hif i Equipment, loudspeakers, magazines Anything relating to 1950's HiFi, Jack Smith, 288 Winter Street, N. Andover, MA 01845

WANTED: Military Surplus Radius: We need Collins 6181, ARC 94, ARC 102, ARC 114, ARC 115, ARC 116, ARC 159, RT 1167 or RT 1168, ARC 164, RT 1299, ARC 186, ARN 118, RT 1159 A, MRC 95, 718F-12, PRC 25, PRC 66, PRC 70, PRC 77, RT 524 V/RC, Antenna Gouplers 4901 1, 4901 9 CU1658A ARC, CU1659, GRC 4150 need munt.R + KWM 2A 516F 2, 312 5, 30L 1, 302C 3 and World War II unmoduled Collins equipment. Top dollar paid or trade for new Amateus gear Write or phone Bill Slep, 704 524 7519, SLEP ELECTRON ICS COMPANY, Highway 441, Otto, NC 28763

RF POWER METER: 01-12.4 GHz Narda 8440 \$95. Heath Gred Dip meter \$15. Comco remote base, outside cabinet, perfect for repeater \$75. K6K21, 2255 Alexander, Los Osos, CA 93402

SOLAR ELECTRIC panels and system components. 1st quality Accorpanels with 10 year warranty. Lowest prices in country. Catalog 51:00 KAROSS, Radiant Distributors, 3900 Dursiam Adam MI 49301. (616) 874-8899.

FOR SALE: Healthist SB 104 \$200, SB 604 w px 576, SB 644 vtp 545, SB 634 consule 545, HW 2036A 2m 5100, Kenwood B, 1000 5130, Consir 2m 530, All equipment in good condition NV0R, 1205 North Mart. O'Fallon, MO 63366

10 WATT HF linear amplifier kit. For infu SASE to: A Ir A Engineering, 2521 W. LaPalma Ave, #K. Anaheim. CA 92801 (714) 957-2114.

MICROWAVE VCOs, Watkins Johnson V901, 3.6 GHz to 5.0 GHz, 535 postpaid. Send SASE for more into. Stanley Bode, 2248 Lockwood, Carrollton, TX 75007.

FOR SALE: Hy Gain #389 Antenna, Tri Ex W 51 Tower A. Gail van, 4808 Bergenline Avenue, Union City, NJ 07087 (201) 864-4881

FOR SALE: Collers Equipment: KWM 2 and 30L1 1 KW. Complete with power supply: 110V and 220V. SM 2 Fix sta. Dynamic Mic: Ivoice control carned: Collins Speaker equip for phone patch Quad Ant 80-40-20 10 meters, Carrying cases. Samsonite for KWM-2 and 30L 1 Amp. Complete with instructions by Collins. Complete with instructions by US GM. (FRC 93, TM 11-5820-554). Mobile Mount: MP.1 (new not used). Mobile priver sup 35: D2 (new not used). Mobile Opnamic Mic. MM 1 (new not used). The equipment above in excellent condition. Will self complete for \$1,000. Oc Contact William J. Maida, 274 W. Sabal Palm PL. Congreson, FL 32779 or phone 305 893 6138.

HOMEBREW PROJECTS, List SASE, PO Box 708, East Hamp ton, NY 11937

DRAKE TR-7, power supply, SB filter, N.B., desk mic, mint, complete with manuals. \$850.00 plus UPS\_K5MEC, 4 Sombrero Lane, St. Rose, LA 70087

UHF PARTS. GaAs Fets, MMICs, tranmers, chip caps, tellion pcb, and other builder parts. SASE trangs list. Microwave Components, 11216 Cape Cod, Taylor, MI 48180

SIGNAL ONE, CX7 B, w spare final, maintenance manual \$850.00 plus UPS\_K5MEC, 4 Sombrero Late. St. Rose, LA 20087

LASERS: Illustrated how to manual on Ham Radie use of lasers 112 bound pages of practical information, plans, schematics, photos, sources of invesperiave parts \$13.95 ppd. S. Noll, 1288 Winford, Ventura, CA 93004

APPLE II%/c/e Morse Code Program menus. 18 modes, les son plans, graphics, word processor. 1.100 wpm, etc. Write LARESCO, PO Box 2018, 1200 Bing Rd, Calumet City. II. 60409 (312):891-3279

SPECIAL ANTENNAS by K30PW featuring the RIW 19.432 MHz beam. 14.9.0Bd for 969.95 and the K1FO 22 et 14.11.432 MHz beam. 15.8.dBd for \$76.64, SASE for information. The macht. Rotland. 12/03 Warrer St. New Comberland, PA.17070

SSSSSUPER SAVINGS on electronic parts, components, supplies and computer accessories. Free 40 page catalog for SASI, Get on our making lot. BCU ELECTRO, PD Box 830119. Re-traid son: T.X. 75083 or call (214) 690-1102. CABLE TV CONVERTERS & EQUIPMENT: Plans and parts Build or buy SASE for information. C & D Electronics, PO Box 1402, Dept. HR, Hope, AR 71801.

YAESU OWNERS: Hundreds of modifications and improve ments for your rig. Select the best from fourteen years of gen ume for rated Fox. Lango Newsletters by using our reev 32 page Cumulative Index. Only 55 postpaid (eash or check) with 54 Re bate Certificate creditable toward Newsletter purchases. Includes famous Fox. Lango Filter and Accessories Lists. Milt Lowerss, N4ML (Editor). Box 15944, W. Palm Beach, FL 33416. Telephone (305) 683 9887.

MARCO: Medical Amateur Radio Council, Ltd. operates daily and Sunday nets. Medically oriented Amateurs (physicians, den bsts, veterinarians, nurses, physiotherapiets, lab technicians, etc. I invited to join. Presentity over 550 members. For information write MARCO, Box 73%, Acme, PA 15610.

IBM-PC RTTY/CW. New CompRity II is the complete RTTY/CW program for IBM PC's and compatibles. Now with larger buffers, better support for packet units, pictures, much more. Virtually any speed ASCII, BAUDOT, CW. Text entry so built in screen editor! Adjustable split screen display. Instant mode speed change. Handcopy, diskcopy, break-in buffer, se lect calling, text file transfer, customizable full screen logging, 24 programmable 1000 character messages Ideal for MARS and taffic handling. Requires 2569 PC or AT compatible, senal port, RS-232C TU 365. Send call letters functuding MARS) with or de. David A. Rice, KC2HO, 25 Village View Bluff. Baltston Lake, NY 12019.

ELECTRONIC ENCLOSURES: Attractive, reasonably priced Aluminum top and sides. Walnut staned solid would ends. Vanety of sizes and custom sizes available. Sample \$5,00 Intomation free Energy Engineering. Custom Division. Bt. 4. Bio, 330. Engenteriate. AR 72701.

NATIONAL RADIO EQUIPMENT manual list or NCL 2000 parts kits. SASE Maximilian Eachs: 11 Plymouth Lane, Swampscott, MA 01907

RTTY JOURNAL—Now in near 34th year. Join the circle of RTTY friends from all over the world. Year's sobscription to RTTY JOURNAL, 5100 foreign 515:00 Send for RTTY JOUR NAL 9085 to Casta Ave. Fountair Valley, CA 92708

IMBA International Mission Radio Association helps mission aries Equipment loaned. Wieckday net, 14:280 MHz, 2:3 PM Eastern Eight bundred Anatoxis in 40 countries. Brother Hey, 1. Pryer Manuel Road. Lanchmond. New York 10538.

RUBBER STAMPS: James 34 50 PPD. Send check or MD to G-L. Pierce, 5521 Britchie Way, San Diego, CA 52117, SAST brings information

ELECTRON TUBES: Receiving, transmitting, microwave all types available: Large stock. Next day delivery, most cases. Daily Electronics, PO Box 5029. Compiliar, CA 90224. (213):774-1255.

CUSTOM MADE EMBROIDERED PATCHES, Any stare, shape colors. Eve patch minimum. Free sample, prices and ordering information. Here Specialties, lor., Dept 301, 4202 N. Dcake Chicago, II. 60618

RECONDITIONED TEST EQUIPMENT \$1.25 for catalog Walter, 2697 Nickel San Pablo CA 94806

CABLE TV CONVERTERS/DESCRAMBLERS. Guaranteed lowest proces in US Jerrold, Hamlin, Zeroth, Many others Lowest dealer proceel Orders shipped within 24 hours! Master card, VISA, COD accepted Free Catalog, call (800) 345,8927, only Pacific Cable Co., Inc., 7325 1, 2 Reseda Blvd, #1020, Rese da, CA 91335, 1818,716,5914.

WANTED: Heath ET 100 Call 913 898 4695 Mike W0XM

MORSE CODE Practice program for IBM PC and Compatibles. Send \$19.95 check to SP Microcomputing Co., 1008 Swallow Drive, Cherry Hill, NJ 08003, Developed by KD25M

## COMING EVENTS Activities — "Places to go . . ."

PENNSYLVANIA: JANUARY 18 Amateur Radio Brunch. The Chaverim of Delaware Valley will hold their 7th annual brunch. Parktowne Place Apartment Complex, 2008 Benjamin Frankler Parkway. Philadelphia at 10 AM. Everyone invited. Contact Bill Soble. W30XT (215): 676-6769 or write to 9357 Hott Street, Philadelphia PA 19115. Reservations are becessiry.

SOUTH BEND, INDIANA Hamtest Swap & Shop, January 4 1987, Irist Sunday after New Year's Day, Century Center down town on US 33 Oneway North Instween 51. Joseph Bark Bildy and triver Four Jane heijtways in duor from all dries borns. Tables 55.5.6. Round 510. 8x2 5. Rectangular, 52,61. wall losations Talk in treg. 52.52, 99.39, 93.33, 69.09, 145-29. K0IX1 (219) 233.5307.

# OPERATING EVENTS

January 20: Mission Trail Net will celebrate as 50th annour sary. MTN meets on 3928 kHz every night at 7 PM Pacific term Desident Harry Edwards. NGESU: tais revited all old time Mession Trail Net members to visit MTN during the remoth of January to say Hi to old thends.

Feb 1-2: YL-ISSB OSO Parties: CW 00012 to 23597. Phone 00012 March 21 to 23592 March 22. Open to at 31.5. Fareward Class performs of bands. Evolution could report. ODIT usane, 5558 roomber and partner or transmittle. Certificates to category, court by state winness. For information. BitLath WAGAEA, PO Box 401. McTeory, TL 60260.0001. USA.



The IC-03AT features 220-224.995-MHz coverage, an LCD readout, DTMF, 2.5-W output (5W optional), ten memories, memory scan, program scan, and 32 built-in subaudible tones. It comes with an IC-BP3 rechargeable battery pack, AC wall charger, belt clip, wrist strap, and earphone.

For information, contact ICOM America, Inc., 2380 116th Avenue N.E., Bellevue, Washington 98009-9029.

Circle #303 on Reader Service Card.

#### 1.3-GHz shirt-pocket frequency counter

OPTOelectronics, Inc. has introduced the model 1300H frequency counter. With an anodized aluminum cabinet measuring only 3-1/2 x 4 x 1 inches, the new unit includes selfcontained, rechargeable Ni-Cad batteries, a signal measurement range of 1 MHz to over 1.3 GHz, 8 red 0.28-inch high LED digits, and a BNC signal input connector. Switches are provided for AC or battery operation, fast or slow gate time, high or normal sensitivity and range select: 1-500 MHz or 500-1300 MHz. Resolution to 1 kHz in 0.25 seconds or 100 Hz in 2.5 seconds over the entire range. Accuracy to  $\pm 1$  count LSD is achieved with an RTXO time base. Additional features include a "measurement in progress" indicator, calibration adjustment without the need to open the case, and excellent sensitivity.

Priced at \$150, the 1300H comes equipped with internally installed Ni-Cad batteries and a 110 VAC/9 VDC adapter for AC operation and charging batteries. Optional accessories include a carrying case, probe and telescoping antenna.

For details, contact OPTOelectronics, 5821 NE 14th Avenue, Fort Lauderdale, Florida 33334. Circle /304 on Reader Service Card.

Circle 1304 on Reader Service Card.

#### C-band/Ku-band receiver

Luxor North America Corporation has introduced the 9993 C/Ku Receiver, a new mid-line block satellite receiver. Decoder-compatible, it's designed to give optimum performance on both C-band and Ku-band.

It has a crisp, bright green front panel LED for display of all basic functions, built-in remote antenna control with three-digit display and a digital signal strength meter.

The 9993 is easily operated by a hand-held, 35-key, full-function, remote control. A threedigit code for lock-out of undesirable channels is controlled via the remote unit. Built-in remote polarity control offers convenience; non-volatile memory is unaffected by power loss.

Video features include functional compatibil-

ity with most popular signal decoders, and an optimal TI (terrestrial interference) filter operable by remote control. Built-in AFC maintains optimum signal reception on each channel; finetuning can be executed from the remote. The 9993 also has outputs for both tv set and monitor.

Audio features include monaural, discrete, and matrix stereo formats, a three-digit display to indicate tunable audio frequencies, wide and narrow bandwidth switchability, and volume control and muting from the hand-held remote.

For details, contact Luxor North America Corporation, 600 108th Avenue N.E., Suite 539, Bellevue, Washington 98004.

Circle #305 on Reader Service Card.


#### plug-in CTCSS for handhelds

Communications Specialists, of Orange, California, is currently expanding their line of programmable CTCSS tone equipment that will plug directly in to many popular two-way radios. Two recent additions to this line — adapter kits for the Standard Communications and TAD USA handhelds — utilize the new TS-32HB hybrid-sized encoder-decoder. The Standard 734L/834L may now use a TS-32HBL (low profile) encoder-decoder and a 01-1030 adapter plug. The TS32HBL is priced at \$64.95 and the 01-1030 adapter is \$7.50.

The TAD M1520-454 uses the TS32HBH (high profile) encoder-decoder and 01-1031 adapter plug. The TS32HB used in these applications employs the popular DIP switch programmability first introduced in 1979 with the company's larger TS-32. The TS32HB uses state-of-the-art hybrid packaging to obtain its small size. A crystal-controlled clock oscillator provides stability under all conditions, and sensitivity is rated at 6mv RMS for use with the lowest output receivers. The adjustable sinewave output is accurate to within  $\pm 0.5$  Hz at a level of 6 volts peak-to-peak across 10k.

For details, contact Communications Specialists, Inc., 426 West Taft Avenue, Orange, California 92665-4296.

Circle #306 on Reader Service Card.

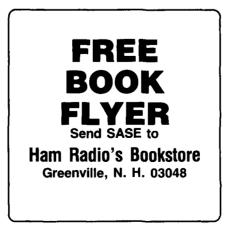

# RF TRANSISTORS

P/N	<b>2-30 MF</b> Ratin	<b>iz 12V (*</b> ⊧ Ia	≈ <b>28V)</b> Each	Match Pr.
MRF412,/A	801		18.00	45.00
MRF421	Q 100\	N	22.50	51.00
MRF422*	150\		38.00	82.00
MRF426,/A* MRF433	25		18.00	42.00
MRF433 MRF449,/A	12.51 Q 301		12.00 12.50	30.00 30.00
MRF450,/A	Q 50\		14.00	31.00
MRF453,/A	Q 60\	N	15.00	35.00
MRF454,/A	Q 80\		15.00	34.00
MRF455,/A MRF458	Q 60\ 80\		12.00 20.00	28.00 46.00
MRF475	12		3.00	9.00
MRF476	31		2.75	8.00
MRF477 MRF479	40\ 15\		11.00 10.00	25.00 23.00
MRF485*	15\		6.00	15.00
MRF492	Q 90\		16.75	37.50
SRF2072	Q 65		13.00	30.00
SRF3662 SRF3775	Q 110\ Q 75\		25.00 14.00	54.00 32.00
SRF3795	Q 901		16.50	37.00
CD2545	50		23.00	52.00
SD1487	Q 100		36.00	76.00
2SC2290 2SC2879	60V Q 100V		15.00 25.00	36.00 56.00
				Available
	VHF/UHF	TRANSI	STORS	
ŀ	Rating	MHz	Net Ea.	Match Pr.
MRF212	10Ŵ	136-174	\$16.00	_
MRF221 MRF222	15W 25W	136-174 136-174	10.00 14.00	_
MRF222	25W 40W	136-174	13.50	32.00
MRF237	4W	136-174	3.00	-
MRF238	30W	136-174	13.00	30.00
MRF239 MRF240	30W 40W	136-174 136-174	15.00 18.00	35.00 41.00
MRF240 MRF245	40 W	136-174	28.00	65.00
MRF247	75W	136-174	27.00	63.00
MRF260	5W	136-174	7.00	_
MRF261 MRF262	10W 15W	136-174 136-174	9.00 9.00	-
MRF264	30W	136-174	13.00	
MRF607	1.75W	136-174	3.00	-
MRF641	15W	407-512	22.00	49.00
MRF644 MRF646	25W 40W	407-512 407-512	24.00 26.50	54.00 59.00
MRF648	60W	407-512	33.00	69.00
SD1441	150W	136-174	74.50	170.00
SD1477 2N3866*	100W 1W	136-174 30-200	32.50 1.25	78.00
2N3600 2N4427	1W	136-174	1.25	_
2N5591	25W	136-174	13.50	34.00
2N6080	4W	136-174	7.75	-
2N6081 2N6082	15W 25W	136-174 136-174	9.00 10.50	_
2N6083	30W	136-174	11.50	24.00
2N6084	40W	136-174	13.00	31.00
			MODUL	
MRF134	\$16.00	SAV6 SAV7		\$32.50
MRF136 MRF137	21.00 24.00	SAV/ S10-		30.00 13.50
<b>MRF138</b>	35.00	2SC1	075	25.00
MRF140	89.50	2SC1		5.00
MRF150 MRF172	89.50 62.00	2SC1	1946A	12.00 3.00
MRF174	80.00	2SC2		10.00
2N1522	7.95	2SC2		20.00
2N4048 NE41137	7.20 3.50	2SC2	2289 2312C	22.00 4.00
2N5590	11.00	23C2 2N59		10.00
2N5642	14.00	2N59		13.00
Selected, mat	ched final	is for Icon	h Atlas Y	aesu Ken
wood, Cubic, 1	TWC, etc. T	echnical a	assistance	and cross-
reference on (				
WE SHIP			all for quo	
			ty Dollars	SAINIC
		744.07		





## California

JUN'S ELECTRONICS 3919 SEPULVEDA BLVD. CULVER CITY, CA 90230 213-390-8003 800-882-1343 Trades Habla Espanol

## Colorado

COLORADO COMM CENTER 525 EAST 70th AVE. SUITE ONE WEST DENVER, CO 80229 (303) 288-7373 (800) 227-7373 Stocking all major lines Kenwood Yaesu, Encomm, ICOM

## Connecticut

HATRY ELECTRONICS 500 LEDYARD ST. (SOUTH) HARTFORD, CT 06114 203-527-1881 Call today. Friendly one-stop shopping at prices you can afford.

## Delaware

AMATEUR & ADVANCED COMMUNI-CATIONS 3208 CONCORD PIKE WILMINGTON, DE 19803 (302) 478-2757 Delaware's Friendliest Ham Store.

#### DELAWARE AMATEUR SUPPLY

71 MEADOW ROAD NEW CASTLE, DE 19720 302-328-7728 800-441-7008 Icom, Ten-Tec, Microlog, Yaesu, Kenwood, Santec, KDK, and more. One mile off I-95, no sales tax.

## Florida

AMATEUR ELECTRONIC SUPPLY 1898 DREW STREET CLEARWATER, FL 33575 813-461-4267 Clearwater Branch West Coast's only full service Amateur Radio Store. Hours M-F 9-5:30, Sat. 9-3

AMATEUR ELECTRONIC SUPPLY 621 COMMONWEALTH AVE. ORLANDO, FL 32803 305-894-3238 Fla. Wats: 1 (800) 432-9424 Outside Fla: 1 (800) 327-1917 Hours M-F 9-5:30, Sat. 9-3

## Georgia

DOC'S COMMUNICATIONS 702 CHICKAMAUGA AVENUE ROSSVILLE, GA 30741 (404) 866-2302 / 861-5610 ICOM, Yaesu, Kenwood, Bird... 9AM-5:30PM We service what we sell.

## Hawaii

HONOLULU ELECTRONICS 819 KEEAUMOKU STREET HONOLULU, HI 96814 (808) 949-5564 Kenwood, ICOM, Yaesu, Hy-Gain, Cushcraft, AEA, KLM, Tri-Ex Towers, Fluke, Belden, Astron, etc.

## Idaho

ROSS DISTRIBUTING COMPANY 78 SOUTH STATE STREET PRESTON, ID 83263 (208) 852-0830 M 9-2; T-F 9-6; S 9-2 Stock All Major Brands Over 7000 Ham Related Items on Hand

## Illinois

ERICKSON COMMUNICATIONS, INC. 5456 N. MILWAUKEE AVE. CHICAGO, IL 60630 312-631-5181 Hours: 9:30-5:30 Mon, Tu, Wed & Fri; 9:30-8:00 Thurs; 9:00-3:00 Sat.

## Indiana

Ham Radio's guide to help you find your loca

THE HAM STATION 220 N. FULTON AVE. EVANSVILLE, IN 47710 812-422-0231 Discount prices on Ten-Tec, Cubic, Hy-Gain, MFJ, Azden, Kantronics, Santec and others. SASE for New & Used Equipment List.

## Maryland

MARYLAND RADIO CENTER 8576 LAURELDALE DRIVE LAUREL, MD 20707 301-725-1212 Kenwood, Ten-Tec, Alinco, Azden. Full service dealer. T-F 10-7 SAT 9-5

## Massachusetts

TEL-COM, INC. 675 GREAT ROAD, RTE. 119 LITTLETON, MA 01460 617-486-3400 617-486-3040 The Ham Store of New England You Can Rely On.

## Michigan

ENCON PHOTOVOLTAICS Complete Photovoltaic Systems 27600 Schoolcraft Rd. Livonia, Michigan 48150 313-523-1850 Amateur Radio, Repeaters, Satellite, Computer applications. Call Paul WD8AHO

## Minnesota

TNT RADIO SALES 4124 WEST BROADWAY ROBBINSDALE, MN 55422 (MPLS/ST. PAUL) TOLL FREE: (800) 328-0250 In Minn: (612) 535-5050 M-F 9 AM-6 PM Sat 9 AM-5 PM Ameritron, Bencher, Butternut, ICOM, Kenwood

### Missouri

MISSOURI RADIO CENTER 102 NW BUSINESS PARK LANE KANSAS CITY, MO 64150 (800) 821-7323 Missouri: (816) 741-8118 ICOM, Kenwood, Yaesu Same day service, low prices.

**Dealers:** YOU SHOULD BE HERE TOO! Contact Ham Radio now for complete details.

## mateur Radio Dealer

#### Nevada

AMATEUR ELECTRONIC SUPPLY 1072 N. RANCHO DRIVE LAS VEGAS, NV 89106 702-647-3114 Dale Porray ''Squeak,'' AD7K Outside Nev: 1 (800) 634-6227 Hours M-F 9-5:30, Sat. 9-3

#### **New Hampshire**

RIVENDELL ELECTRONICS 8 LONDONDERRY ROAD DERRY, N. H. 03038 603-434-5371 Hours M-S 10-5; THURS 10-9 Closed Sun/Holidays

#### New Jersey

**KJI ELECTRONICS** 66 SKYTOP ROAD CEDAR GROVE, NJ 07009 (301) 239-4389 Gene K2KJI Maryann K2RVH Distributor of: KLM, Mirage, ICOM, Larsen, Lunar, Astron. Wholesale - retail. QEP's 110-4 ROUTE 10 EAST HANOVER, N. J. 07936 201-887-6424 In N.J. 1-800-USA-9913 **Bill KA2QEP** Jim N2GKW VISA/Mastercard **Belden** Coaxial Cable Amphenol Connectors Hours: 9:30 am-7:00 pm

#### **New York**

BARRY ELECTRONICS 512 BROADWAY NEW YORK, NY 10012 212-925-7000 New York City's Largest Full Service Ham and Commercial Radio Store.

VHF COMMUNICATIONS 915 NORTH MAIN STREET JAMESTOWN, NY 14701 716-664-6345 Call after 7 PM and save! Supplying all of your Amateur needs. Featuring ICOM "The World System." Western New York's finest Amateur dealer.

### North Carolina

F & M ELECTRONICS 3520 Rockingham Road Greensboro, NC 27407 1-919-299-3437 9AM to 7PM Closed Monday ICOM our specialty — Sales & Service

### Ohio

#### AMATEUR ELECTRONIC SUPPLY 28940 EUCLID AVE.

WICKLIFFE, OH44092 (Cleveland Area) 216-585-7388 Ohio Wats: 1 (800) 362-0290 Outside Ohio: 1 (800) 321-3594 Hours M-F 9-5:30, Sat. 9-3

#### DEBCO ELECTRONICS, INC.

3931 EDWARDS RD. CINCINNATI, OHIO 45209 (513) 531-4499 Mon-Sat 10AM-9PM Sun 12-6PM We buy and sell all types of electronic parts.

UNIVERSAL AMATEUR RADIO, INC. 1280 AIDA DRIVE REYNOLDSBURG (COLUMBUS), OH 43068 614-866-4267 Featuring Kenwood, Yaesu, Icom, and other fine gear. Factory authorized sales and service. Shortwave specialists. Near I-270 and airport.

#### Pennsylvania

HAMTRONICS, DIV. OF TREVOSE ELECTRONICS 4033 BROWNSVILLE ROAD TREVOSE, PA 19047 215-357-1400 Same Location for over 30 Years

LaRUE ELECTRONICS 1112 GRANDVIEW STREET SCRANTON, PENNSYLVANIA 18509 717-343-2124 ICOM, Bird, Cushcraft, Beckman, Larsen, Amphenol, Astron, Belden, Antenna Specialists, W2AU/W2VS, Tokyo Hy-Power Labs, WELZ, Daiwa, Sony, Saxton, Vibroplex, Weller.

### Tennessee

MEMPHIS AMATEUR ELECTRONICS 1465 WELLS STATION ROAD MEMPHIS, TN 38108 Call Toll Free: 1-800-238-6168 M-F 9-5; Sat 9-12 Kenwood, ICOM, Ten-Tec, Cushcraft, Hy-Gain, Hustler, Larsen, AEA, Mirage, Ameritron, etc.

### Texas

#### MADISON ELECTRONICS SUPPLY

3621 FANNIN HOUSTON, TX 77004 713-520-7300 Christmas?? Now??

#### KENNEDY ASSOCIATES

AMATEUR RADIO DIVISION 5707A MOBUD SAN ANTONIO, TX 78238 Stocking all major lines. San Antonio's Ham Store. Great Prices — Great Service. Factory authorized sales and service. Hours: M-F 10-6; SAT 9-3

#### **MISSION COMMUNICATIONS**

11903 ALEIF CLODINE SUITE 500 (CORNER HARWIN & KIRKWOOD) HOUSTON, TEXAS 77082 (713) 879-7764 Now in Southwest Houston—full line of equipment. All the essentials and extras for the "ham."

#### Wisconsin

AMATEUR ELECTRONIC SUPPLY 4828 W. FOND DU LAC AVE. MILWAUKEE, WI 53216 414-442-4200 Wisc. Wats: 1 (800) 242-5195 Outside Wisc: 1 (800) 558-0411 M-F 9-5:30 Sat 9-3



Includes all Current, Obsolete, Antique, Hard-To-Find Receiving, Broadcast, Industrial, Radio/TV types. **LOWEST PRICES,** Major Brands, In Stock.

UNITY Electronics Dept. H P.O. Box 213 Elizabeth, NJ 07206



Your COMPLETE Packet Source making Packet Radio as easy as 1-2-3



#### ADVERTISER'S INDEX AND READER SERVICE NUMBERS

Listed below are the page number and reader service number for each company advertising in this issue. To get more information on their advertised products, use the bind-in card found elsewhere in this issue, select the correct reader service number from either the ad or this listing, check off the numbers, fill in your name and address, affix a postage stamp and return to us. We will promptly forward your request to the advertiser and your requested information should arrive shortly. If the card is missing, send all the pertinent information on a separate sheet of paper to: ham radio magazine, Attn: Reader Service, Greenville, NH 03048.

ADER SERVICE #	PAGE #
108 - Advanced Computer Controls, Inc	
176 - Advanced Receiver Research	
_149 - AEA	
178 - All Electronics Corp	
Amateur Electronic Supply	
197 - Amateur Wholesale Electronics 137 - Amidon Associates	
	53
_177 - AMSAT 115 - Antennas, Etc.	
165 - Antique Radio Classified	
128 - ARRL 167 - Astron Corp	
- Barker & Williamson	
Barry Electronics	
181 - Bilal Company	
134 - BMA Software	
182 - Buckmaster Publishing	
191 - Buckmaster Publishing	
186 - Burghardt Amateur Center	
Butternut Electronics	terreter to the second s
Caddell Coil Corp	
196 - California Packet Concepts	
192 - Coaxial Dynamics, Inc.	
116 - Communication Concepts, Inc	
198 - Communications Specialists	
_185 - CTM	
Dayton Hamvention	
Dick Smith Electronics	
180 Digitrex	
151 - Doppler Systems	
187 - Down East Microwave	
Engineering Consulting	
124 - Fair Radio Sales	
131 - Fluke Manufacturing Co	
* - Fox Tango Corp	
125 - GLB Electronics	
152 - H.L. Heaster, Inc.	
111 - HAL Communications Corp	
113 Hal-Tronix	
143 - Ham Radio Outlet	
* - Ham Radio's Bookstore .38, 49, 72	
* - Hamtronics, NY	
* Hamtronics, PA	
105 · ICOM America, Inc	
194 - IIX Equipment Ltd	
122 - Jensen Tools, Inc	
190 - Kagil	
106 - Kantronics	
* - KB1T Radio Specialties	
Trio-Kenwood Communications	
118 - Kiron Corporation	
156 - Larsen Antennas	
114 - Madison Electronics Supply	
175 - Glen Martin Engineering, Inc	
146 - The Meadowlake Corp	
107 - MFJ Enterprises	
138 - Micro Control Specialties	
123 - Midland Technologies	
141 - Minds Eye Publications	
109 - Mirage Communications	2.2

ADER SERVICE #	PAGE #
_ 126 - Mirage Communications	
169 - Mirage Communications	
184 - Monitoring Times	
_155 - Mosley Electronics, Inc	
135 - Motron Electronics	
127 - Multifax	
_161 - NCG	
153 - Nel-Tech Labs, Inc	
160 - Nemal Electronics	
NRI Schools	
170 - Nuts & Volts	
189 - Omega Concepts, Inc.	
144 - Optoelectronics	
* - Orlando Hamcation	40
110 - P.C. Electronics	
139 - Pac-Comm Packet Radio Systems, Inc.	
140 - Pacific Rim Communications	
119 - Palomar Engineers	
168 - Processor Concepts	
183 - Pro-Search Electronics	
121 - The PX Shack	
_164 - QEP'S	
150 - Quay Technologies	
145 - Radio Amateur Callbook	
162 - Radiokit	
171 - Radiosporting	
173 - Ramsey Electronics, Inc.	
_154 - RF Kit Co	
RF Parts/Westcom Engineering	
188 - RF Products	
_158 - S-Com	
_201 - Sias Engineering Co.	
- Spec-Com	
112 - Spectronics	
130 - Spectrum International	
117 - Stone Mountain Engineering Co	28
_166 - STV/OnSat *	
174 - Synthetic Textiles, Inc.	
200 - TAD USA	
_159 - TE Systems	
120 - Telewave, Inc.	
163 - Texas Radio Products	78
142 - Transverters Unlimited	
Tropical Hamboree	
195 - Unity Electronics	
- University Microfilm Int	
147 - Vanguard Labs	
_129 - Varian	
172 - W9INN Antennas	
157 - Webster Communications	
148 - Western Electronics	
136 - Yaesu Electronics Corp	
199 - Yaesu Electronics Corp	

#### PRODUCT REVIEW/NEW PRODUCTS

306 - Communications Specialists	
301 - Heath Company	
303 - ICOM America, Inc.	
305 - Luxor (North America) Corp	
304 - Optoelectronics	
302 - Pac-Comm Packet Radio Systems, Inc	113

\*Please contact this advertiser directly.

Please use before February 28, 1987.

Limit 15 inquiries per request.

a registered Hademork of International Business Machines Corp. 196

118 January 1987

# We Reque THE STANDARD OF EXCELLENCE Definitely Superior! AZDEN PCS-5000 COMMERCIAL - GRADE

EN DISERT TRANS

UNPRECEDENTED WIDE FREQUENCY RANGE: Covers 140.000-153.000 MHz in steps that can be set to any multiple of 5 kHz up to 50 kHz.

CAP/MARS/NAVY MARS, BUILT IN: The wide frequency range facilitates use of CAP and ALL MARS FREQUENCIES including NAVY MARS. COMPARE!

TINY SIZE: Only 2 inches high, 5½ inches wide and 7¼ inches deep!

MICROCOMPUTER CONTROL: Gives you the most advanced operating features available.

UP TO 11 NONSTANDARD SPLITS: COMPARE this with other units!

20 CHANNELS OF MEMORY IN TWO SEPARATE BANKS: Retains frequency, offset information, PL tone frequency.

DUAL MEMORY SCAN: Scan memory banks separately or together. ALL memory channels are tunable independently. COMPARE!

MEMORY SCAN LOCKOUT: Allows you to skip over channels you don't want to scan.

TWO RANGES OF PROGRAMMABLE BAND SCANNING: Limits are quickly reset. Scan ranges separately or together with independently selective steps in each range. COMPARE!

BUSY SCAN AND DELAY SCAN: Busy scan stops on an occupied channel. Delay scan provides automatic auto-resume.

DISCRIMINATOR CENTERING (AZDEN EXCLUSIVE PATENT): Always stops on frequency desired when scanning.

PRIORITY MEMORY AND ALERT: Unit constantly monitors one memory channel for signals, alerting you when channel is occupied. LITHIUM BATTERY BACKUP: Memory information can be stored for up to 5 years even if power is removed.

FREQUENCY REVERSE: Allows you to listen to repeater input frequency.

ILLUMINATED KEYBOARD WITH ACQUISITION TONE: Keys are easily seen in the dark, and actuation is positively verified audibly. CRISP, BACKLIGHTED LCD DISPLAY: Easily read no matter what the lighting conditions!

DIGITAL S/RF METER: Shows incoming signal strength and relative transmitter power.

MULTI-FUNCTION INDICATOR: Shows a variety of operating parameters on the display.

FULL 16-KEY TOUCHTONE PAD: Keyboard functions as autopatch when transmitting.

MICROPHONE CONTROLS: Up/down frequency control and priority channel recall.

PL TONE GENERATOR BUILT IN: Instantly program any of the standard PL frequencies into the microcomputer. COMPARE! TRUE FM, NOT PHASE MODULATION: Unsurpassed intelligibil-

ity and audio fidelity. COMPARE!

HIGH/LOW POWER: Select 25 watts or 5 watts output — fully adjustable.

SUPERIOR RECEIVER: Sensitivity is better than 0.15 microvolt for 20-db quieting. Commercial-grade design assures optimum dynamic range and noise suppression. COMPARE!

DIRECT FREQUENCY ENTRY: Streamlines channel selection and programming.

OTHER FEATURES: Rugged dynamic microphone, built-in speaker, mobile mounting bracket, remote speaker jack, and all cords, plugs, fuses and hardware are included.

EXCLUSIVE DISTRIBUTOR: DEALER INQUIRIES INVITED FOR YOUR NEAREST DEALER OR TO ORDER: AMATEUR-WHOLESALE ELECTRONICS TOLL FREE...800-327-3102 46 Greensboro Highway, Watkinsville, Georgia 30677 Telephone (404) 769-8706 Telex: 4930709 ITT



MANUFACTURER: JAPAN PIEZO CO., LTD.

1-12-17 Kamirenjaku, Mitaka, Tokyo, 181 Japan

Telex: 781-2822452

# The Nicest Things Come In Small Packages.

The SS-32HB is a new hybrid sub-audible encoder plucked from Communications Specialists' Hothouse. It has grown through a cross of the time tested SS-32, the subminiature SS-32M and space age micro circuitry. This programmable 32 tone encoder measures a scant .5 x 1.0 x .15 inches; no small wonder it allows the addition of continuous tone control to a bunch of hand held transceivers that lack space.

Why not snip your problems in the bud, with our fast, one day delivery and attractive one year warranty.






198





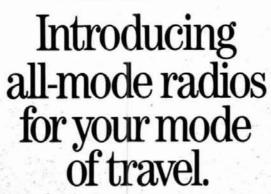

Yaesu's 2-meter FT-290R and 6-meter FT-690R Mark II Series are the perfect all-mode traveling companions.

On the road, simply snap on the heat sink, apply 12 volts of power, and you've got a 25-watt mobile station. (FT-690R: 10 watts).

On foot, attach the optional C-cell battery pack and shoulder strap, and take off with 2.5 watts RF output.

You get around fast on SSB, CW and FM with ten memories, dual VFOs, LCD display, automatic storage of repeater shift into memory register, offset tuning during receive or transmit for satellite operation, relative power output/S-meter, and optional CTCSS unit.

And everything fits into a lightweight-yet-rugged case, measuring just 21/4 x 61/2 x 81/4 inches.

The FT-290R and FT-690R Mark II are perfect for emergency use, camping trips, talking around town, and DX work. Plus each is priced to maximize your ham budget's mileage.

So discover Yaesu's 2-meter FT-290R Mark II and 6-meter FT-690R Mark II all-mode transceivers today. They're just a quick trip away at your nearest Yaesu dealer.



Yaesu USA 17210 Edwards Road, Cerritos, CA 90701 (213) 404-2700 Customer Service: (213) 404-4884 Parts: (213) 404-4847 Yaesu Cincinnati Service Center 9070 Gold Park Drive, Hamilton, OH 45011 (513) 874-3100

Prices and specifications subject to change without notice.

# KENWOOD

... pacesetter in Amateur radio

## Ultimate Affordable HT! TH-205AT 12 VDC input terminal—allows direct mobile or external / Heavy-duty final amplifier and he sink. The die-cast rear panel ass

KENWOOD

3

3

6

9

#

LAMP OFFSET/R SCAN

2

5

8

0

1

4

7

\*

Affordable 5-watt hand-held transceiver. Ultimate Affordability!

It's here now! The affordable. "Kenwood Quality" hand-held transceiver. Standard features include a large, easy-to-read LCD display, wide-range power requirements (operates on 7.2 VDC-16 VDC), 3-channel memory, built-in battery saver circuit, and, when operated on 12 VDC, a robust five watts of power! The diecast metal rear panel/heat sink assures cool, reliable operation. **Receiver frequency coverage** from 141-163 MHz is also standard-you can even listen to the "weather channels" at 162.40 or 162.55 MHz!

- Monitor switch—to check fre-quency when PL encode/ decode switch is on.
- Extended frequency coverage for certain MARS and CAP operations.
- 3 memory channels store frequency and offset. And so easy to use! Simply press the memory channel number to recall your favorite channels!
- . Night light, offset/reverse. -
- 16-key DTMF pad for repeater autopatch is standard.



 NEW! Twist-Lok Positive-Connect<sup>™</sup> battery case. A wide range of quickchange commercial duty battery packs are available.

Complete service manuals are available for all Trio. Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

 12 VDC input terminal—allows direct mobile or external power supply operation.
 When 12 VDC is applied, power output increases to 5 watts!

VHF


TUNE

M F.LOCK

TH-205AT

Heavy-duty final amplifier and heat sink. The die-cast rear panel assures reliable operation. With the optional 12-volt PB-1 battery pack, the TH-205AT provides 5 W output. The standard 8.4 volt PB-2 provides 2.5 W output. (300 mW low power).

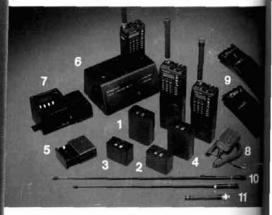- Large, easy-to-read LCD display. Frequency, offset, memory channel, TX, RX, and battery indicator.
- Frequency UP/DOWN keys. Used to select frequency or scanning direction.
- Scan function key.
- Automatic battery saver circuit extends battery life. No buttons to push!
- Supplied accessories include: Rubber flex antenna, belt hook, 8.4 V, 500 mAH NiCd battery pack, wall charger.



#### Optional Accessories.

PB-112 V 800 mAh NiCd batt. pack (5 W output)
 PB-2 8 4 V 500 mAh NiCd batt. pack (25 W output)
 PB-3 7 2 V 800 mAh NiCd batt. pack (15 W output)
 PB-3 7 2 V 800 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-4 7 2 V 1600 mAh NiCd batt. pack (15 W output)
 PB-3 7 2 V 100 mount
 PG-3 C Filtered cigar lighter cord.



TRIO-KENWOOD COMMUNICATIONS 1111 West Walnut Street Compton, California 90220