



ARRL Periodicals Archive – Search Results

A membership benefit of ARRL and the ARRL Technical Information Service

ARRL Members: You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

Need a higher quality reprint or scan? Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at www.arrl.org/tis or email photocopy@arrl.org.

QST on CD-ROM: Annual CD-ROMs are available for recent publication years. For details and ordering information, visit www.arrl.org/qst.

Non-Members: Get access to the ARRL Periodicals Archive when you join ARRL today at www.arrl.org/join. For a complete list of membership benefits, visit www.arrl.org/benefits.

Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.

For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: permission@arrl.org.

QST Issue: Dec 1966

Title: HW-12 Rattle

Author: Robert A. Sullivan, W0YVA/9

[Click Here to Report a Problem with this File](#)



2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

SEARCH the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

System Requirements: Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at www.adobe.com.

2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001

Only \$24.95*

*plus shipping and handling

Additional sets available:

2009 Ed., ARRL Order No. 1486, \$24.95
 2008 Ed., ARRL Order No. 9406, \$24.95
 2007 Ed., ARRL Order No. 1204, \$19.95
 2006 Ed., ARRL Order No. 9841, \$19.95
 2005 Ed., ARRL Order No. 9574, \$19.95
 2004 Ed., ARRL Order No. 9396, \$19.95
 2003 Ed., ARRL Order No. 9124, \$19.95
 2002 Ed., ARRL Order No. 8802, \$19.95
 2001 Ed., ARRL Order No. 8632, \$19.95



ARRL The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.
 ONLINE WWW.ARRL.ORG/SHOP
 ORDER TOLL-FREE 888/277-5289 (US)

HW-12 RATTLE

THOSE whose cars have developed mysterious rattles after the installation of a Heath HW-12, HW-22 or HW-32 might try removing the unit and bending back slightly the bracket that supports the lamp illuminating the meter. It seems that road vibration will cause the lamp to bump against the rear of the plastic meter case in a most annoying manner if the lamp is allowed to rest near the case. — Robert A. Sullivan, W0YVA/9

EQUALIZING THE LOW-VOLTAGE REQUIREMENTS OF THE HW-12 AND THE SB-100

AFTER reading W9LSZ's hint in QST for May 1966 on using the HP-23 a.c. power supply with both the HW-12 and the SB-100, I feel that it should be pointed out that there is an easier and safer way to accomplish the desired results. The HW-12 will operate from a low B-plus source as high as 325 volts (250 volts is normal) if the voltage supplied to the screens of

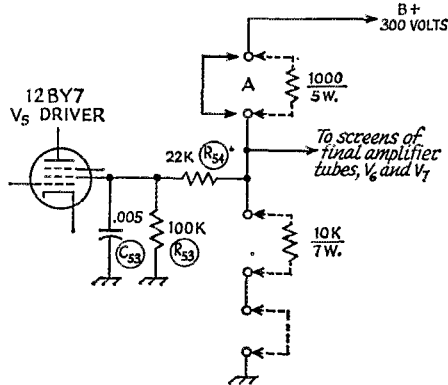


Fig. 4—To operate the Heath HW-12 from a low B-plus source of 300 volts, it is only necessary to remove the jumper from A and install the components shown in the dotted lines.

the driver and final-amplifier tubes is dropped to the proper value. As pointed out in the HW-12 instruction book and as shown in Fig. 4, it is only necessary to add two resistors and change a couple of jumpers to do this. The resistors required for the modification are a 1000-ohm, 5-watt unit and a 10,000-ohm, 7-watt unit.

The above modification has an added advantage over the previously described hint: if either

transceiver is operated mobile, the low B-plus tap in the HP-12 d.c. supply may be set at 300 volts, and the rigs will be interchangeable without attention to the power supply. Also, there is no switch that could be inadvertently left in the wrong position, permitting too high a voltage to be applied to the HW-12 and possibly burning out three tubes.

— Robert C. Clark, K9HVW/WA4VYL


TRANSISTOR POWER SUPPLY

THE circuit shown in Fig. 5 is an 8.7-volt 500-ma. electronically filtered transistor power supply based on a design submitted by Ralph W. Parlette, WB6JOY. Easily constructed, the supply is inexpensive, has good regulation and very low ripple. CR₁ through CR₄ form a bridge rectifier and C₁, a capacitor-input filter. Zener diode CR₅ provides the reference voltage for emitter-follower Q₁. C₂ smooths out the small amount of ripple that appears across CR₅. The effective capacitance across the load is equal to the current gain of Q₁ multiplied by the capacitance of C₂. R₁ limits the amount of Zener current through CR₅; it is adjusted for a Zener current of approximately 15 ma. (no load). C₃ is an r.f. bypass capacitor and R₂ provides a small (10 ma.) bleeder load for the supply.

The output voltage of the unit is equal to the Zener voltage minus the emitter-to-base bias voltage of Q₁. Other voltages can be obtained by using different Zeners and changing R₁. R₁ should be chosen so that the Zener will operate as a more or less constant voltage reference for the transistor regulator at output loads of 0 to 500 ma. yet stay within its maximum current rating when no external load is attached. Q₁ is not special; any similar power transistor should work. Of course, the higher the current gain of the transistor, the better will be the electronic filtering. Q₁ should be mounted on a heat sink.

Power-supply ripple at full load was measured with an oscilloscope at 4 millivolts r.m.s. Increasing both C₁ and C₂ to 1000 μf. lowered the ripple to approximately 1 millivolt r.m.s. If less filtering can be tolerated, removing C₂ from across the Zener will raise the ripple to 15 millivolts r.m.s. The output changed only 0.1 volt as the line voltage was varied over a 30-volt range. Increasing the external load current from 0 to 500 ma. dropped the output voltage 0.2 volt. — W1YDS

Fig. 5—Circuit diagram of regulated 8.7-volt transistor power supply.

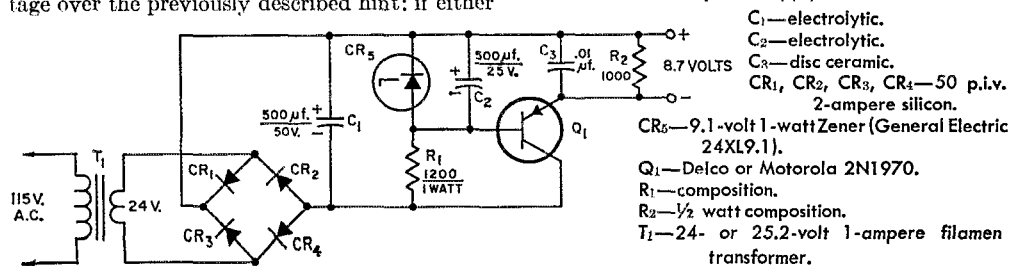

- C₁—electrolytic.
- C₂—electrolytic.
- C₃—disc ceramic.
- CR₁, CR₂, CR₃, CR₄—50 p.i.v. 2-ampere silicon.
- CR₅—9.1-volt 1-watt Zener (General Electric 24XL9.1).
- Q₁—Delco or Motorola 2N1970.
- R₁—composition.
- R₂—½ watt composition.
- T₁—24- or 25.2-volt 1-ampere filament transformer.